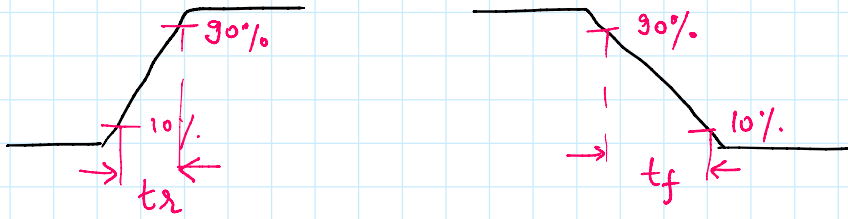


HW-1 posted online.

Rise time & Fall time



Characteristic Impedance:


$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \frac{a + ib}{a - ib}$$

Observations:



- 1) $Z_0 \rightarrow$ It is a complex quantity
- 2) Lossless Transmission line has "real" characteristic impedance

$$R=0 ; G=0 ; Z_0 = \sqrt{\frac{L}{C}} \} \text{ Real}$$

Reflections on a Transmission Line.

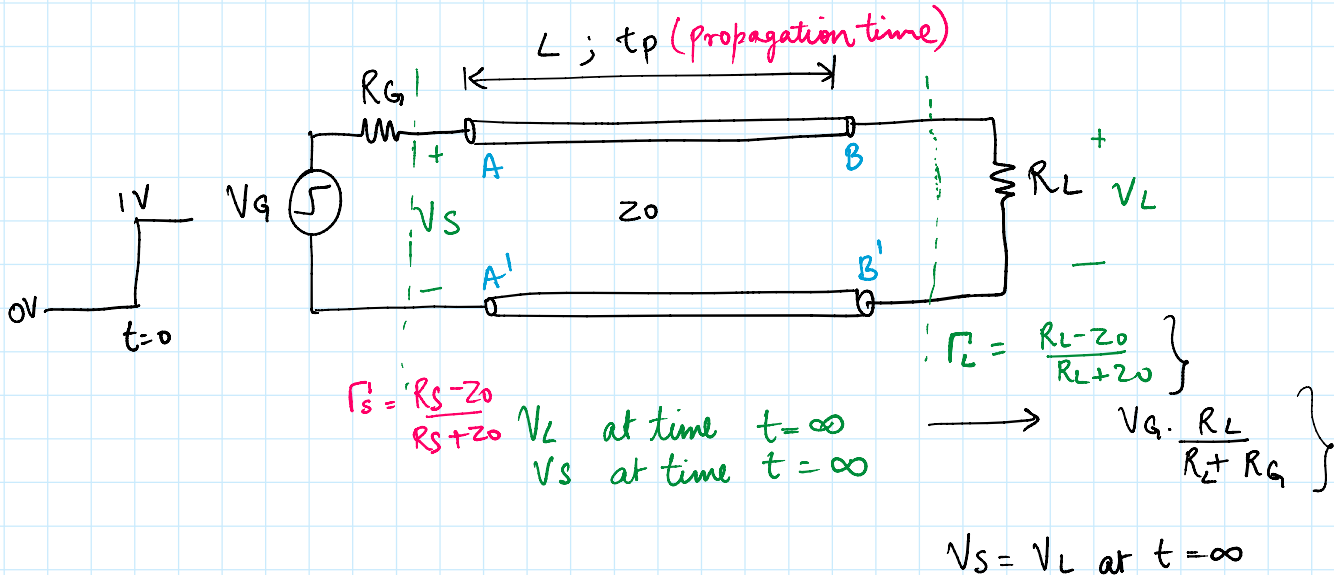

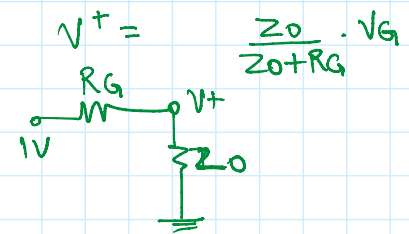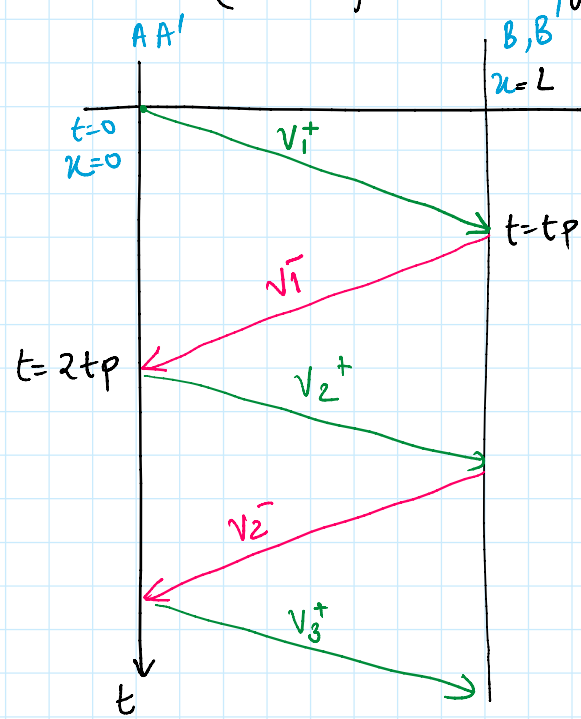{ Bounce Diagram or Lattice Diagram
or Reflection Diagram }



$$V_1^- = \Gamma_L \cdot V_1^+$$

Reflection coefficient at the load


$$V_2^+ = \Gamma_G \cdot V_1^-$$

$$V_2^- = \Gamma_L \cdot V_2^+$$


$$V_3^+ = \Gamma_G \cdot V_2^-$$

At $t = \infty$ the $V_n^+ = 0$
 $n \rightarrow \infty$

Example 1:

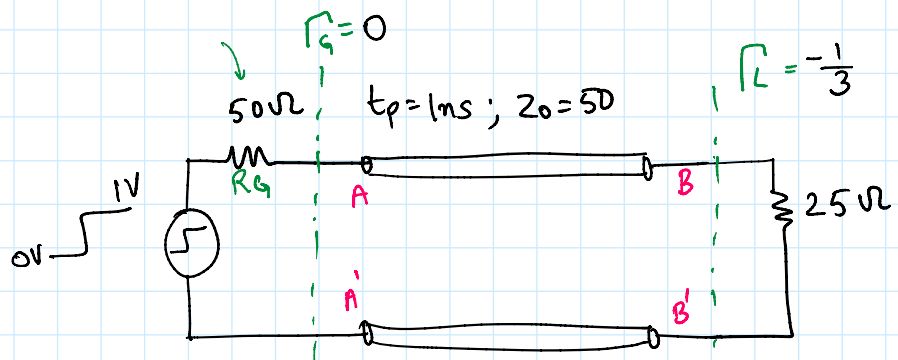

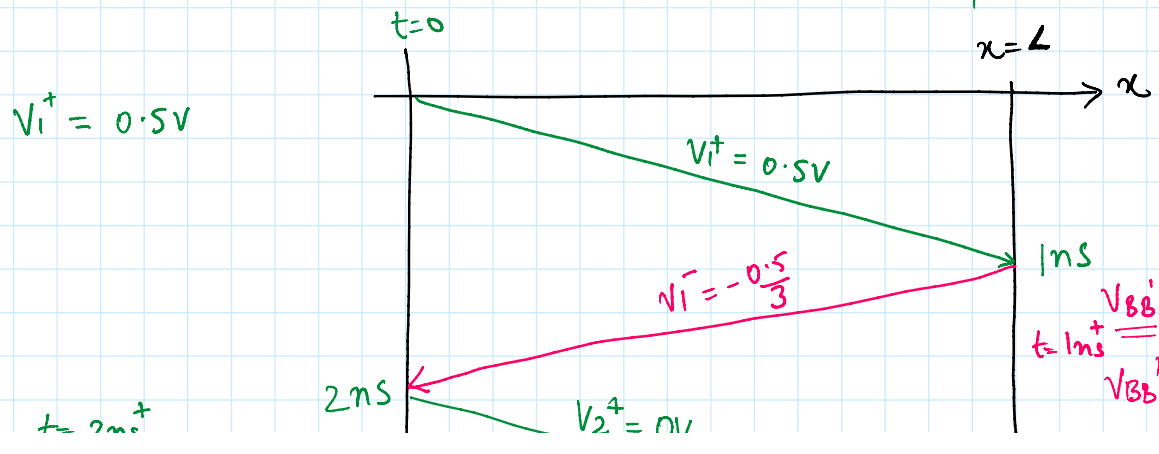
$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$



$$V_{BB}^+ = 0.5 \text{ V} - 0.5 \text{ V} \cdot \frac{1}{3}$$

$$V_{BB}^+ = 0.33 \text{ V}$$
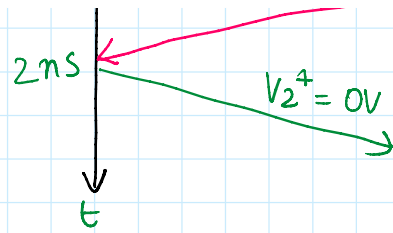
$$t = 2\text{ms}^+$$
$$V_{AA'} = V_1^+ + V_1^-$$
$$= 0.33\text{V}$$



$$t = 1\text{ms}^-$$
$$V_{BB'} = 0.33\text{V}$$