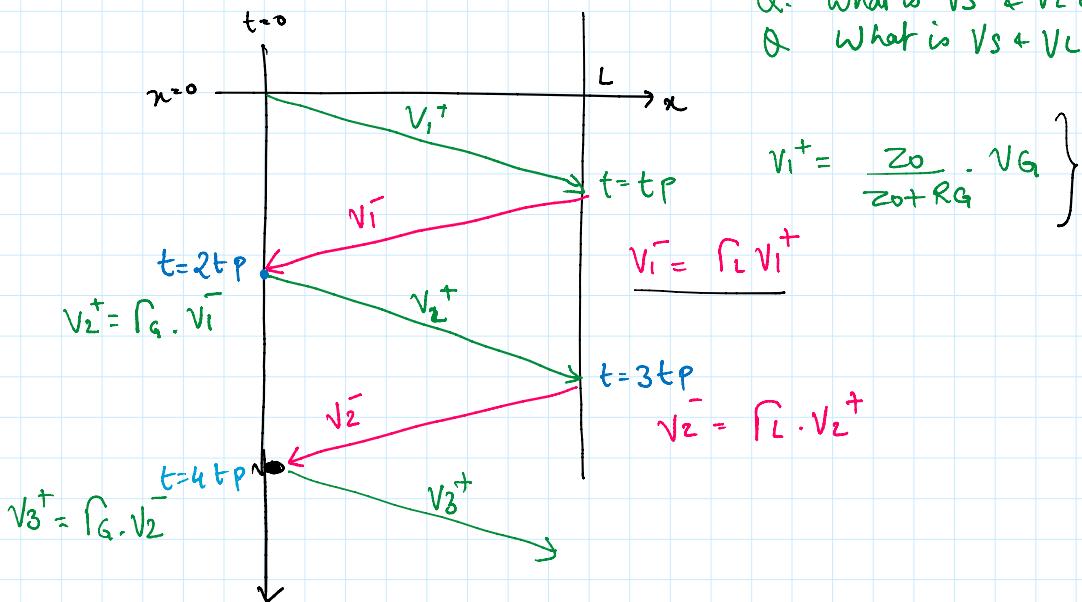


$$\Gamma_s = \frac{z_G - z_0}{z_G + z_0}$$

$$V_s = V_L \text{ at } t=\infty$$

Q: What is $V_s \leftarrow V_L$ at $t=\infty$?
Q: What is $V_s + V_L$ at any time t ?



$$V_i^+ = \frac{z_0}{z_0 + R_g} \cdot V_g$$

$$V_i^- = \Gamma_g V_i^+$$

$$V_2^- = \Gamma_L \cdot V_2^+$$

- Voltage near the generator (left side of T -line) at time t
 $t=0^+ = V_i^+$

$$t=2t_p^+ = V_i^+ + V_i^- + V_2^+ = V_i^+ + \Gamma_L V_i^+ + \Gamma_g V_i^- = V_i^+ + \Gamma_L V_i^+ + \Gamma_L \Gamma_g V_i^+$$

$$t=4t_p^+ = V_i^+ + V_i^- + V_2^+ + V_2^- + V_3^+ = V_i^+ + \Gamma_L V_i^+ + \Gamma_L \Gamma_g V_i^+ + \Gamma_L^2 \Gamma_g^2 V_i^+$$

$$t = \infty =$$

$$\sqrt{V_i^+} \left[1 + R_L + R_L^2 R_G + R_L^2 R_G^2 + R_L^2 R_G^3 + \dots \right]$$

$$= \sqrt{V_i^+} \left[1 + R_L R_G + R_L^2 R_G^2 + R_L^3 R_G^3 + \dots \right]$$

$$+ R_L \left\{ 1 + R_L R_G + R_L^2 R_G^2 + \dots \right\}$$

$$= \sqrt{V_i^+} \left[\frac{1}{1 - R_L R_G} + \frac{R_L}{1 - R_L R_G} \right]$$

$$= \sqrt{V_i^+} \left[\frac{1 + R_L}{1 - R_L R_G} \right]$$

$$= V_G \left[\frac{Z_0}{Z_0 + R_G} \right] \left[\frac{1 + \frac{R_L - Z_0}{R_L + Z_0}}{1 - \left(\frac{R_L - Z_0}{R_L + Z_0} \right) \left(\frac{R_G - Z_0}{R_G + Z_0} \right)} \right]$$

$$= V_G \left[\frac{Z_0}{Z_0 + R_G} \right] \cdot \left[\frac{\frac{R_L + Z_0 + R_L - Z_0}{R_L + Z_0}}{\frac{(R_L + Z_0)(R_G + Z_0) - R_L R_G + R_L Z_0 + R_G Z_0 - Z_0^2}{(R_L + Z_0)(R_G + Z_0)}} \right]$$


$$= V_G \left[\frac{Z_0}{Z_0 + R_G} \right] \left[\frac{\frac{2 R_L (R_G + Z_0)}{R_L R_G + R_L Z_0 + R_G Z_0 + Z_0^2 - R_L R_G + R_L Z_0 + R_G Z_0 - Z_0^2}}{\frac{2 R_L (R_G + Z_0)}{R_L R_G + R_L Z_0 + R_G Z_0 + Z_0^2 - R_L R_G + R_L Z_0 + R_G Z_0 - Z_0^2}} \right]$$

$$= \frac{V_G \cdot Z_0 \cdot 2 R_L}{2 Z_0 [R_L + R_G]}$$

Voltage max at generator at $t = \infty$ = $V_G \cdot \frac{R_L}{R_L + R_G}$ = Voltage at load at $t = \infty$

Voltage max at generator at $t = \infty$ = $V_g \cdot \frac{R_L}{R_L + R_g}$ = Voltage at load at $t = \infty$

Example:

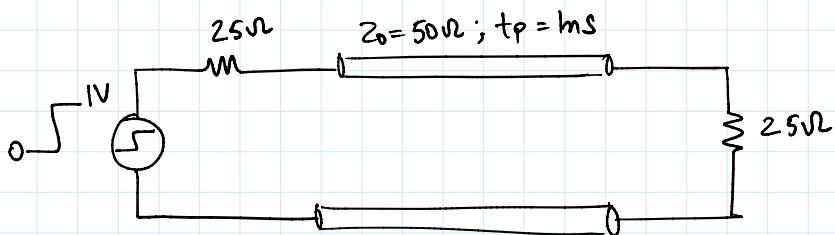

$$r_g = -1/3$$

$$V_1^+ = 2/3$$

$$r_L = -\frac{1}{3}$$

$$V_1^- = -2/9$$

$$V_2^+ = -\frac{2}{9} \times -\frac{1}{3} = \frac{2}{27}$$