


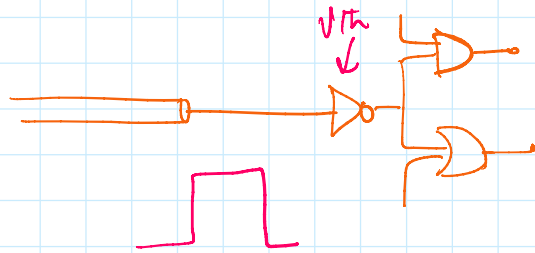
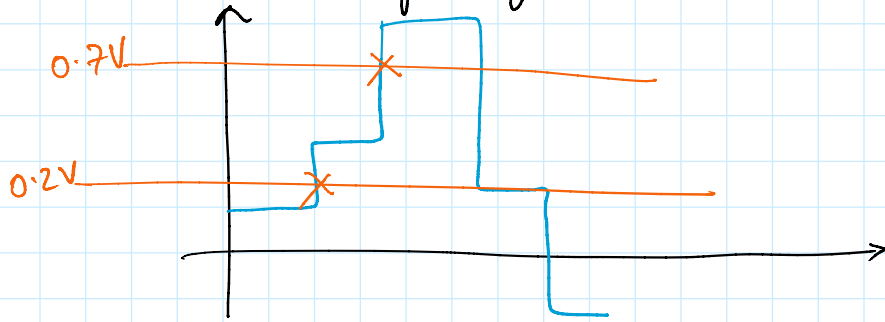
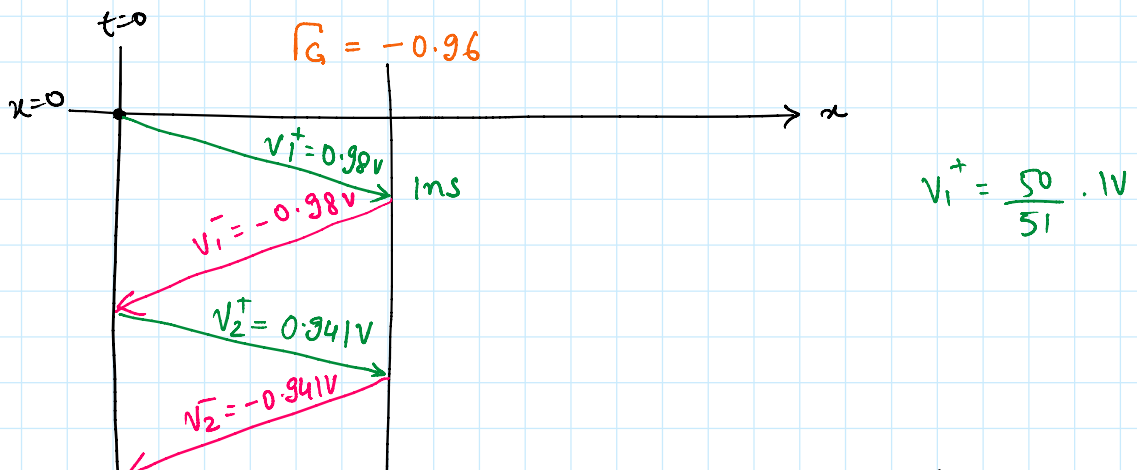
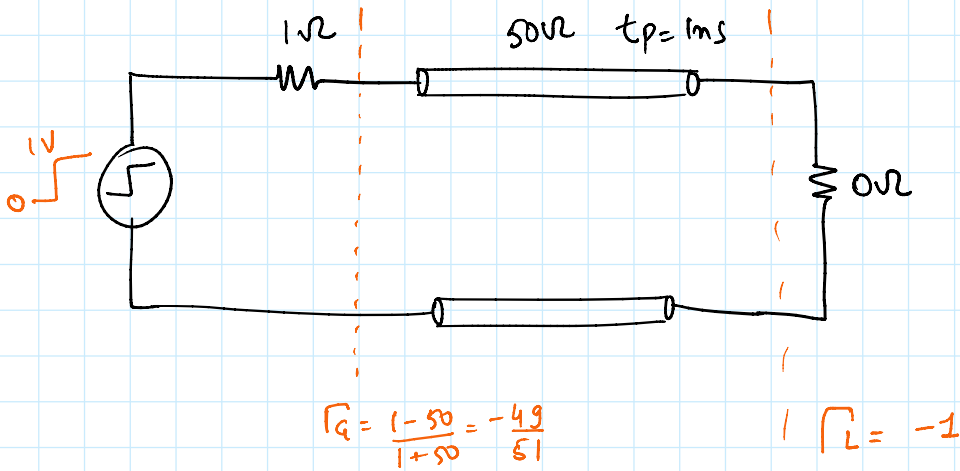


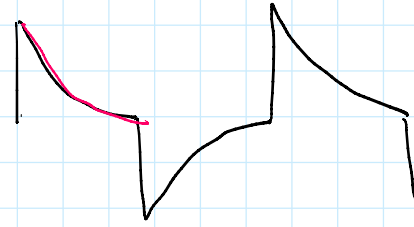Problem of digital logic due to reflections




Transmission Line Terminated by a short.

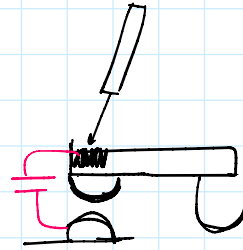

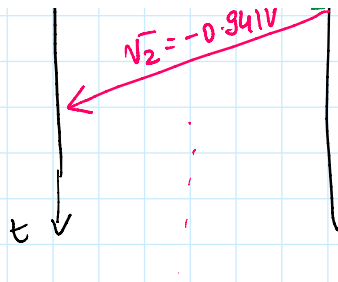

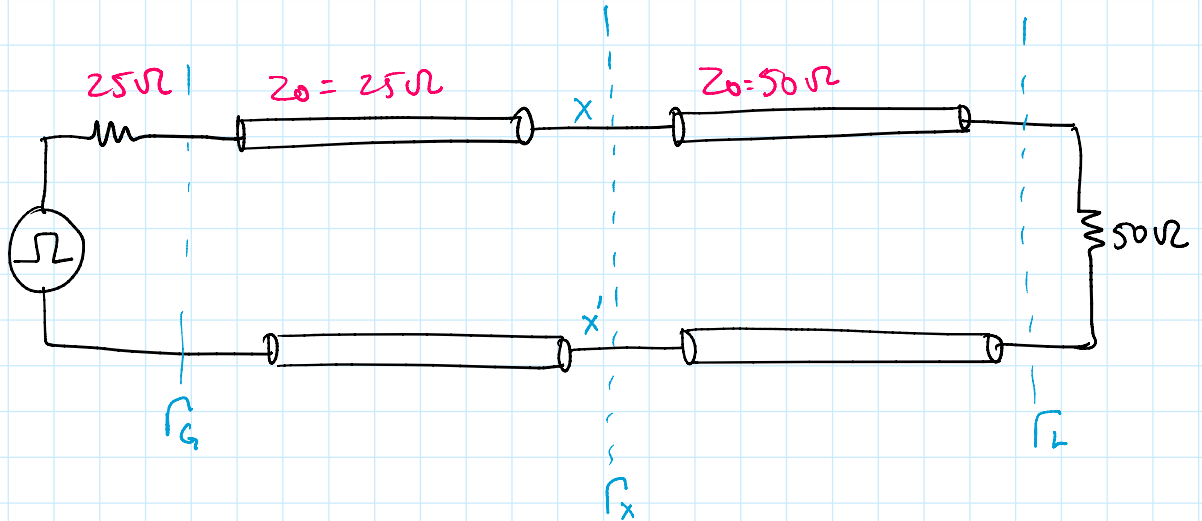Connection of Tx Lines with different characteristic impedance



Estimating V & I at any point in a transmission line

$$V(l) = V^+ e^{\gamma l} \{ 1 + \Gamma(l) \} \quad \text{--- (1)}$$

$$I(l) = \frac{I^+ e^{\gamma l}}{Z_0} \{ 1 - \Gamma(l) \} \quad \text{--- (2)}$$

$$\Gamma(l) = \frac{V^+ e^{-\gamma l}}{V^- e^{\gamma l}}$$

Divide eq (1) & (2)

Divide eq. (1) & (2)

$$Z(l) = \frac{V(l)}{I(l)} = Z_0 \left\{ \frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right\} \quad (3)$$

$$V^- e^{-\gamma l}$$

$$\Gamma(l) = \Gamma_L e^{-2\gamma l}$$

$$\Gamma_L = \frac{V^+}{V^-}$$

Reflection coefficient at the load end



Impedance seen at any point in a transmission line.

$$\Gamma(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0} \quad (4)$$

$$Z(l) = Z_0 \left\{ \frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right\}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$


$$Z(l) = Z_0 \left\{ \frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0} \cdot e^{-2\gamma l}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l}} \right\}$$

Impedance Transformation Relation.

$$Z(l) = Z_0 \left\{ \frac{Z_L \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_L \sinh \gamma l} \right\}$$

$$\cosh \gamma l = \frac{e^{\gamma l} + e^{-\gamma l}}{2}$$
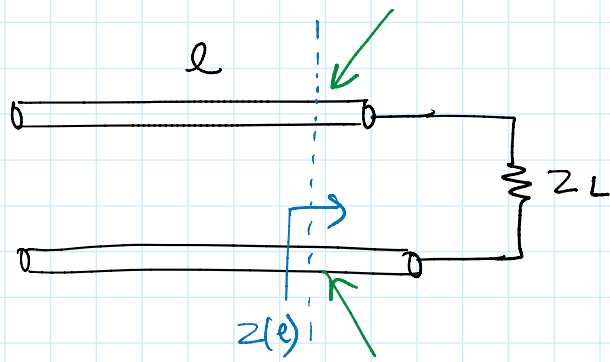
$$\sinh \gamma l = \frac{e^{\gamma l} - e^{-\gamma l}}{2}$$



$$\sinh \gamma l = \frac{e^{\gamma l} - e^{-\gamma l}}{2}$$