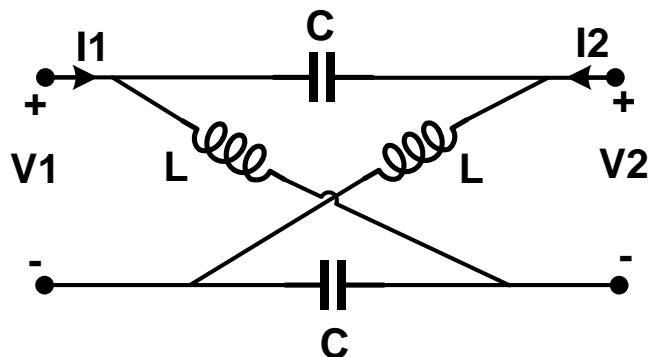


# ECE580 HW-1


Due Oct 12, 2016 in the class

Q1:

- (a) Calculate Z parameters of the following network.



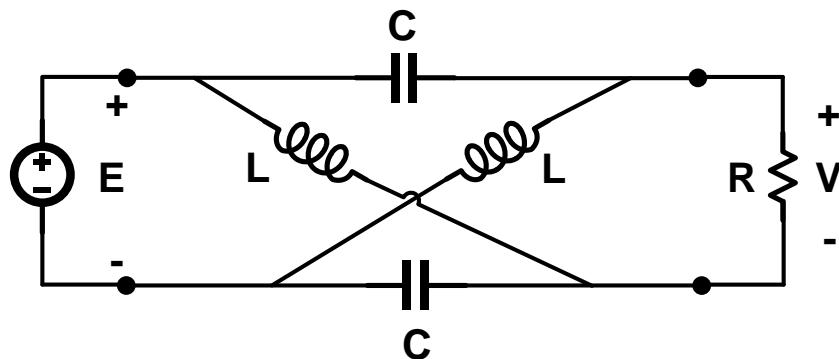- (b) Calculate V/E for the following network.



Q2: Calculate the transmission zero of the following network.

