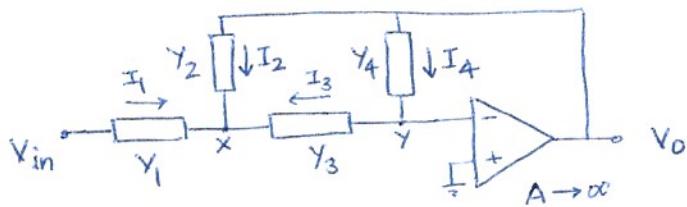


HOMEWORK 3

(Q1)



$$(a) \quad V_y = 0$$

KCL at NODE Y,

$$I_3 = I_4 \quad \text{---} \quad ①$$

KCL at NODE X,

$$I_1 + I_2 + I_3 = 0$$

$$(V_{IN} - V_x)Y_1 + (V_o - V_x)Y_2 - V_x Y_3 = 0$$

$$V_{IN}Y_1 + V_o Y_2 - V_x (Y_1 + Y_2 + Y_3) = 0$$

$$I_4 = V_o Y_4$$

$$V_x = -\frac{I_3}{Y_3}$$

USING ①,

$$V_x = -V_o \frac{Y_4}{Y_3}$$

$$\therefore V_{IN}Y_1 + V_o Y_2 + V_o \frac{Y_4}{Y_3} (Y_1 + Y_2 + Y_3) = 0$$

$$V_{IN}Y_1 = -V_o \left[Y_2 + \frac{Y_4}{Y_3} (Y_1 + Y_2 + Y_3) \right]$$

$$\frac{V_o}{V_{IN}} = \frac{-Y_1 Y_3}{Y_2 Y_3 + Y_4 (Y_1 + Y_2 + Y_3)}$$

(b) FOR A BANDPASS SYSTEM, THE TRANSFER FUNCTION IS OF THE FORM,

$$H(s) = \frac{A_0 \left(\frac{\omega_0}{Q} \right) s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

THERE ARE 2 POSSIBLE SOLUTIONS,

CASE 1 $Y_1 = \frac{1}{R} = G$ & $Y_3 = SC$

SINCE DENOMINATOR IS SECOND ORDER, ATLEAST TWO OF THE ELEMENTS HAVE TO BE CAPACITORS.

SAY $Y_4 = SC$ & $Y_2 = \frac{1}{R} = G$

$$H(s) = \frac{-SCG}{SGC + SC(G+G+SC)} = \frac{-SCG}{SC(3G+SC)}$$

THIS CANNOT BE A SOLUTION.

THEREFORE,

$$\boxed{\begin{array}{ll} Y_1 = \frac{1}{R} = G & Y_3 = SC \\ Y_2 = SC & Y_4 = \frac{1}{R} = G \end{array}}$$

$$H(s) = \frac{-SCG}{S^2C^2 + G(2SC + G)}$$

$$\boxed{H(s) = \frac{-S\frac{G}{C}}{S^2 + 2S\frac{G}{C} + \frac{G^2}{C^2}}}$$

CASE 2 $Y_1 = SC$ $Y_3 = \frac{1}{R} = G$

USING THE SAME ARGUMENTS AS IN CASE 1, ONLY POSSIBLE COMBINATION IS,

$$\boxed{\begin{array}{ll} Y_1 = SC & Y_3 = \frac{1}{R} = G \\ Y_2 = \frac{1}{R} = G & Y_4 = SC \end{array}}$$

$$\cancel{H(s) = \frac{-SCG}{G + G(SC + SC + G)}}$$

$$H(s) = \frac{-SCG}{G^2 + SC(SC + G + G)}$$

$$H(s) = \frac{-sG/C}{s^2 + 2sG/C + G^2/C^2}$$



c) $\omega_0^2 = \frac{G^2}{C^2}$

$$\therefore \omega_0 = \frac{G}{C} = \frac{1}{RC}$$

$$\frac{\omega_0}{C} = 2 \frac{G}{C}$$

$$\therefore Q = \frac{C\omega_0}{2G} = \frac{1}{2}$$

(82)

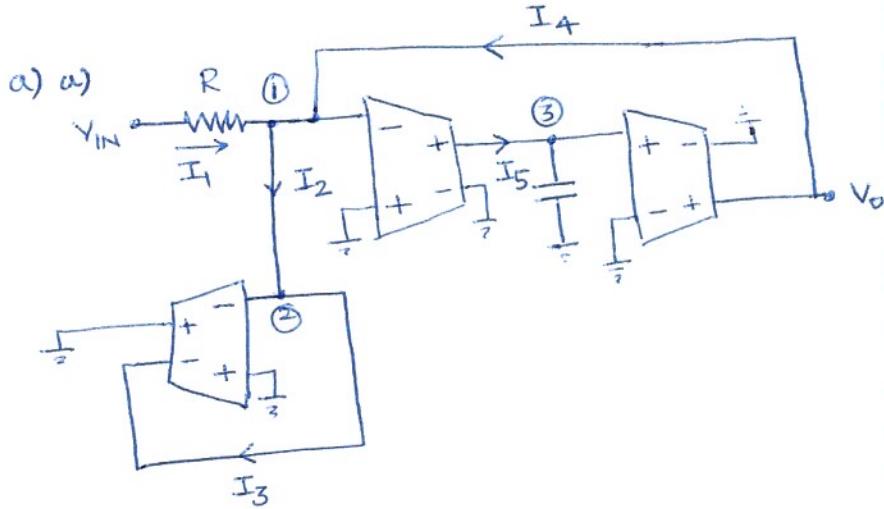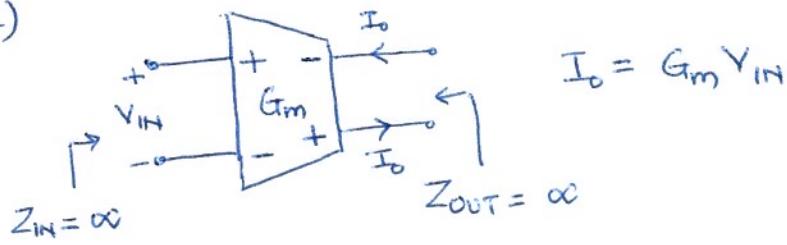

NODE 1 & NODE 2 ARE THE SAME (SHORTED)

$$V_1 = V_2 = V_o$$

$$I_3 = I_2 = -G_m V_o$$

KCL AT NODE 1

$$I_1 + I_4 = I_2$$

$$\frac{V_{IN} - V_o}{R} + G_m V_3 = -G_m V_o \quad -\textcircled{1}$$

KCL AT NODE 3

$$I_5 = V_3 SC$$

$$V_3 = \frac{I_5}{SC}$$

$$\text{BUT } I_5 = -G_m V_o$$

$$\therefore V_3 = -\frac{G_m V_o}{SC}$$

SUBSTITUTING V_3 IN EQN. $\textcircled{1}$

$$\frac{V_{IN}}{R} = V_o \left[\frac{1}{R} - G_m \right] + \frac{G_m^2 V_o}{SC}$$

$$V_{IN} = V_o \left[1 - G_m R + \frac{G_m^2 R}{SC} \right]$$

$$\therefore \frac{V_o}{V_{IN}} = \frac{SC}{(1-G_m R)SC + G_m^2 R}$$

$$\boxed{\frac{V_o}{V_{IN}} = \frac{\frac{SC}{G_m^2 R}}{1 + SC \frac{(1-G_m R)}{G_m^2 R}}}$$

a) b)

$$\frac{V_o}{V_{IN}} = \frac{\frac{s}{1-G_m R}}{s + \frac{G_m^2 R}{(1-G_m R)C}}$$

FOR A STABLE FILTER, POLE MUST BE IN LHP,

$$\therefore s = \frac{-G_m^2 R}{(1-G_m R)C} < 0$$


Since $G_m > 0, R > 0 \& C > 0$

$$1 - G_m R > 0$$

$$\therefore G_m R < 1$$

$$\boxed{G_m < \frac{1}{R}}$$

b)

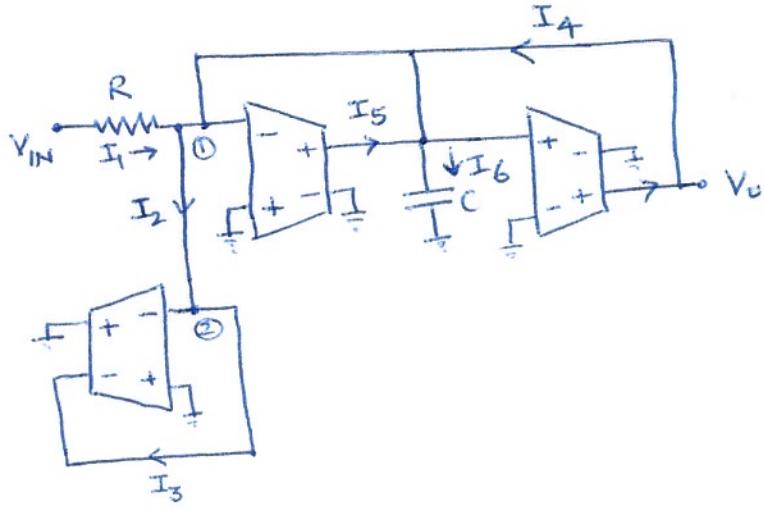

KCL AT NODE ①

$$I_1 + I_5 + I_4 = I_2 + I_6$$

$$I_1 = \frac{V_{IN} - V_o}{R}$$

$$I_5 = -G_m V_o$$

$$I_4 = G_m V_o$$

$$I_2 = I_3 = -G_m V_o$$

$$I_6 = V_o S C$$

$$\therefore \frac{V_{IN} - V_o}{R} - G_m V_o + G_m V_o = -G_m V_o + V_o S C$$

$$\frac{V_{IN}}{R} = V_o \left[\frac{1}{R} - G_m + S C \right]$$

$$V_{IN} = V_o [1 - G_m R + S R C]$$

$$\boxed{\frac{V_o}{V_{IN}} = \frac{1}{1 - G_m R + S R C}}$$