

# CMOS Integrated Circuits I

## Operational Amplifier Design Project

Emily Becher  
Nicholas Kim

December 2023

### Contents

<b>1</b>	<b>Design Objective</b>	<b>2</b>
<b>2</b>	<b>Design Process</b>	<b>2</b>
<b>3</b>	<b>Cadence Simulation Results</b>	<b>3</b>
3.1	Result Tables and Schematics . . . . .	3
3.2	Simulation Plots . . . . .	6

# 1 Design Objective

The objective of the project is to design a two-stage single-ended CMOS operational amplifier in the 0.18 $\mu$ m process with the following specifications:

- Load capacitance: 4pF
- Power supply:  $V_{dd} = 0.9\text{V}$ ,  $V_{ss} = -0.9\text{V}$
- Open-loop gain:  $\geq 60\text{dB}$
- Phase margin:  $\geq 60^\circ$
- Unity gain frequency:  $\geq 12\text{MHz}$

# 2 Design Process

The first step in the design process was to determine a CMOS configuration that would meet the requirements. This op-amp was implemented with a single-ended differential amplifier followed by a telescopic cascode gain stage.

After calculating the differential gain of the op-amp in terms of  $gm$  and  $r_{ds}$ , the  $gm$  and  $r_{ds}$  values were assumed to be equal across all gain stage devices in order to approximate a  $gm$ - $r_{ds}$  relationship that would achieve a DC gain well above the requirement.

By setting a  $gm$  of 1mS, a transconductance efficiency of 10 for moderate inversion was targeted on all gain stage devices in order to determine an  $I_d$  of 0.1mA. In Cadence simulations on isolated NMOS and PMOS devices, an  $I_d$  of 0.1mA was set to determine device sizes such that  $gm = 1\text{mS}$ . The drain-source resistances, channel length modulation parameters, transconductance parameters, and threshold voltages were determined for NMOS and PMOS devices during this step.

The differential amplifier and telescopic cascode are supplied by a current mirror, approximating a current draw of 0.5mA and power consumption of 0.9mW.

Initial calculations and fine-tuning in Cadence simulation determined the bias voltages on the telescopic cascode achieving saturation on all devices with a DC output of  $\approx 0\text{V}$ .

The final design choice was to shift the pole frequencies by adding a capacitor across the output and  $V_{ss}$  to achieve an appropriate phase margin at  $\approx 80^\circ$ .

### 3 Cadence Simulation Results

#### 3.1 Result Tables and Schematics

Requirement	Specification	Simulated Result
Load capacitance	4pF	4pF
Power supply	$V_{dd} = 0.9V$ , $V_{ss} = -0.9V$	$V_{dd} = 0.9V$ , $V_{ss} = -0.9V$
Open-loop gain	$\geq 60dB$	73.6dB
Phase margin	$\geq 60^\circ$	80.3°
Unity gain frequency	$\geq 12MHz$	48.8MHz
Power	N/A	0.878mW


Table 1: Specifications and Simulated Results

Device label	Width	Length	Drain-source current
NM0	3.5 $\mu m$	180nm	94.4572 $\mu A$
NM1	3.5 $\mu m$	180nm	94.4572 $\mu A$
NM2	3.5 $\mu m$	180nm	96.581 $\mu A$
NM3	3.5 $\mu m$	180nm	96.581 $\mu A$
PM0	24 $\mu m$	180nm	193.162 $\mu A$
PM1	12 $\mu m$	180nm	94.4572 $\mu A$
PM2	12 $\mu m$	180nm	94.4572 $\mu A$
PM3	12 $\mu m$	180nm	96.581 $\mu A$
PM4	12 $\mu m$	180nm	96.581 $\mu A$
PM5	12 $\mu m$	180nm	200 $\mu A$

Table 2: Device sizes and drain-source currents (see Figure 3)

Node label	DC voltage
$V_{dd}$	0.9V
$V_{ss}$	-0.9V
$V_1$	242.893mV
$V_2$	356.267mV
$V_3$	-227.625mV
$V_4$	-227.625mV
$V_5$	-300.267mV
$V_6$	410.267mV
$V_{b1}$	385mV
$V_{b2}$	-250mV
$V_{out}$	-0.936mV

Table 3: DC voltages at all nodes (refer to Figure 2 node labels)

 

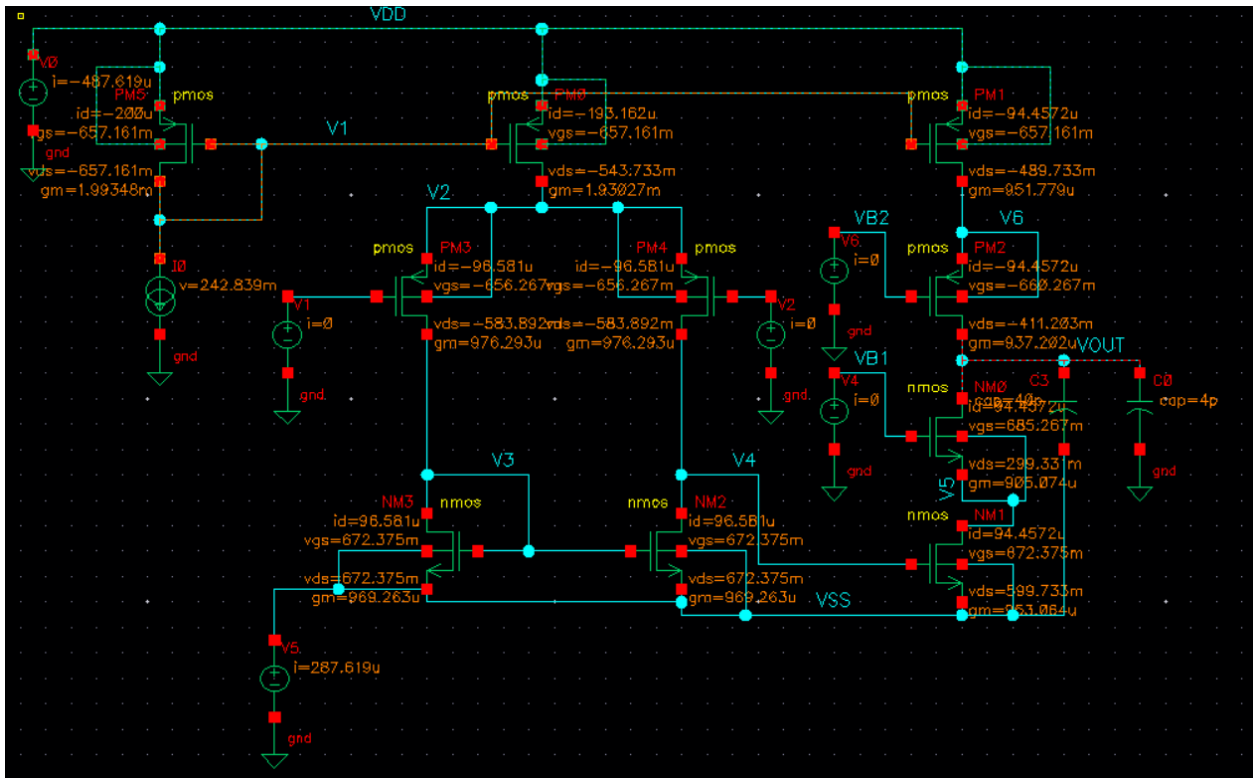


Figure 3: Schematic with Device Currents

### 3.2 Simulation Plots

 


Figure 4: Common-Mode Input Range

Figure 4 is a plot of all transistor regions of operation as a function of the common-mode input voltage. Region 2 indicates saturation. The op-amp has a common-mode input range of approximately  $-325\text{mV}$  to  $-285\text{mV}$ .

 


Figure 5: Output Swing

Figure 5 is a plot of the gain as a function of the output voltage. The DC gain of the op-amp is 73.627dB. The output swing is defined as the output voltage range within which the gain remains within 3dB of the DC gain. The op-amp has an output swing of approximately  $-142\text{mV}$  to  $145\text{mV}$ .

 


Figure 6: Open-Loop Gain

 


Figure 7: Gain and Phase Plots

Figures 6 and 7 are gain and phase plots. The DC gain is 73.627dB. The unity gain frequency is 48.797MHz. The phase margin is 80.3442°.