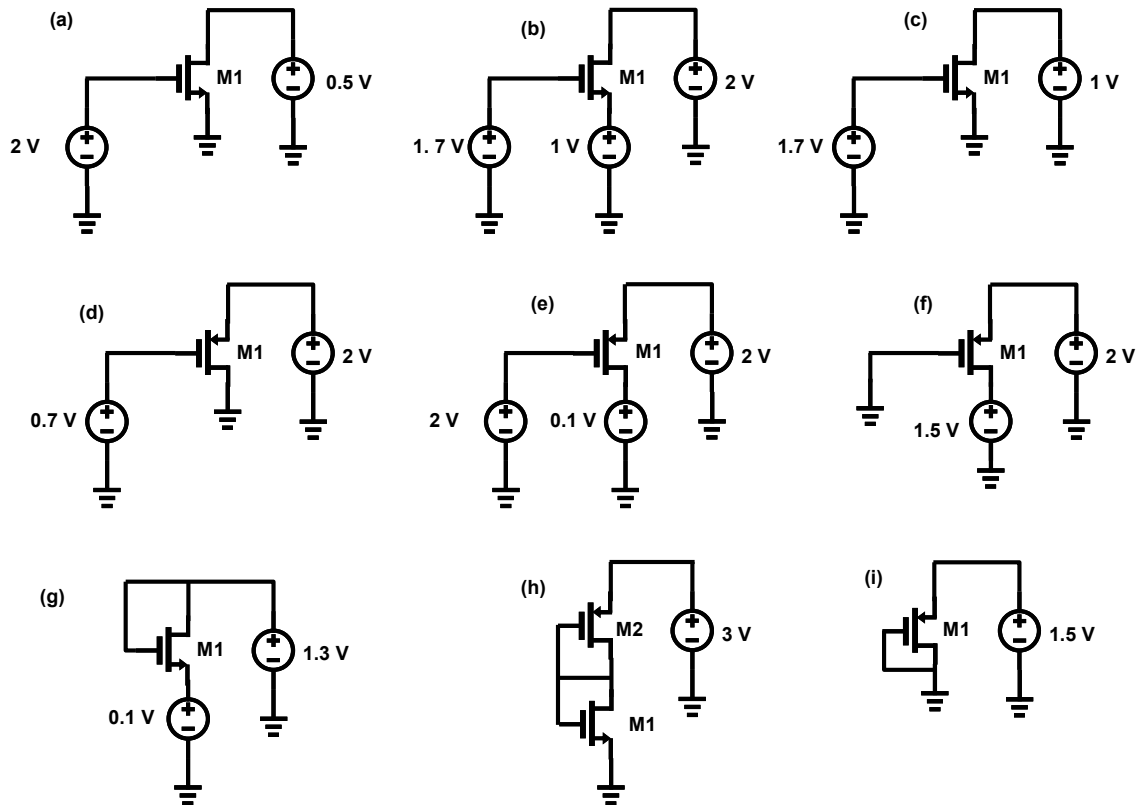


ECE 323 Homework 1

- 1) Determine the region of operation of M1 in each of the circuits below.
Assume $V_{THN} = |V_{THP}| = 1 \text{ V}$.



$$V_{GS} < V_{TH} \rightarrow \text{cutoff}$$



$$0 < V_{GS} - V_{TH} < V_{DS} \rightarrow \text{saturation}$$

$$0 < V_{GS} - V_{TH} > V_{DS} \rightarrow \text{triode}$$

(a) triode (b) cutoff (c) sat. (d) sat. (e) cutoff

(f) triode (g) sat. (h) sat. (i) sat.

- 2) What value of W/L places M1 at the brink of saturation? $V_{THN} = |V_{THP}| = 1\text{ V}$,
 $\mu_n C_{ox} = 100\text{ uA/V}^2$ $\mu_p C_{ox} = 50\text{ uA/V}^2$

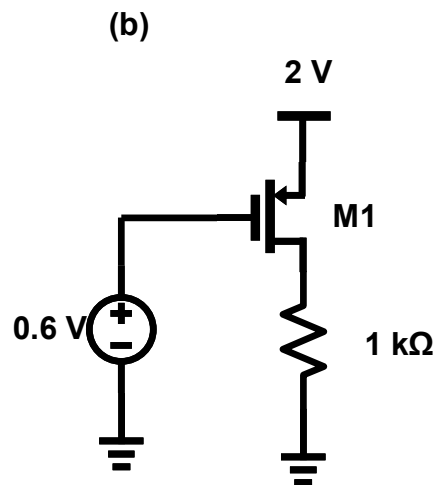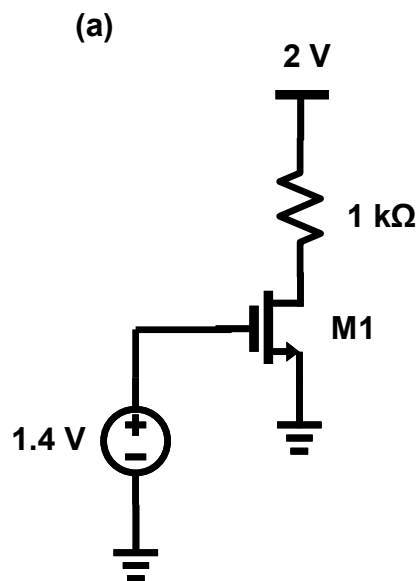


Brink of saturation $\rightarrow V_{DS} = V_{GS} - V_{TH}$
 Either triode or sat. equation works.

(a) $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 = 1.6\text{ mA} \rightarrow \left(\frac{W}{L}\right)_{M1} = 200$

(b) $\mu_p C_{ox} = \frac{1}{2} \mu_n C_{ox}$

Similar conditions of sat. $\rightarrow I_D \rightarrow \left(\frac{W}{L}\right)_{M1} = 400$

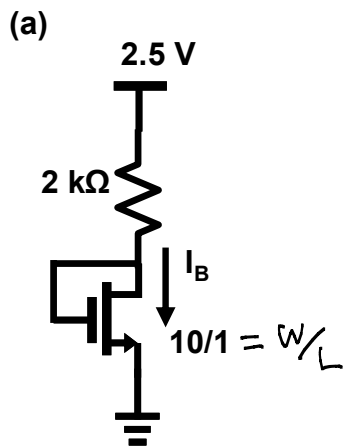3) Determine I_B in the following circuits. Use parameters from problem 2.




Sat. region

$$I_B = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2$$

$$\rightarrow V_B = 1.82 \text{ V}$$

$$I_B = 338.5 \mu\text{A}$$

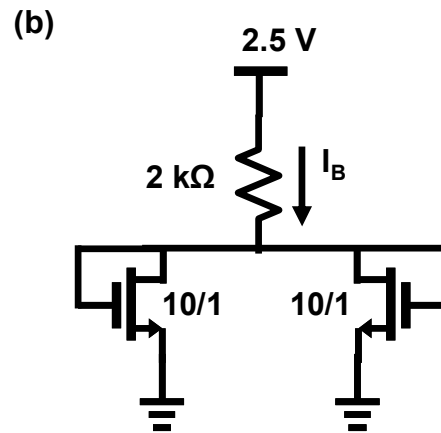


Sat.

$$\left[\left(\frac{10}{1} \right)^2 + \left(\frac{10}{1} \right)^2 \right] = \left(\frac{20}{1} \right)^2 = \frac{W}{L}$$

$$V_B = 1.65 \text{ V}$$

$$I_B = 425 \mu\text{A}$$

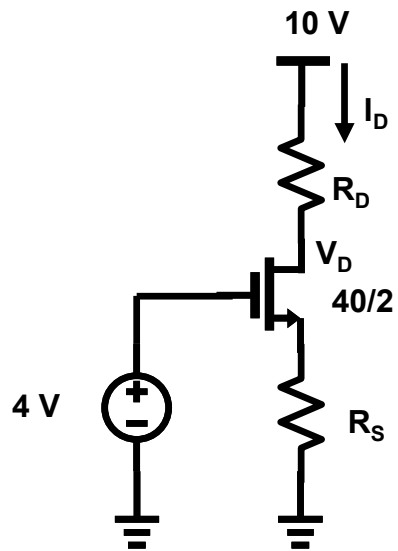- 4) Design the circuits below such that $I_D = 2\text{mA}$ and $V_D = 5\text{V}$. $V_{\text{THN}} = 1\text{V}$, $\mu_n C_{\text{ox}} = 100\text{ uA/V}^2$.




$V_D = 5\text{V}$ means in saturation.

$$I_D = \frac{10 - V_D}{R_D} \quad 4\text{V} = V_{GS} + I_D \cdot R_S = V_{GS} + V_S$$

Solving for I_D, V_S

$$R_D = 2.5\text{K}\Omega \quad V_S \approx 1.6\text{V} \quad R_S \approx 800\Omega$$

- 5) For the circuits in Fig 5, find values for the labeled node voltages and branch currents. Assume β to be very high and $|V_{BE}| = 0.7 \text{ V}$

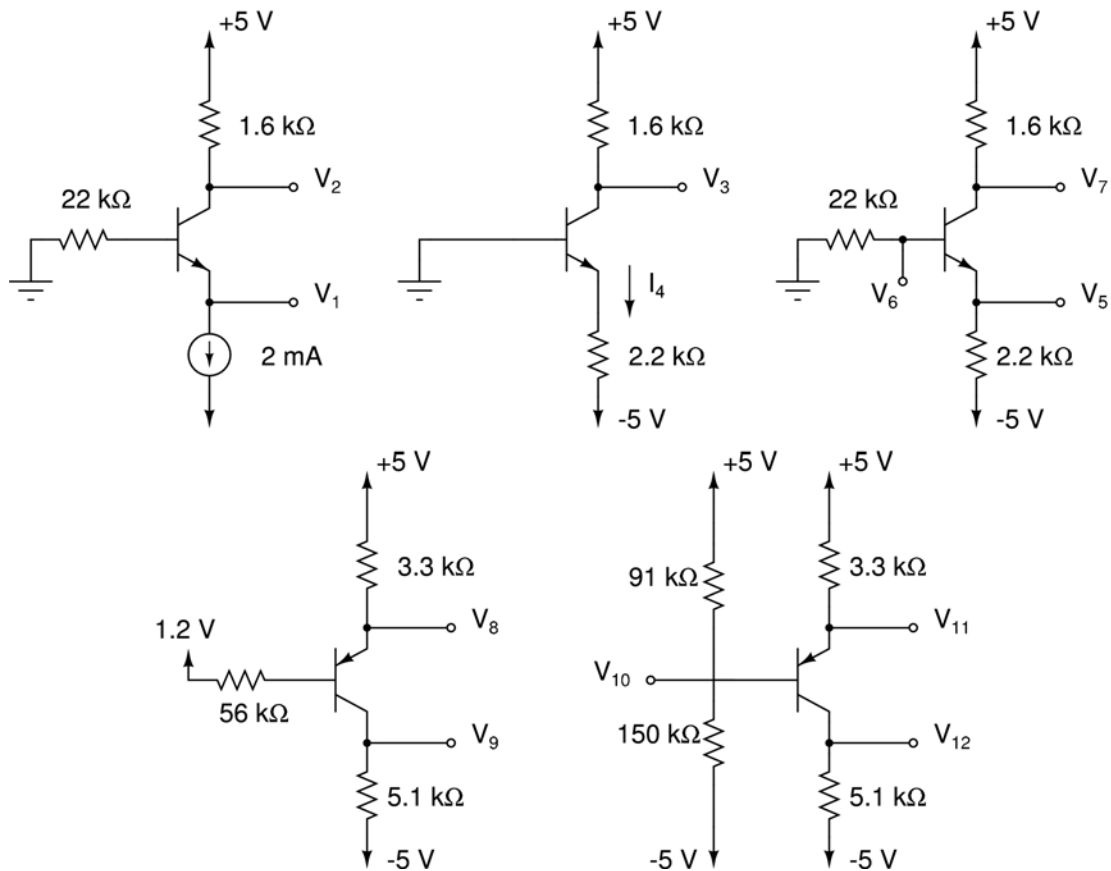

β is very high = no base current.

$$I_B = 0, \quad I_C = I_E$$

$$V_1 = -0.7 \text{ V}$$

$$V_2 = 1.8 \text{ V}$$

$$V_3 = 1.88 \text{ V}$$

$$I_4 = 1.95 \text{ mA}$$

$$V_5 = -0.7 \text{ V}$$

$$V_6 = 0 \text{ V}$$

$$V_7 = 1.88 \text{ V}$$

$$V_8 = 1.9 \text{ V}$$

$$V_9 = -0.2 \text{ V}$$

$$V_{10} = 1.224 \text{ V}$$

$$V_{11} = 1.924 \text{ V}$$

$$V_{12} = -0.24 \text{ V}$$