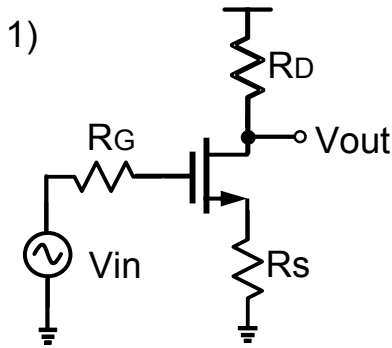


ECE323

Homework 2


Find expression for R_{in} , R_{out} and small signal voltage gain for the circuit shown below.

Assume: 1) $r_o = \infty$, 2) All transistor are biased in saturation.




$$R_{in} = \infty \quad R_{out} = R_D$$

$$Gain = \frac{-g_m R_D}{1 + g_m R_S}$$

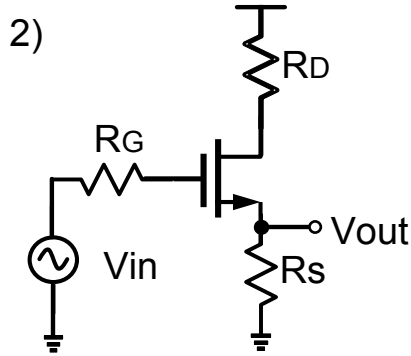


$$R_{in} = \infty \quad R_{out} = R_S \parallel \frac{1}{g_m}$$

$$Gain = \frac{g_m R_S}{1 + g_m R_S}$$

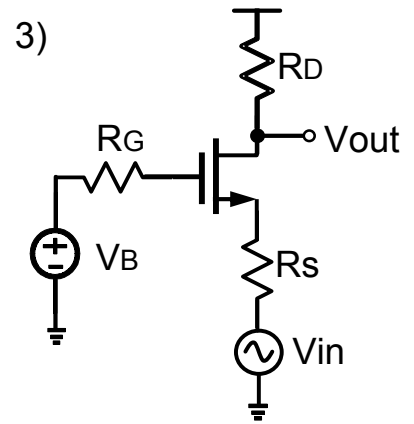


$$R_{in} = R_S + \frac{1}{g_m} \quad R_{out} = R_D$$

$$Gain = \frac{g_m R_D}{1 + g_m R_S}$$

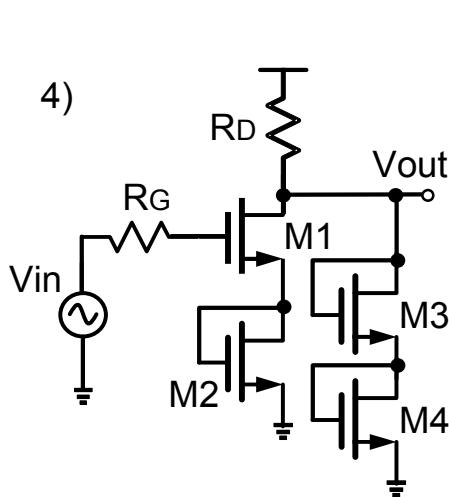

$$R_{in} = \infty \quad R_{out} = R_D \parallel \left(\frac{1}{g_{m3}} + \frac{1}{g_{m4}} \right)$$

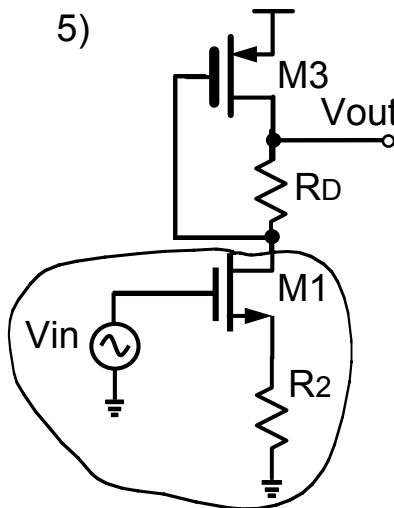
$$Gain = \frac{-g_{m1} R_{out}}{1 + g_{m1} \frac{1}{g_{m2}}}$$



$$\parallel \frac{g_{m1} V_{in}}{1 + g_{m1} R_2}$$







$$R_{in} = \infty \quad R_{out} = \frac{1}{g_{m3}}$$
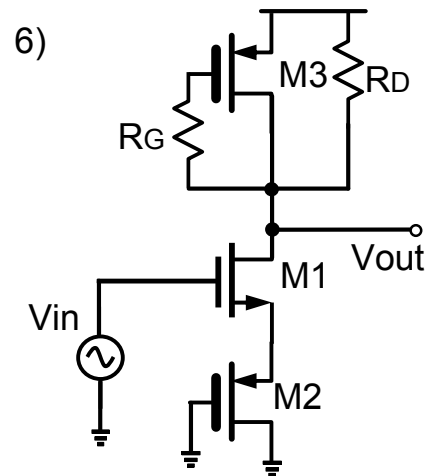
$$Gain = \frac{g_{m1}}{1 + g_{m1} R_2} (R_D g_{m3} - 1) \frac{1}{g_{m3}}$$




$$R_{in} = \infty \quad R_{out} = R_D \parallel \frac{1}{g_{m3}}$$
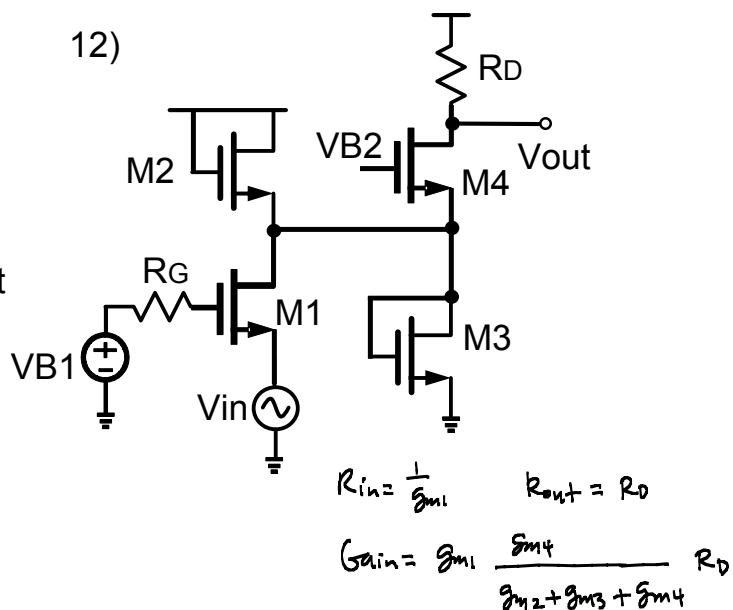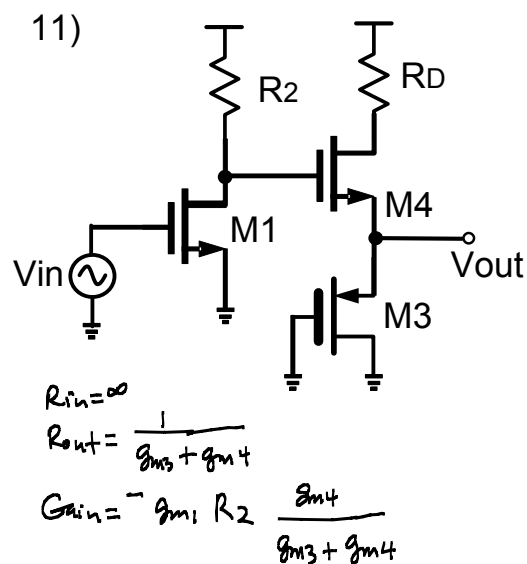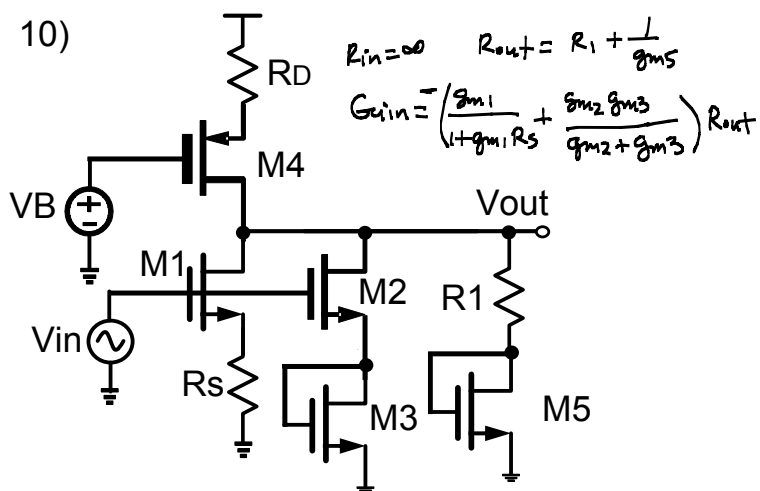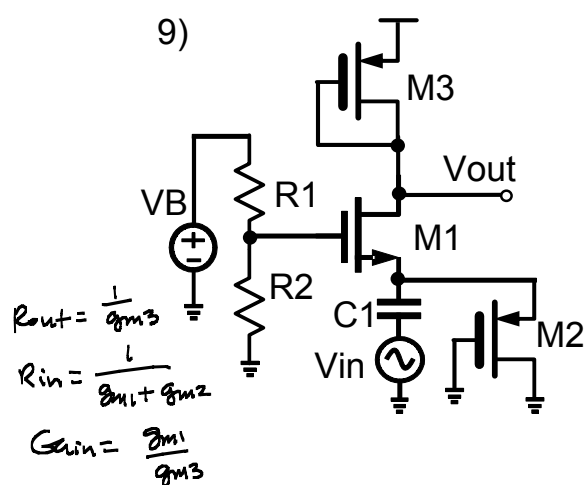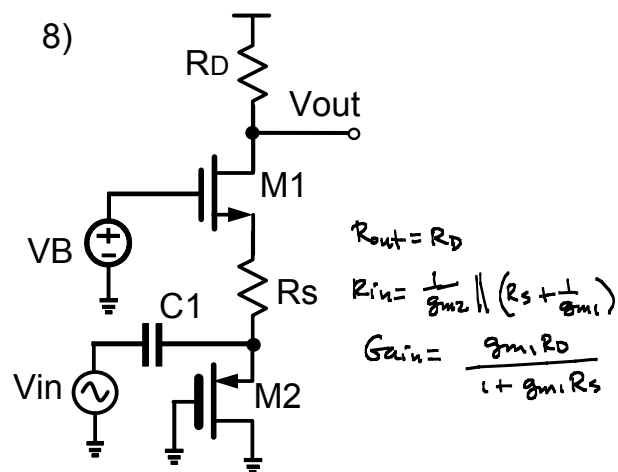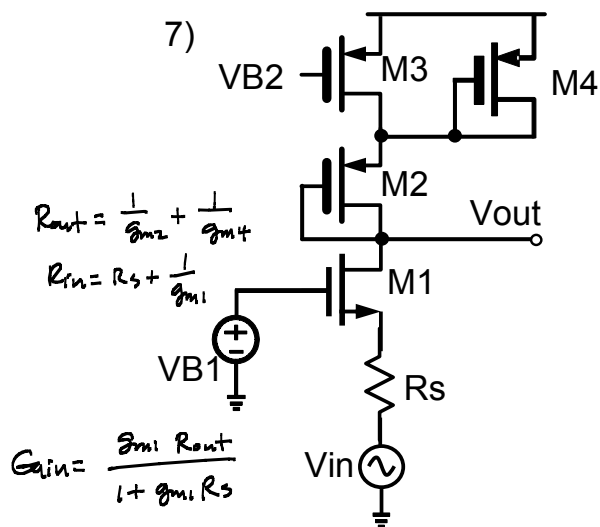
$$Gain = \frac{-g_{m1}}{1 + g_{m1} \frac{1}{g_{m2}}} R_{out}$$




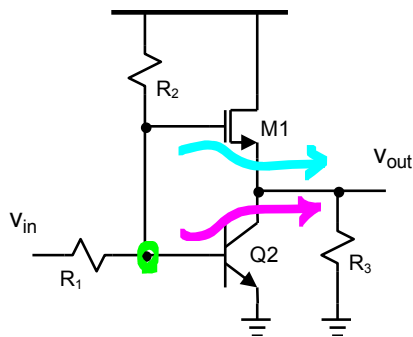13) Find the small-signal gain from V_{in} to V_{out} .



$$Gain = \frac{R_2 \parallel r_{\pi 2}}{R_1 + (R_2 \parallel r_{\pi 2})} \left(\frac{R_3}{\frac{1}{g_{m1}} + R_3} - g_{m2} [R_3 \parallel \frac{1}{g_{m1}}] \right)$$

14) Find the small-signal R_{eq1} .

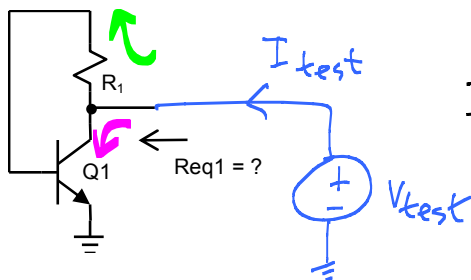

$$I_{test} = \frac{V_{test}}{R_1 + r_{\pi 1}} + V_{test} \frac{r_{\pi 1}}{R_1 + r_{\pi 1}} g_{m1}$$

$$R_{eq1} = \frac{V_{test}}{I_{test}} = (R_1 + r_{\pi 1}) \parallel \left(\frac{r_{\pi 1} g_{m1}}{R_1 + r_{\pi 1}} \right)^{-1} = \frac{R_1 + r_{\pi 1}}{1 + \beta_1}$$