
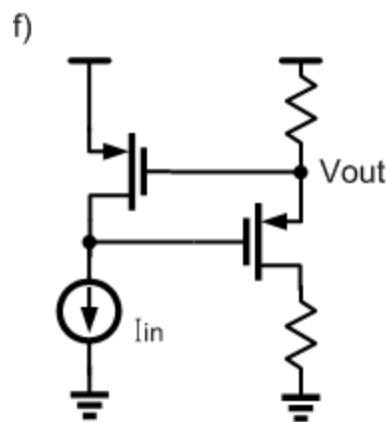
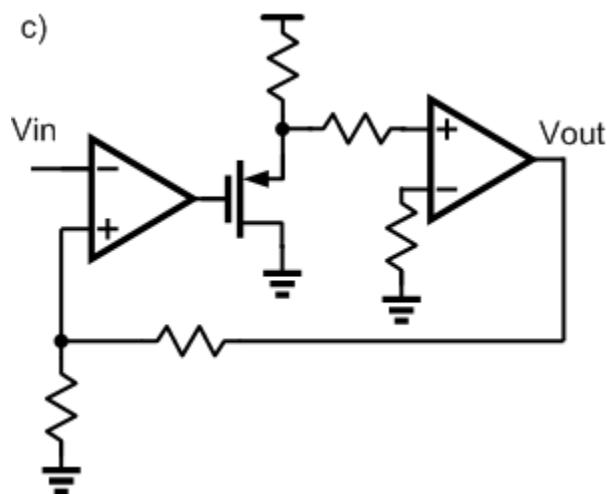
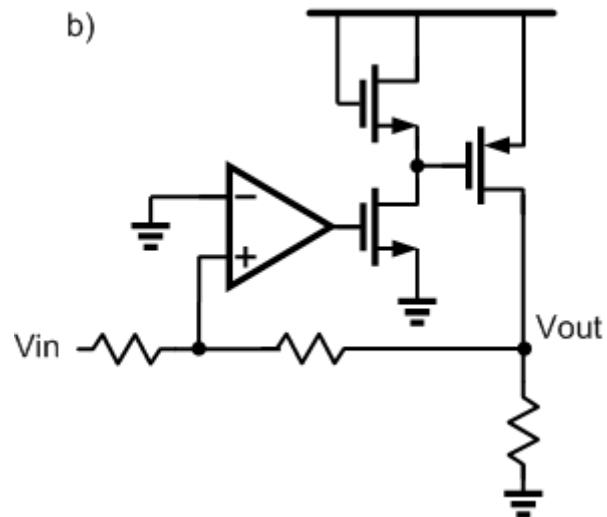



ECE323

Homework 5

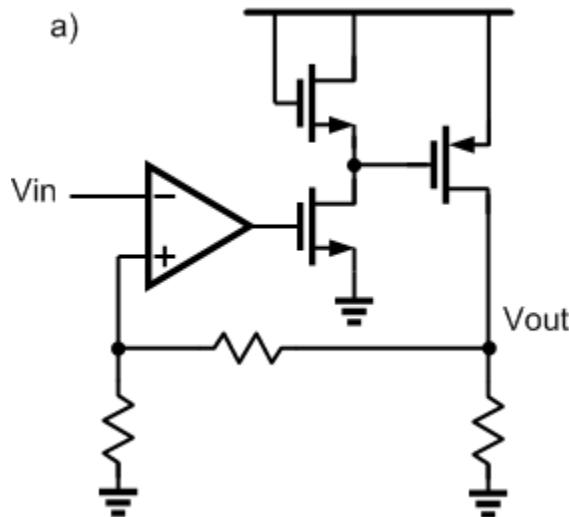1. Determine the polarity of the feedback circuits shown below.




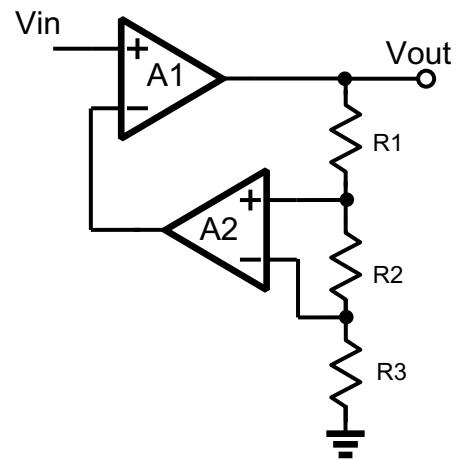2. Compute the closed loop gain of the circuit shown below. Assume opamps have finite gain of A_1 , A_2 , but are otherwise ideal.




3. In problem 2, assume opamp A1 has a transfer function $H_{OL}(s) = \frac{A1}{1+s/\omega_p}$, determine the closed loop -3dB bandwidth.

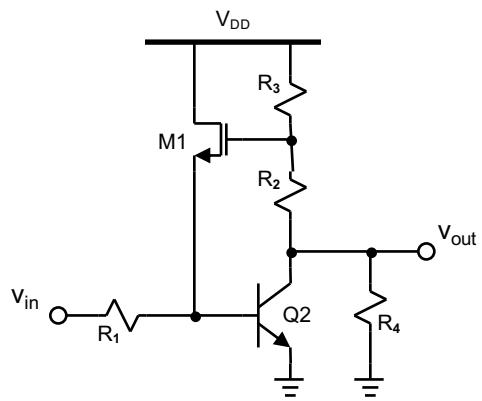4. Find the input-to-output small-signal gain.



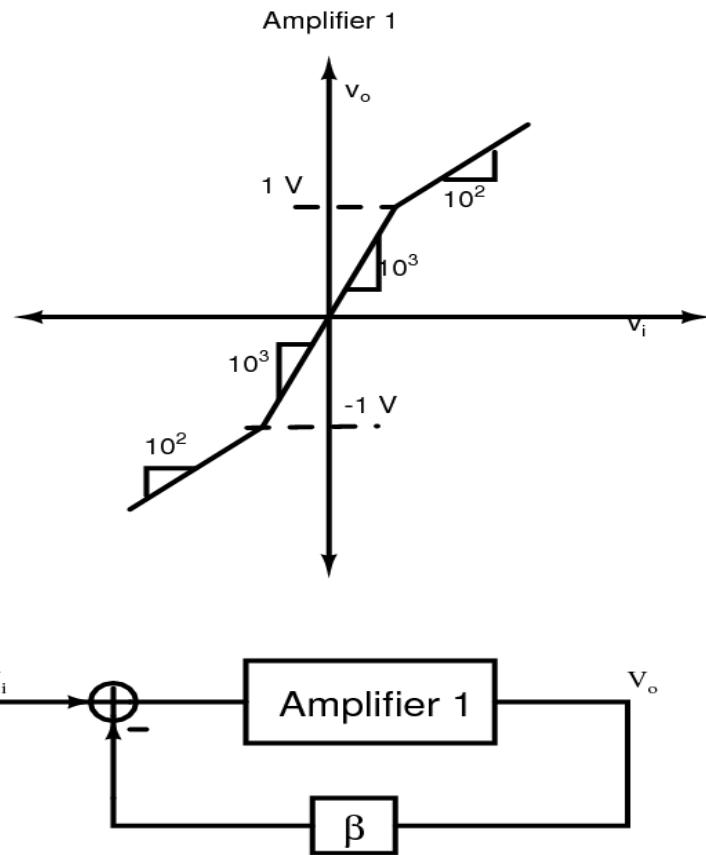5. A realistic amplifier can be modeled by the following non-linear transfer function. For this amplifier, the open-loop gain changes from 1000 to 100 for output voltage larger than 1 V. Find the feedback factor (β) to be used in the closed loop amplifier shown below such that, the closed loop gain varies only by 10%, when the output voltage is above and below 1V. What is the transfer characteristic of the resulting closed-loop feedback amplifier?



6. Find the input-to-output small-signal gain.

