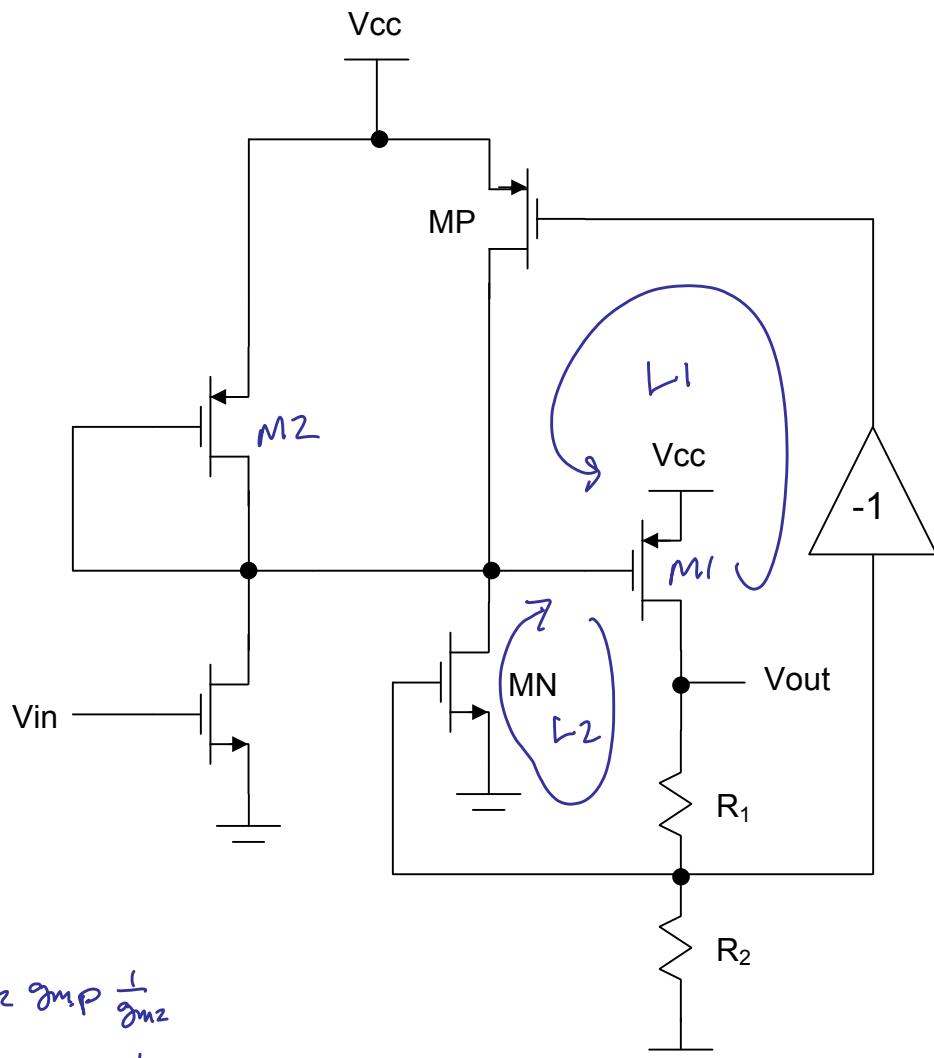


Prob-1. Determine in which of the two cases (a) $g_{mp} > g_{mn}$ (b) $g_{mp} < g_{mn}$ the circuit will be unstable and why? g_{mp} and g_{mn} are respective transconductances of MP and MN.



$$L_1 = -g_{m1} R_2 g_{mp} \frac{1}{g_{m2}}$$

$$L_2 = +g_{m1} R_2 g_{mn} \frac{1}{g_{m2}}$$

$(g_{mp} > g_{mn})$ yields net negative feedback loop \rightarrow STABLE

$(g_{mp} < g_{mn})$ yields net positive feedback loop \rightarrow UNSTABLE

(only if magnitude of)
loop gain > 1 .

Prob-2. A second order system has an open loop transfer function $H(s) = \frac{2000}{(\frac{s}{10} + 1)(\frac{s}{p} + 1)}$ and feedback factor of β .


Determine the location of pole p for which the loop phase margin is 45° if (a) $\beta=1/2$ and (b) $\beta=1/20$. Show the bode plot of loop transfer function for both the cases.

④ 45° phase margin implies 2nd pole is located at 0 dB loopgain.


$$L(s) = H(s) \cdot \beta$$

$$\left\{ \begin{array}{l} L(s) = \frac{1000}{(1 + \frac{s}{10})(1 + \frac{s}{p})} \\ \beta = \frac{1}{2} \end{array} \right. \rightarrow \text{want } p = 10^4 \text{ for } 45^\circ \text{ PM.}$$
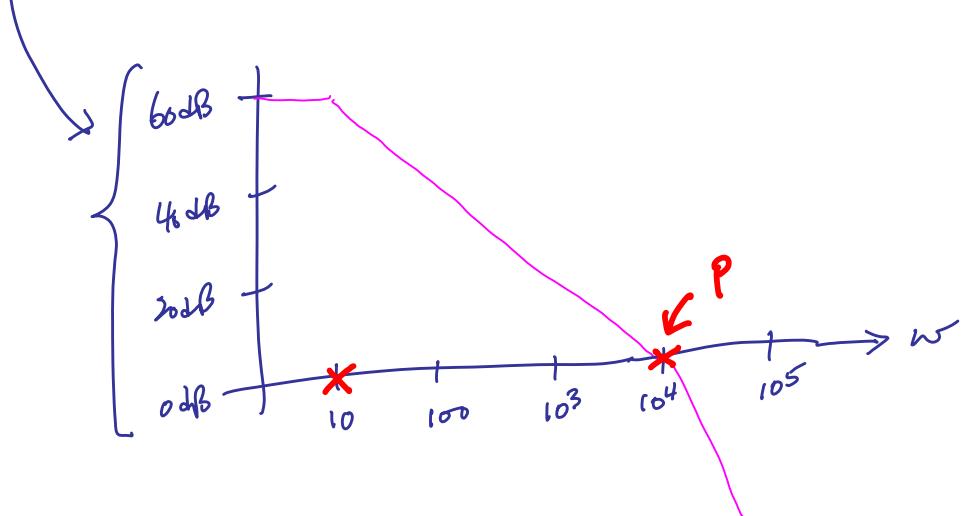
$$\left\{ \begin{array}{l} L(s) = \frac{100}{(1 + \frac{s}{10})(1 + \frac{s}{p})} \\ \beta = \frac{1}{20} \end{array} \right. \rightarrow \text{want } p = 10^3 \text{ for } 45^\circ \text{ PM}$$



Prob-3. Figure below shows a non-inverting amplifier achieved by connecting an opamp in negative feedback configuration. Assuming open loop gain of opamp $A=\infty$, the closed loop gain V_{out}/V_{in} of the circuit is given by $1+R_1/R_2$ which is simply $1/\beta$ where β is the feedback factor $R_2/(R_1+R_2)$. Find the expression for closed loop gain if A is finite and determine % error in the closed loop gain for (a) $A=1000$ and (b) $A=10000$.

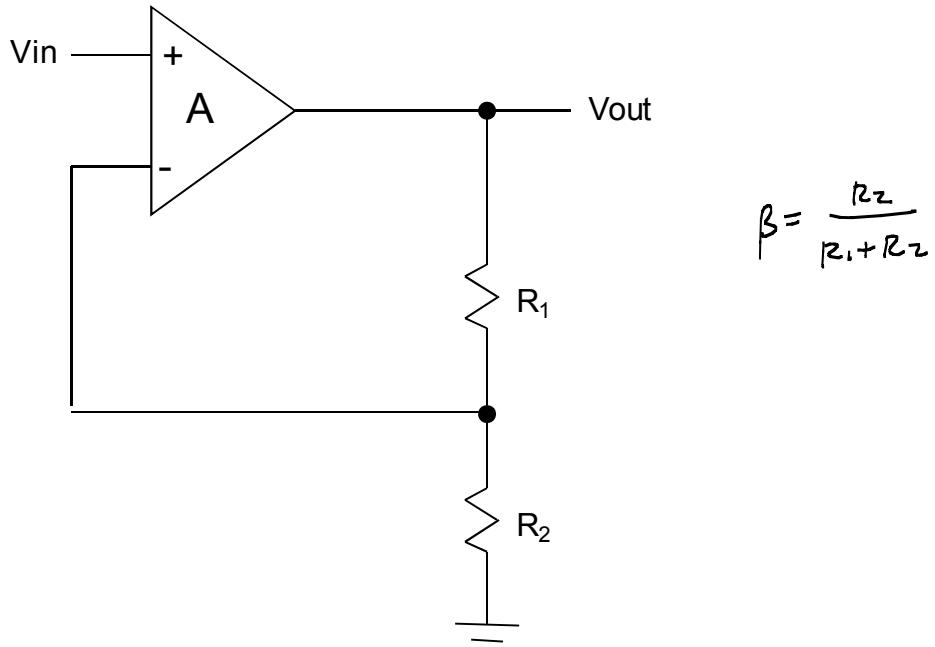


$$\text{Closed loop gain} = \frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta} = \underbrace{\frac{1}{\beta}}_{\substack{\text{ideal} \\ \text{gain}}} \frac{A\beta}{1 + A\beta}$$

$$\text{ideal gain} \sim \frac{R_1 + R_2}{R_2}$$

$$\text{Error} = 1 - \frac{A\beta}{1 + A\beta} = \frac{1}{1 + A\beta}$$

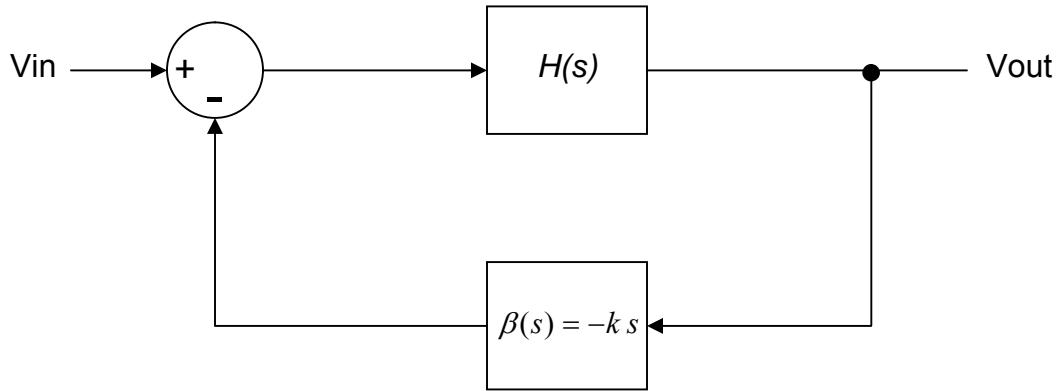Prob-4. A system is said to be unstable if any of the poles lie in right half of the s-plane. This property can be used to convert a second order system into oscillator by using negative feedback and choosing a proper feedback function. Find the closed loop transfer function $V_{out}(s)/V_{in}(s)$ of the system and show how the location of poles change w.r.t k in s-plane.



$$H(s) = \frac{A}{s^2 + \frac{w_n}{Q_0} s + w_n^2}$$

$$A(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{H(s)}{1 - (H(s) \cdot k s)} = \frac{A}{s^2 + s \left(\frac{w_n}{Q_0} - A k \right) + w_n^2}$$

"b" part of quadratic formula


$$s = \frac{-b}{2a} \pm \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}}$$

$(b=0) \rightarrow k = \frac{w_n}{Q_0 A} \rightarrow$ poles on jw-axis (all imaginary)

$(b > 0) \rightarrow k < \frac{w_n}{Q_0 A} \rightarrow$ STABLE (poles in left half plane)

$(b < 0) \rightarrow k > \frac{w_n}{Q_0 A} \rightarrow$ UNSTABLE

Prob-5. A common source amplifier with DC gain $gm_1 R$ and pole location $wp = 1/RC$ is connected in negative feedback configuration as shown in figure below. Determine the closed loop transfer function $V_{out}(s)/V_{in}(s)$, closed loop DC gain and closed loop $-3dB$ bandwidth of the circuit. Show the bode plot for gain and phase for (a) $\beta=0$ (b) $\beta=1$ and (c) $\beta=1/2$ and compare the DC gain and Bandwidth of the closed system with that of open loop gain and bandwidth of common source amplifier. Consider $ro=\infty$.

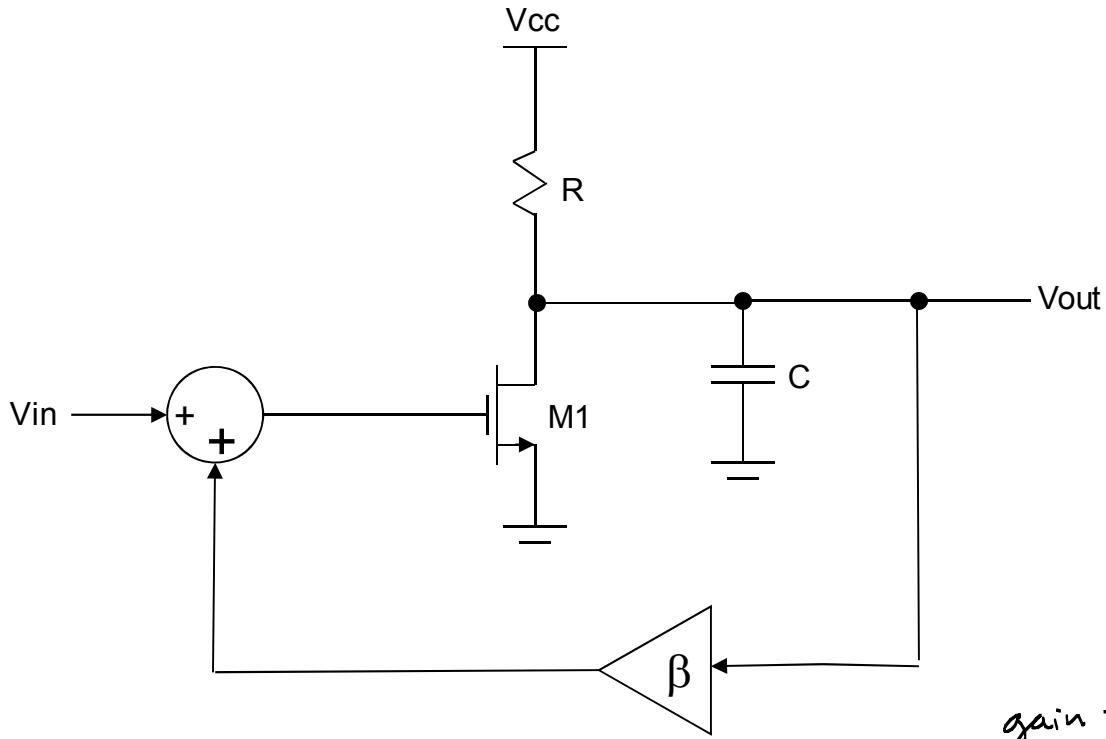

$$A(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-gm_1 R \frac{1}{1+SRC}}{1 + gm_1 R \frac{1}{1+SRC} \cdot \beta} = \frac{\left(\frac{-gm_1 R}{1 + gm_1 R \beta} \right)}{1 + \frac{SRC}{(1 + gm_1 R \beta)}}$$

$$BW = \frac{1}{RC} (1 + gm_1 R \beta)$$

When $\beta=0$, $A(s)$ is same as open loop.


$$gain = -gm_1 R$$

$$BW = \frac{1}{RC} = pole$$

For $\beta = \frac{1}{2}$, $\beta = 1$,

$A(s)$ sees decrease in gain and increase in BW, by $(1 + gm_1 R \beta)$.

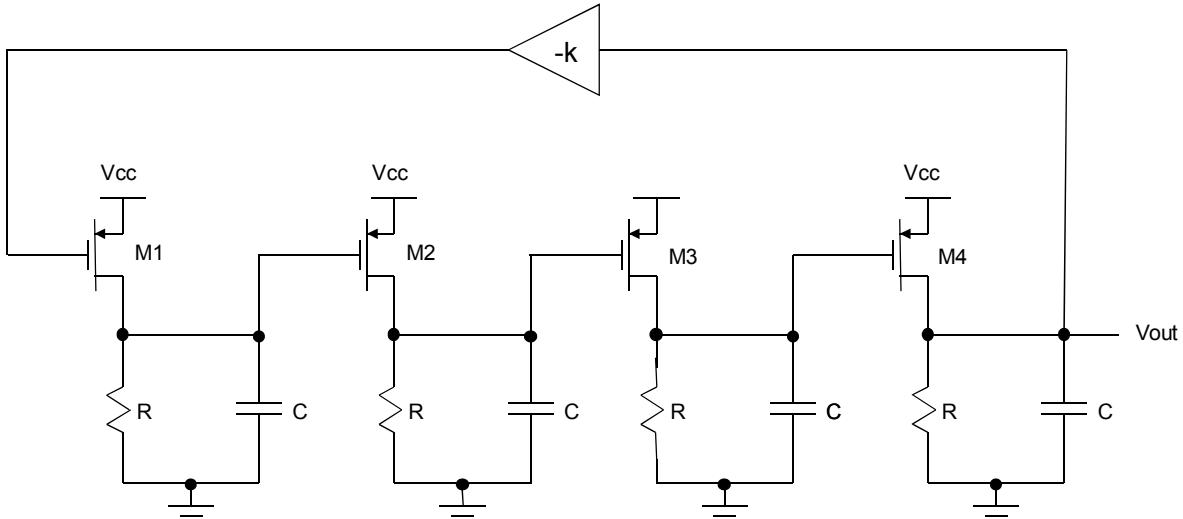Prob-6 For the circuit shown below, find (a) minimum gain k if $R=1K\Omega$ and (b) minimum value of R if $k=0.25$ for which the circuit will oscillate and determine the expression for frequency of oscillation in both the cases. Consider $ro=\infty$ and $gm=1m A/V$ for all the PMOS.



Each stage to contribute 45° phase delay \rightarrow results in positive FB loop.

45° is at pole frequency, where gain is reduced by $\sqrt{2}$ (3dB).

$$\text{Loop gain at that frequency} = \frac{k (gm_1 R)^4}{(\sqrt{2})^4}$$


$$\frac{1}{kC}$$

$$(R=1k\Omega) \rightarrow \text{want loop gain } k \left(\frac{gm_1 R}{\sqrt{2}} \right)^4 > 1 \rightarrow k > \left(\frac{\sqrt{2}}{gm_1 R} \right)^4 = 4$$

$$(k=0.25) \rightarrow k \left(\frac{gm_1 R}{\sqrt{2}} \right)^4 > 1 \rightarrow R > \left(\frac{\sqrt{2}}{gm_1} \right) \cdot k^{-1/4} = 2k\Omega$$

ECE 323 HW # 6


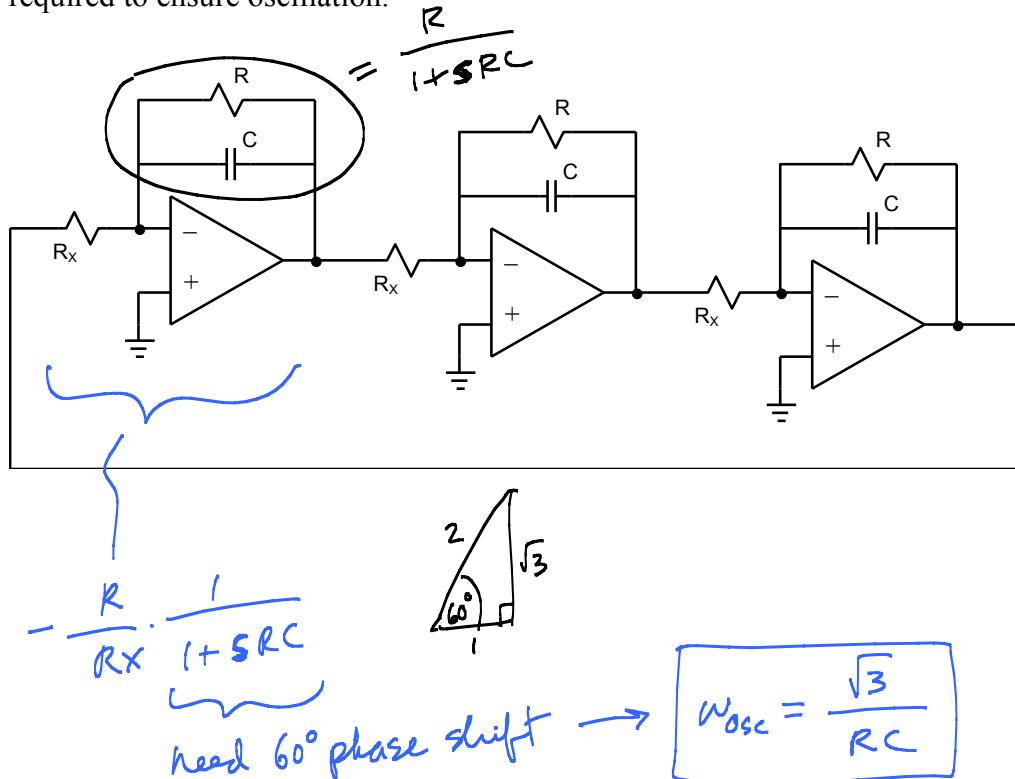
Prob-7. For the linear oscillator shown, find the oscillation frequency ω_0 and R_x value required to ensure oscillation.



$$\left| \text{Loop gain} (s = j\omega_{\text{osc}}) \right| = \left(\frac{R}{R_x} \frac{1}{2} \right)^3 \geq 1 \quad \text{to ensure oscillation}$$

$$\rightarrow R_x \leq \frac{1}{2} R$$

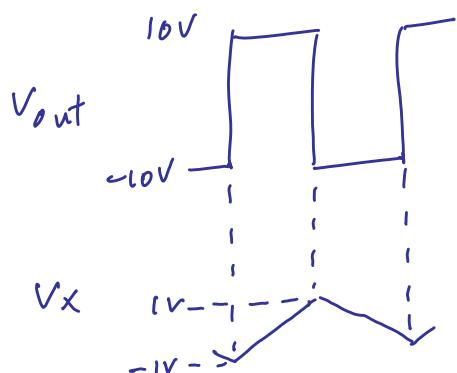
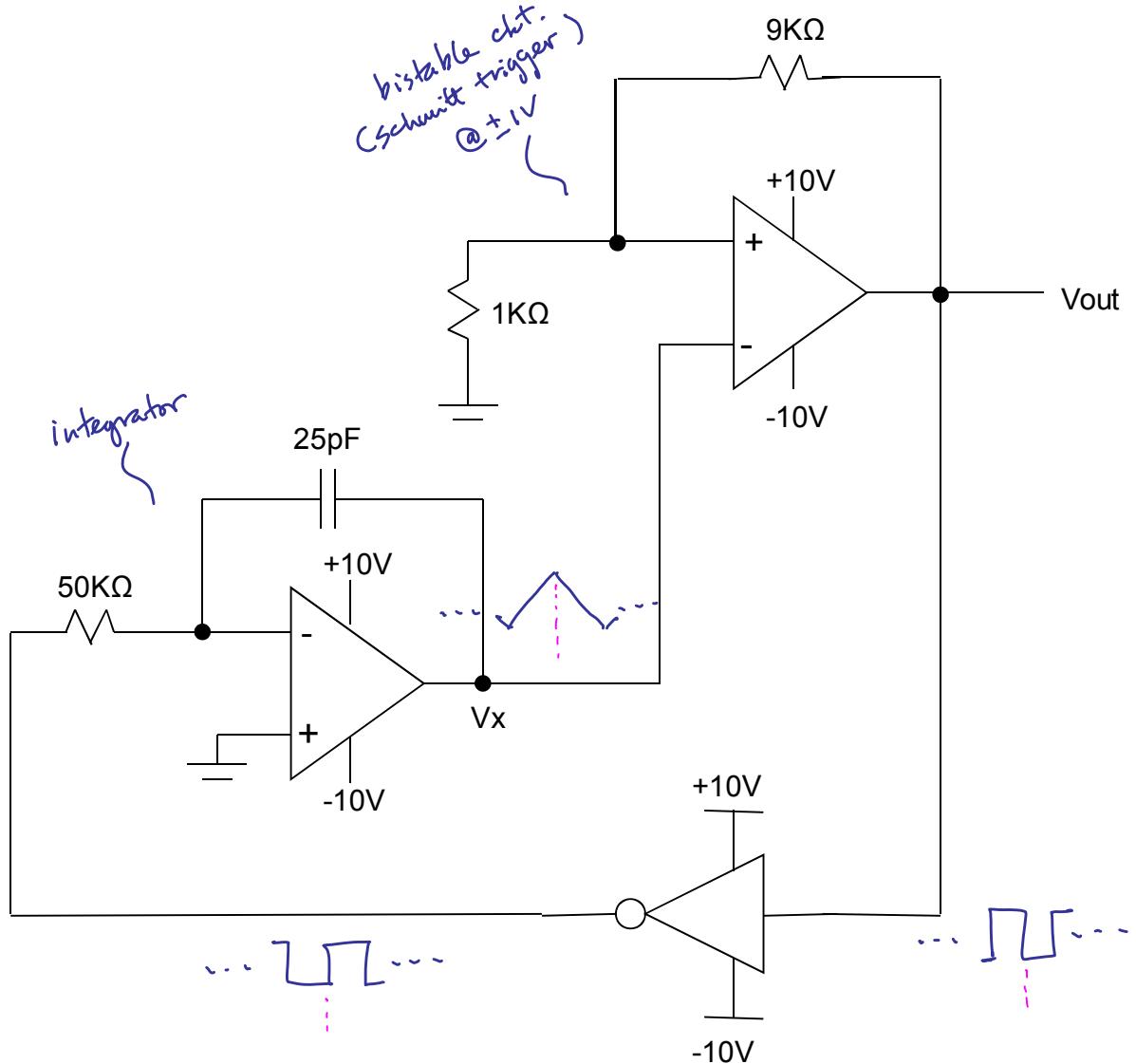
Prob-8. Plot the waveforms at V_{out} and V_x . Mark the voltages clearly and determine the frequency of oscillation.



$$I = C \frac{dV}{dt} \rightarrow \text{slope} = \frac{\Delta V}{\Delta t} = \frac{I}{C} = \frac{10}{RC} = \frac{10}{(50k\Omega)(25pF)}$$

$$T = \left(\frac{2}{\text{slope}} \right) \cdot 2 = 0.5 \text{ nsec} \rightarrow f_{osc} = 2 \text{ MHz}$$

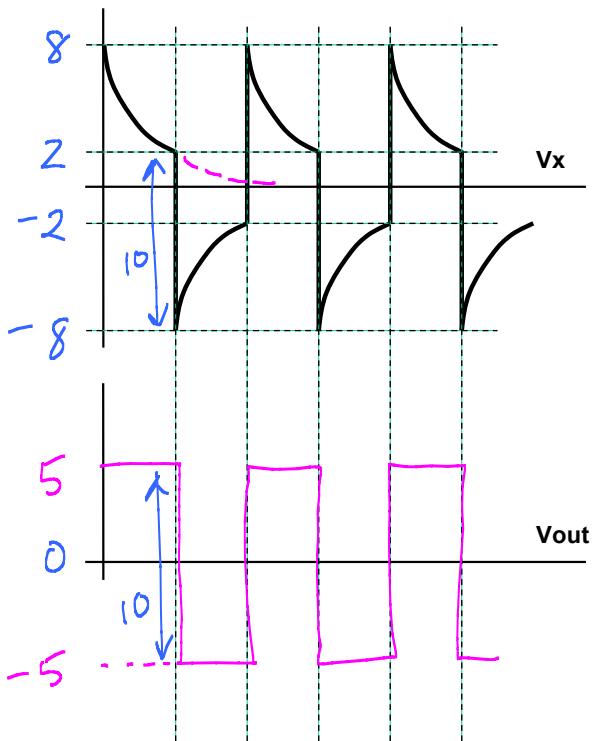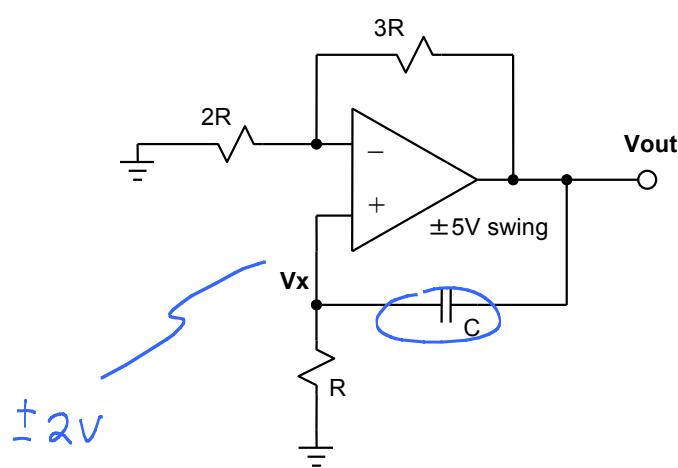Prob-9. Note all critical voltage levels in the V_x waveform. Sketch V_{out} waveform, with proper time alignment and voltages. Find the resulting period (T_{osc}) of oscillation.



$$\frac{2}{8} = e^{-\frac{t_1}{RC}} \rightarrow t_1 = RC \ln(4)$$

$$T_{osc} = 2t_1$$