
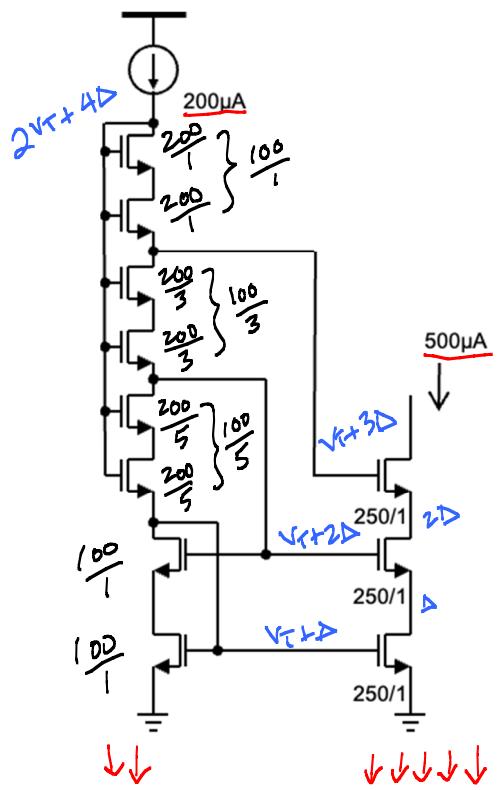


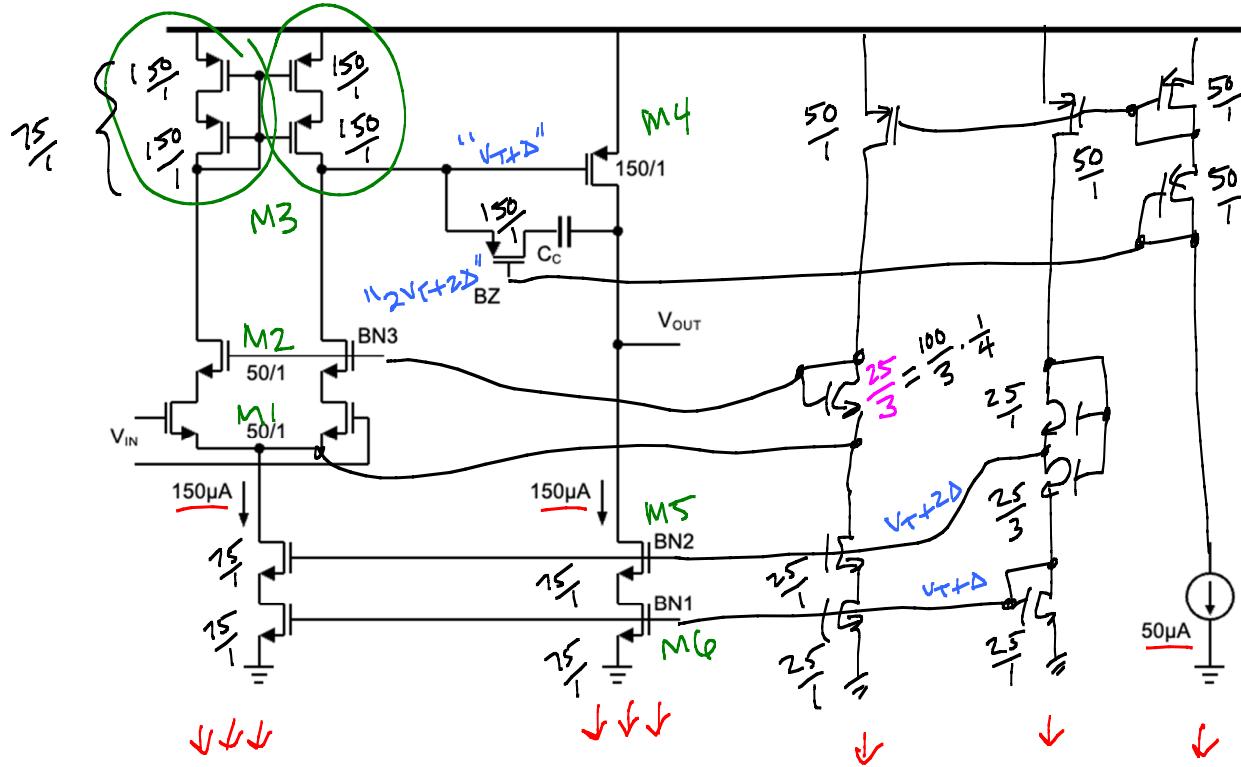1. [10 pts total] Optimally bias the current source by specifying all transistor sizes where W/L is not given.




2. [10 pts total] Design the optimum bias for BN1, BN2, BN3, BZ (for no/minimal systematic offset and RHP zero cancellation). Specify all transistor sizes where W/L is not given. Find the small-signal gain expression (label transistors as needed and treat composite as one transistor).




$$\text{gain} \approx g_{m1} (r_{o2} g_{m2} r_{o1} \parallel r_{o3}) g_{m4} (r_{o4} \parallel r_{o5} g_{m5} r_{o6})$$

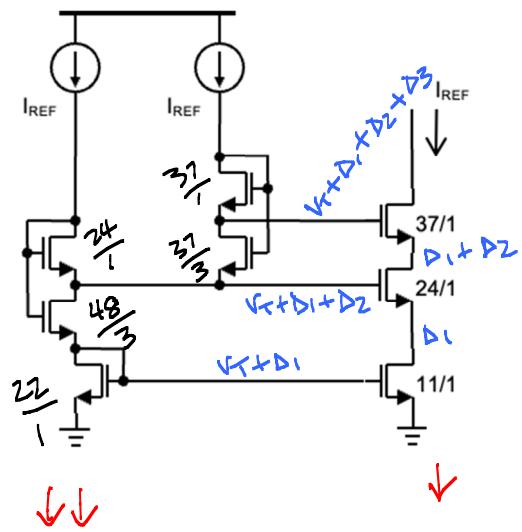3. [10 pts total] Optimally bias the current source by specifying all transistor sizes where W/L is not given.



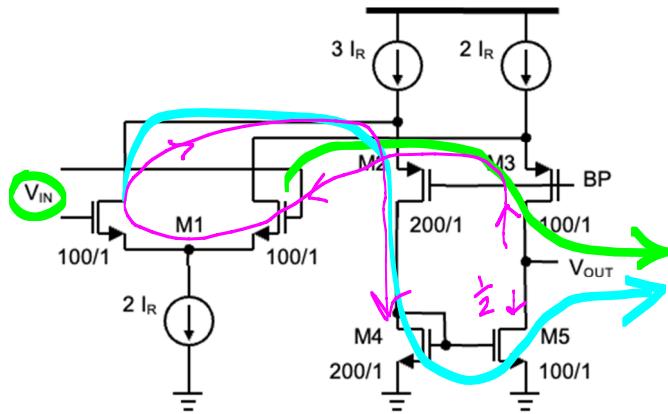4. [10 pts total] Find the Norton-equivalent small-signal G_m and R_{out} .



$$G_m \approx \frac{1}{2} g_{m1} + \frac{1}{2} g_{m1} \cdot \frac{1}{2} = \frac{3}{4} g_{m1}$$

$$R_{out} \approx r_{os} \parallel \frac{r_{o3} g_{m3} (2 r_{o1})}{1 + \frac{1}{2}}$$