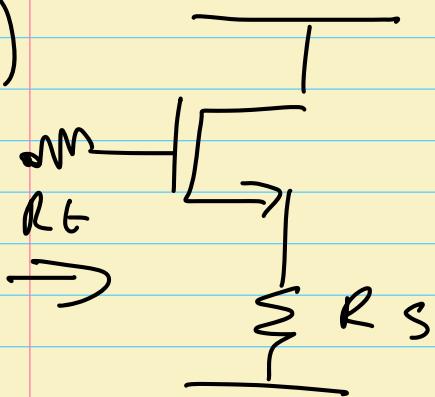


HW 2 .



1) a)



$$R_{in} = \infty$$

Reason: gate is open ckt.

b)

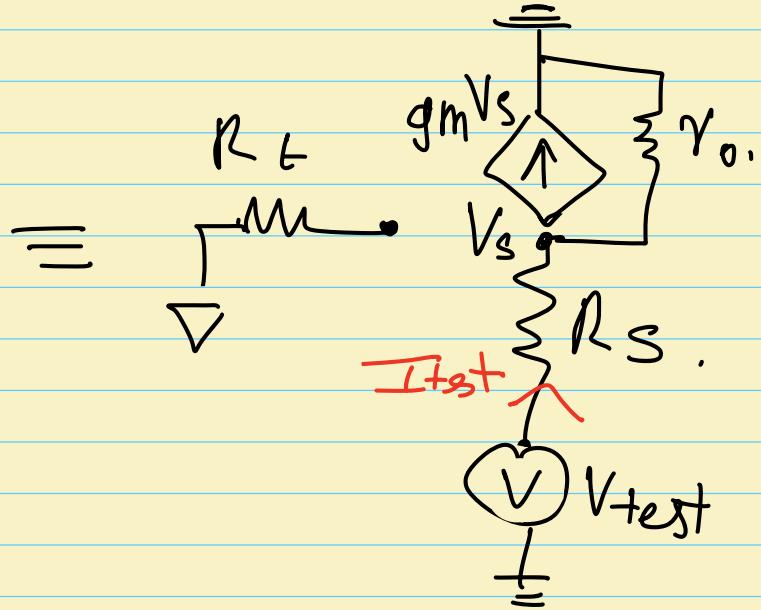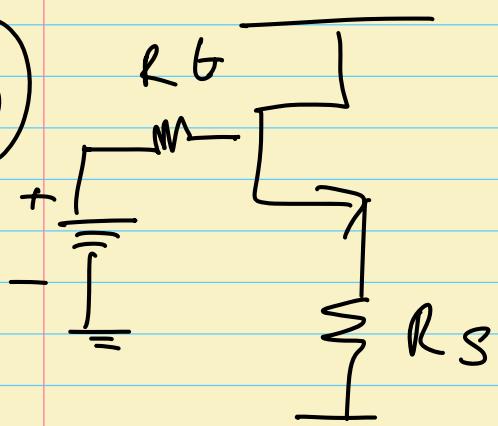

$$I_{test} = V_{test} - V_s = \frac{gmV_s + \frac{V_s}{\gamma_0}}{R_s}$$

$$V_{test} - V_s = gmV_s R_s + \frac{V_s R_s}{\gamma_0}$$

$$V_{test} = V_s \left[1 + gmR_s + \frac{R_s}{\gamma_0} \right]$$

$$I_{test} = V_{test} - \frac{V_{test}}{\left[1 + gmR_s + \frac{R_s}{\gamma_0} \right]}$$




R_S .

$$I_{test.} = \frac{V_{test} [g_m R_S + R_S / r_o]}{R_S [1 + g_m R_S + R_S / r_o]}$$

$$\therefore R_{eq} = R_S [1 + g_m R_S + R_S / r_o]$$
$$= R_S + \frac{R_S}{g_m R_S + R_S / r_o}$$


$$R_{eq} = R_S + \frac{r_o}{1 + g_m r_o}$$

c)

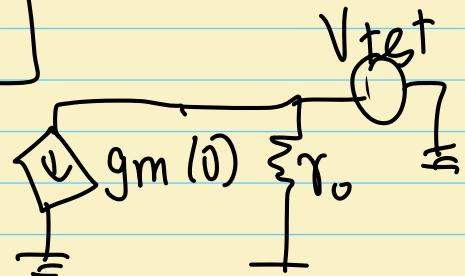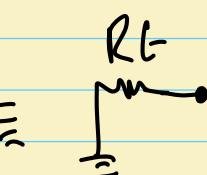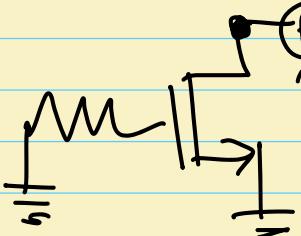

$$r_{eq} = r_o$$

d)

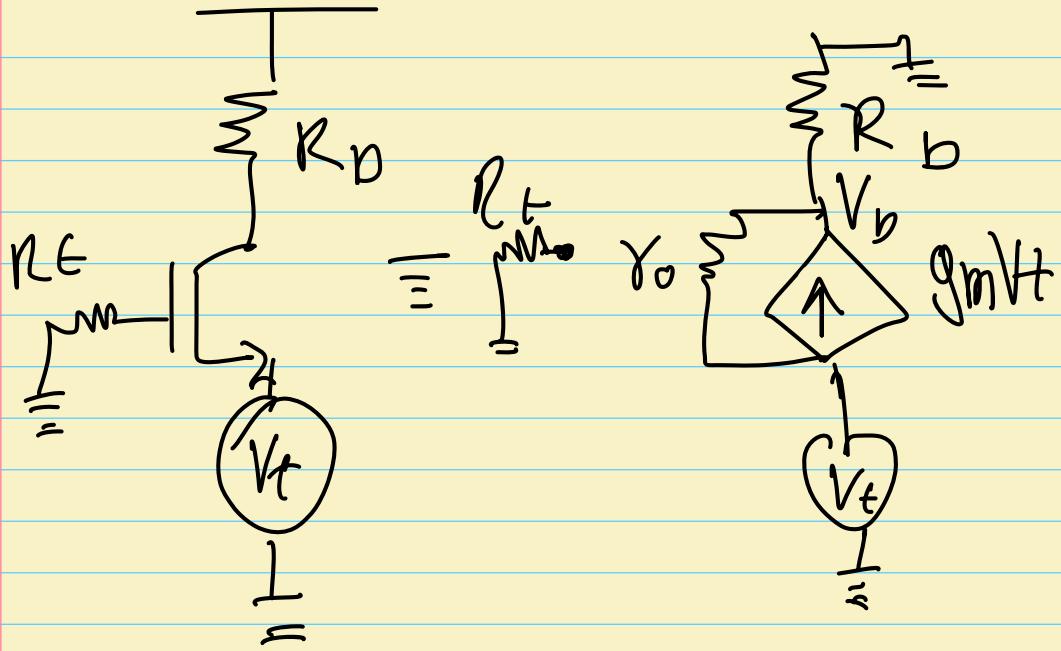

$$I_f = \frac{V_b}{R_D} = \frac{V_t - V_D}{r_o} + g_m V_t,$$

$$\therefore \frac{r_o V_D}{R_D} = V_t - V_D + g_m r_o V_t$$

$$\therefore V_D \left[1 + \frac{r_o}{R_D} \right] = V_t \left[1 + g_m r_o \right]$$


$$\therefore V_D = V_t \left[1 + g_m r_o \right] \frac{1}{\left[1 + \frac{r_o}{R_D} \right]}$$

$$\therefore I_f = V_t \left[1 + g_m r_o \right] \frac{1}{R_D \left[1 + \frac{r_o}{R_D} \right]}$$

$$\therefore I_T = \frac{V_T [1 + g_m r_o]}{R_D + r_o}$$

$$\therefore R_{eq} = \frac{R_D + r_o}{1 + g_m r_o}$$

c)

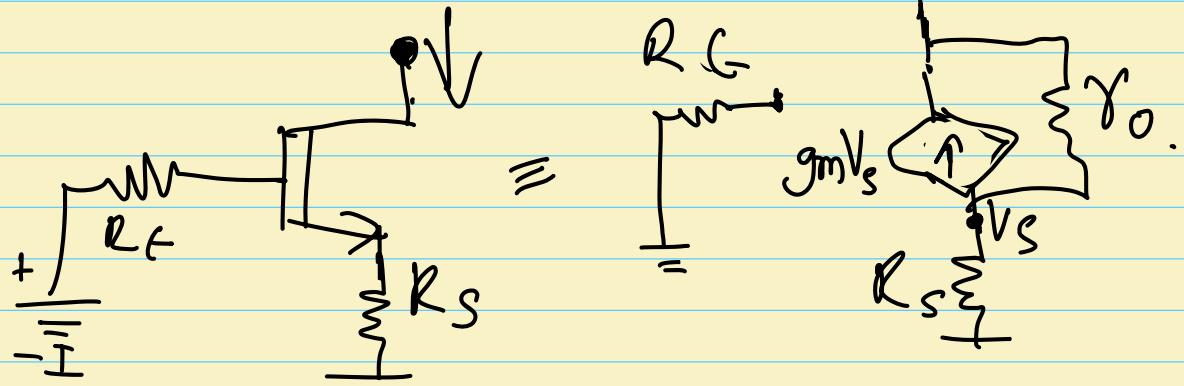

$$\therefore I_T = \frac{V_S}{R_S} = -g_m V_S + \frac{V_T - V_S}{r_o}$$

$$\therefore \frac{V_S r_o}{R_S} = -g_m r_o V_S + V_T - V_S$$

$$\therefore V_T = V_S \left[\frac{r_o}{R_S} + g_m r_o + 1 \right]$$

$$\frac{V_T}{R_S \left[\frac{r_o}{R_S} + g_m r_o + 1 \right]} = I_T$$

$$\frac{V_f}{\gamma_0 + g_m \gamma_0 R_s + R_s} = T_f$$


$$R_{eq} = R_s + \gamma_0 + g_m \gamma_0 R_s$$

2. a)

$$R_{eq} = R_s + \gamma_{o1} + g_m \gamma_{o1} R_s$$

$$R_{eq} = R_{s_{eq}} + \gamma_{o2} + g_m \gamma_{o2} R_{s_{eq}}$$

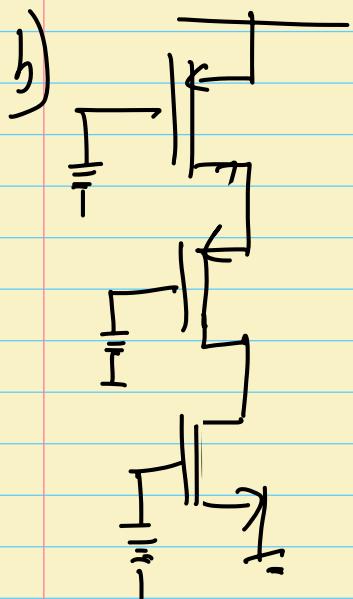
$$R_{eq} = R_s + \gamma_{o1} + g_m \gamma_{o1} R_s + \gamma_{o2} + g_m \gamma_{o2} R_s + g_m \gamma_{o2} \gamma_{o1} + g_m \gamma_{o2} g_m \gamma_{o1} R_s$$



$$R_{D_{eq}} = \gamma_{0_3} + \gamma_{0_2} + g m_2 \gamma_{0_2} \gamma_{0_3}$$

$$R_{eq} = \frac{R_{D_{eq}} + \gamma_{0_1}}{1 + g m_1 \gamma_{0_1}}$$
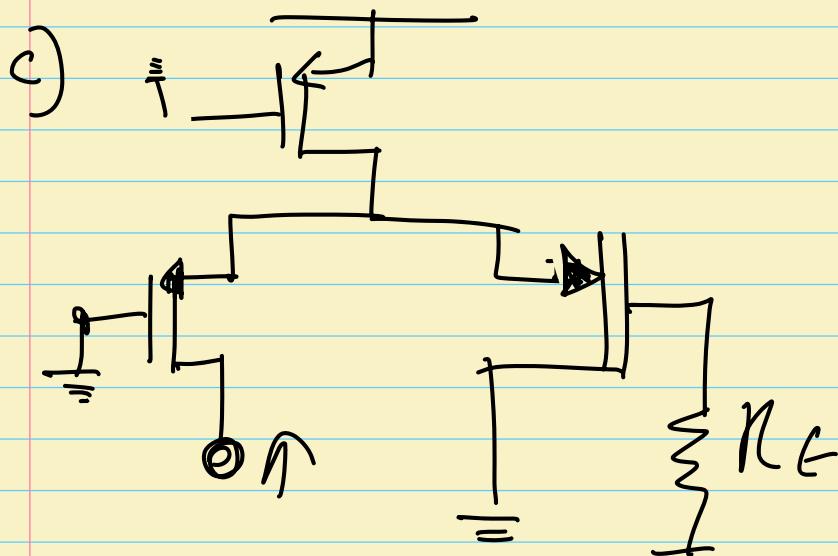
$$R_{eq.} = \frac{\gamma_{0_3} + \gamma_{0_2} + g m_2 \gamma_{0_2} \gamma_{0_3} + \gamma_{0_1}}{1 + g m_1 \gamma_{0_1}}$$



$$= \frac{\gamma_{0_2} + g m_3 \parallel \gamma_{0_3}}{\gamma_{0_1}}$$


$$= \frac{\gamma_{0_1}}{\gamma_{0_1} + \gamma_{0_2} + g m_3 \parallel \gamma_{0_3}}$$

$$R_{eq} = \gamma_{01} + \gamma_{02} \left| \left| \frac{1}{gm_3} \right| \right| \gamma_{03} \\ + gm_1 \cdot \gamma_{01} \cdot \left(\gamma_{02} \left| \left| \frac{1}{gm_3} \right| \right| \gamma_{03} \right)$$

Q3.


Transistor bias voltages:

Diff pair:

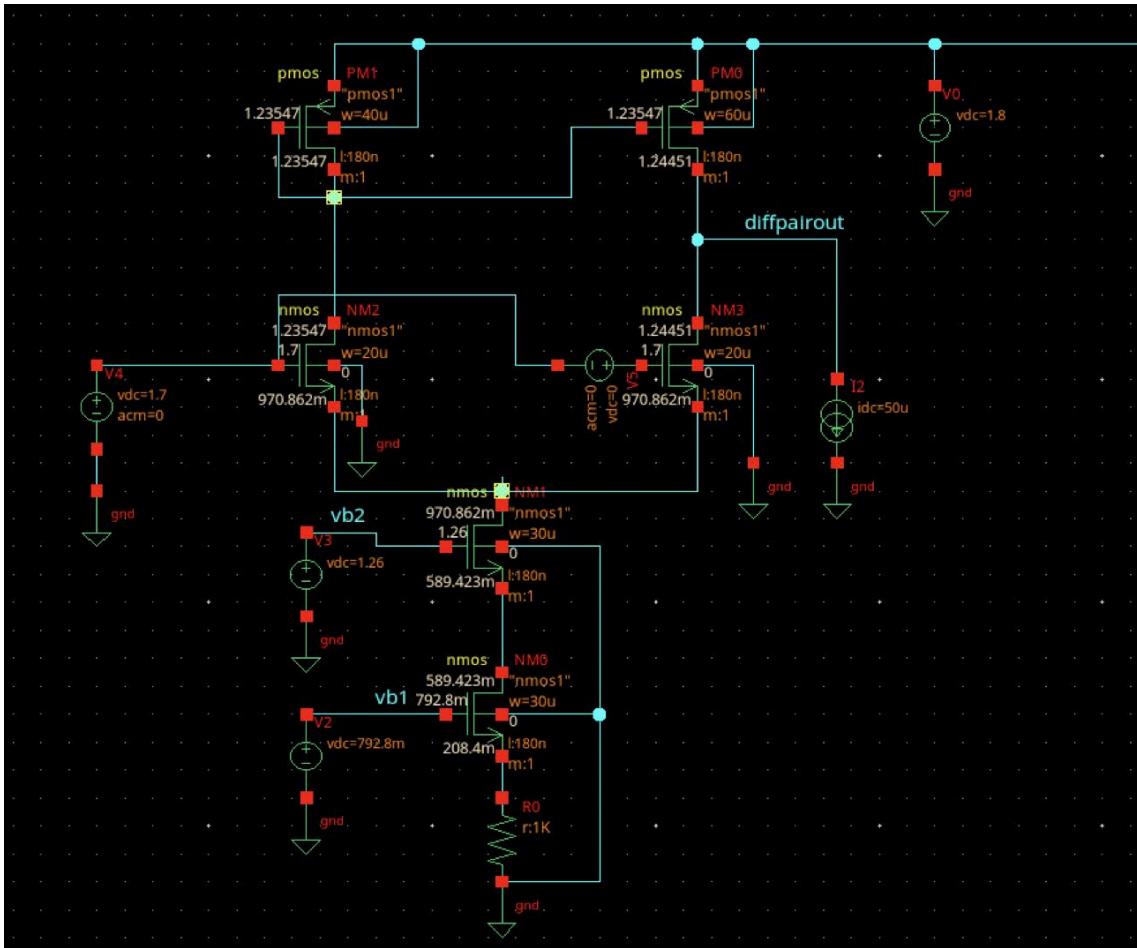


The gates of NM2 and NM3 are biased at 1.7V. Voltage source V5 is set to 0 V.

Cascode :

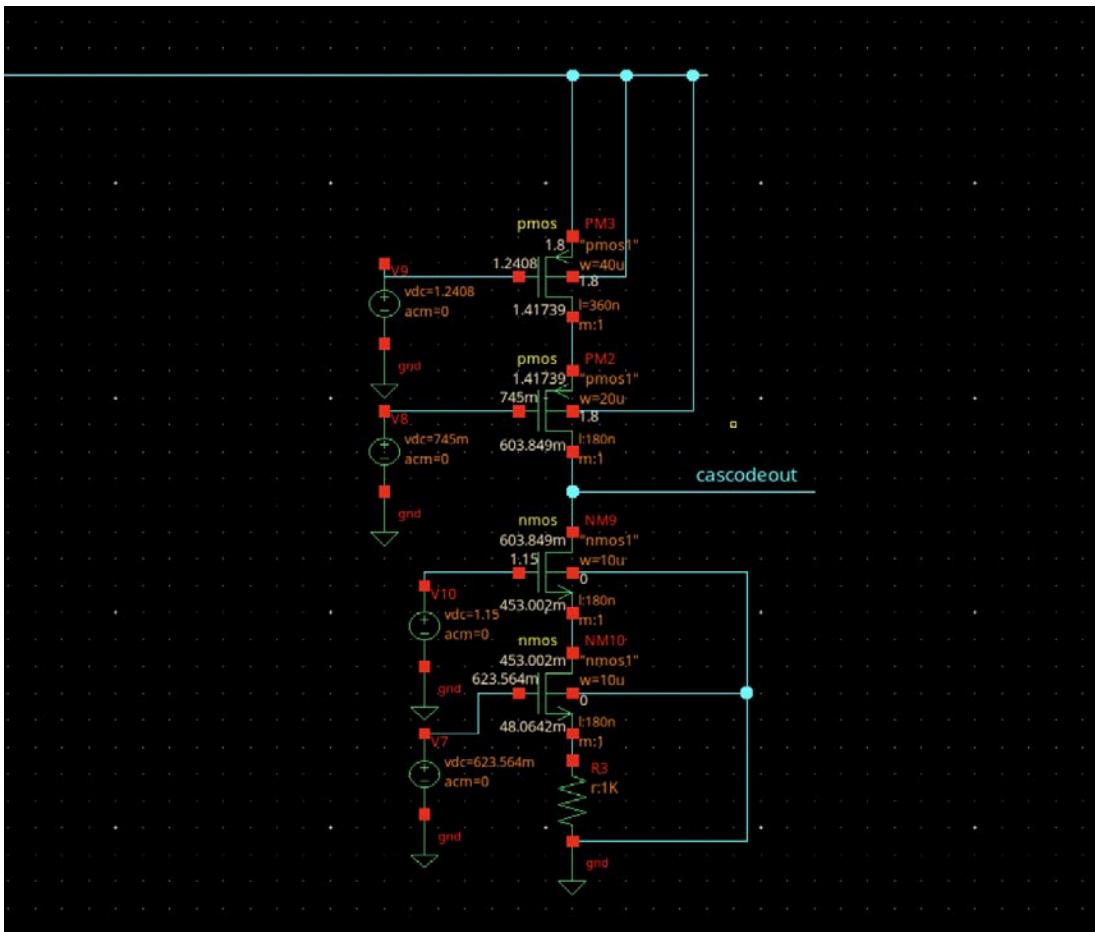


Regions of operation and DC operating points:


Diff pair:

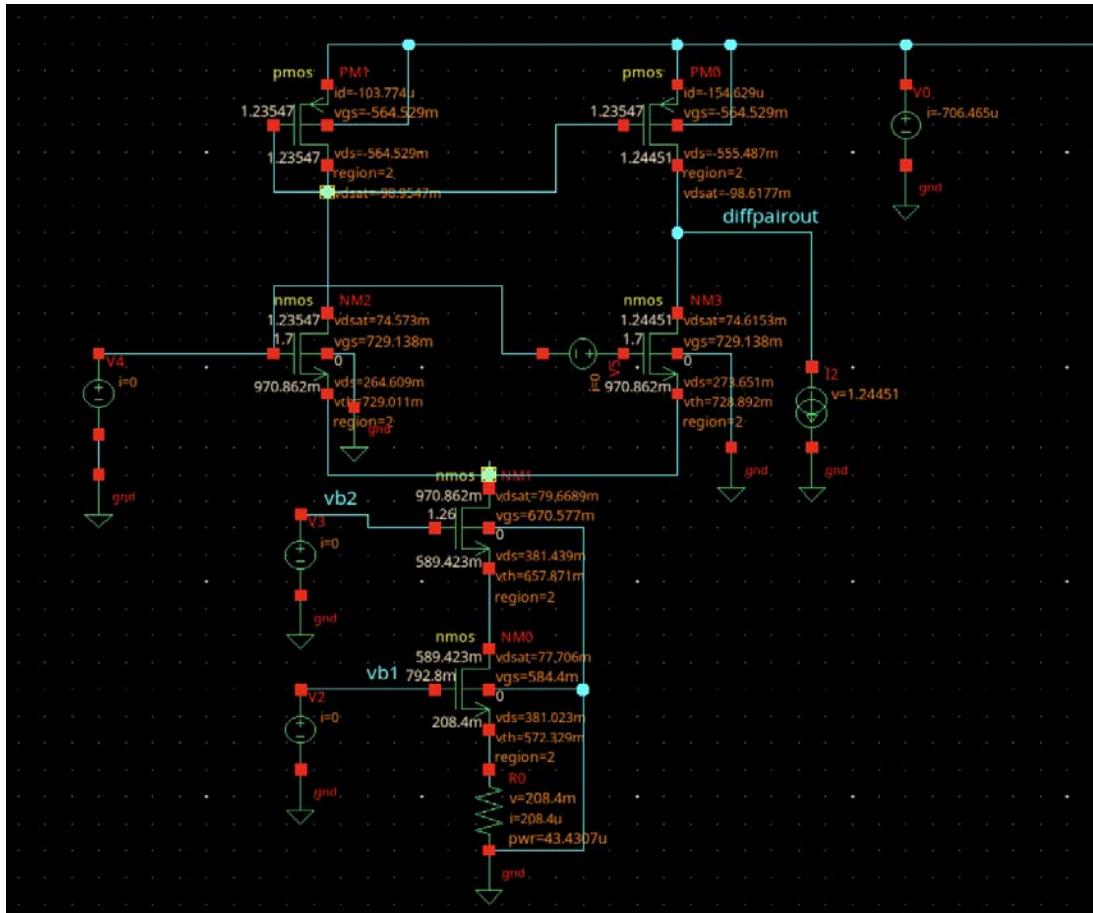


Cascode DC operating points:

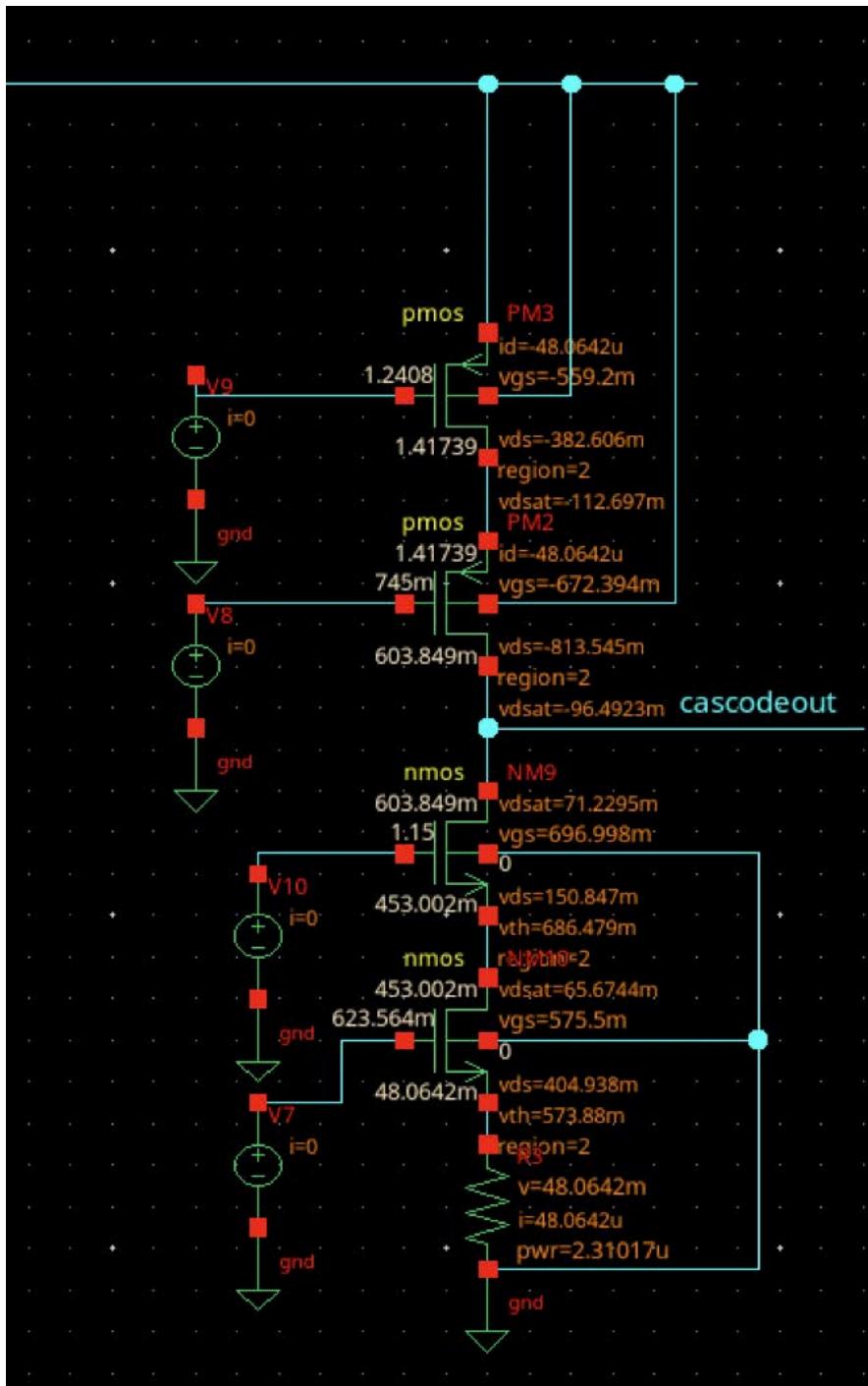

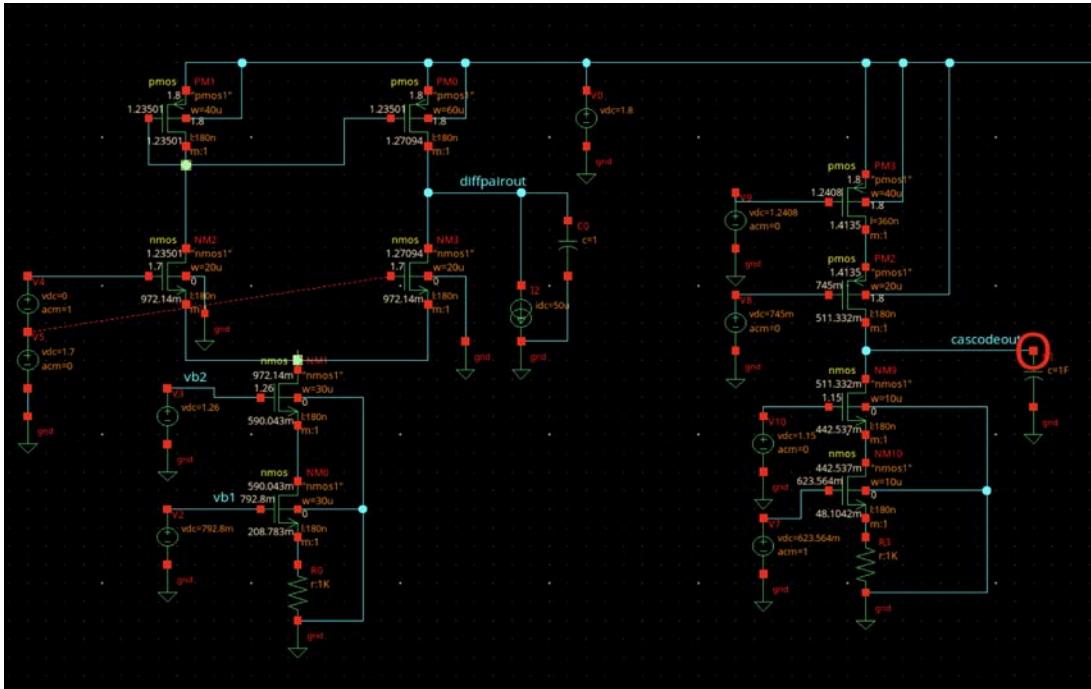
Gm calculation: I put a large capacitor at the output node, gave an AC input of 1 volt to the input transistor and measured the output current going into the large capacitor.




Diffpair measured Gm = 2.18521mS

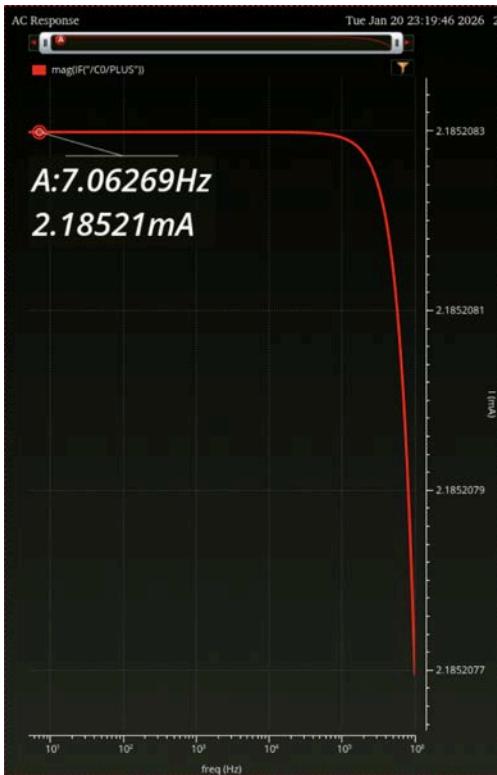


Cascode measured Gm = 392.832 uS

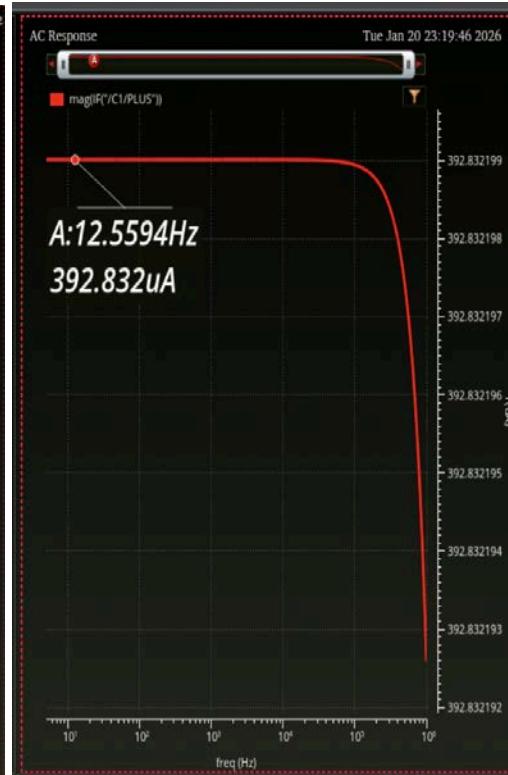

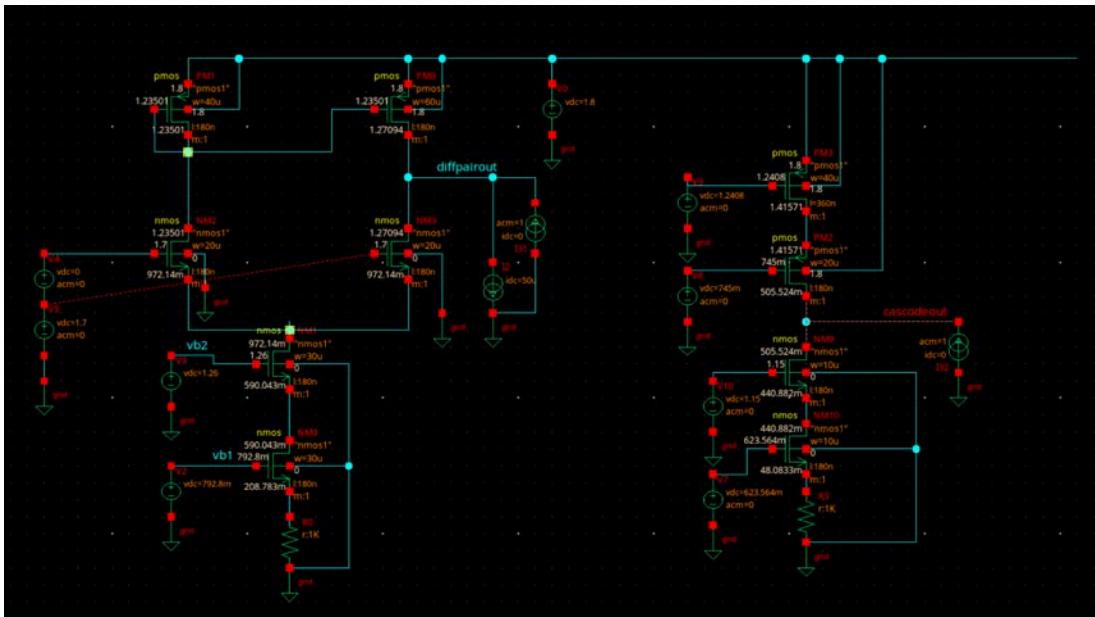
Rout calculation: I put an AC current source of 1 A at the output, shorted the AC inputs to gnd, then measured the voltage developed at the output node.



Diff pair Rout: 5.93492 Kilo Ohms

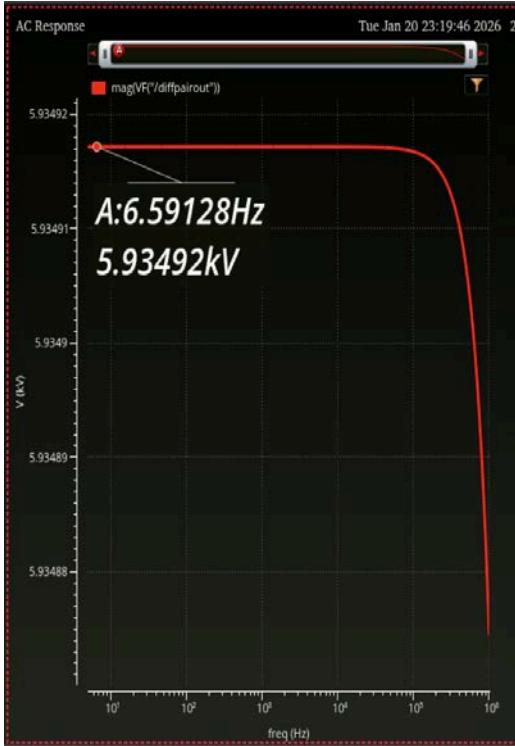


Cascode Rout: 1.09711 Mega Ohms

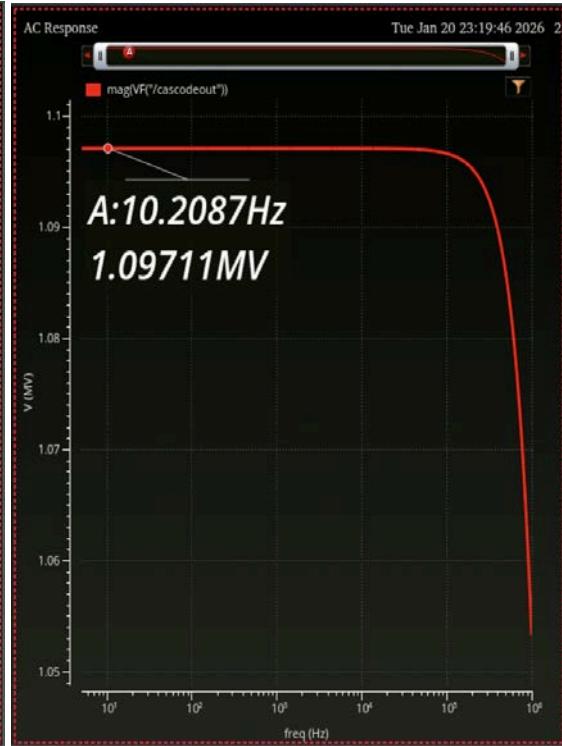

Diffpair Gm*Rout gain = $2.18521 \text{ mS} * 5.93492 \text{ kohm} = 12.96904653$
Cascode Gm*Rout gain = $392.832 \text{ uS} * 1.09711 \text{ Mega Ohms} = 430.9799155$

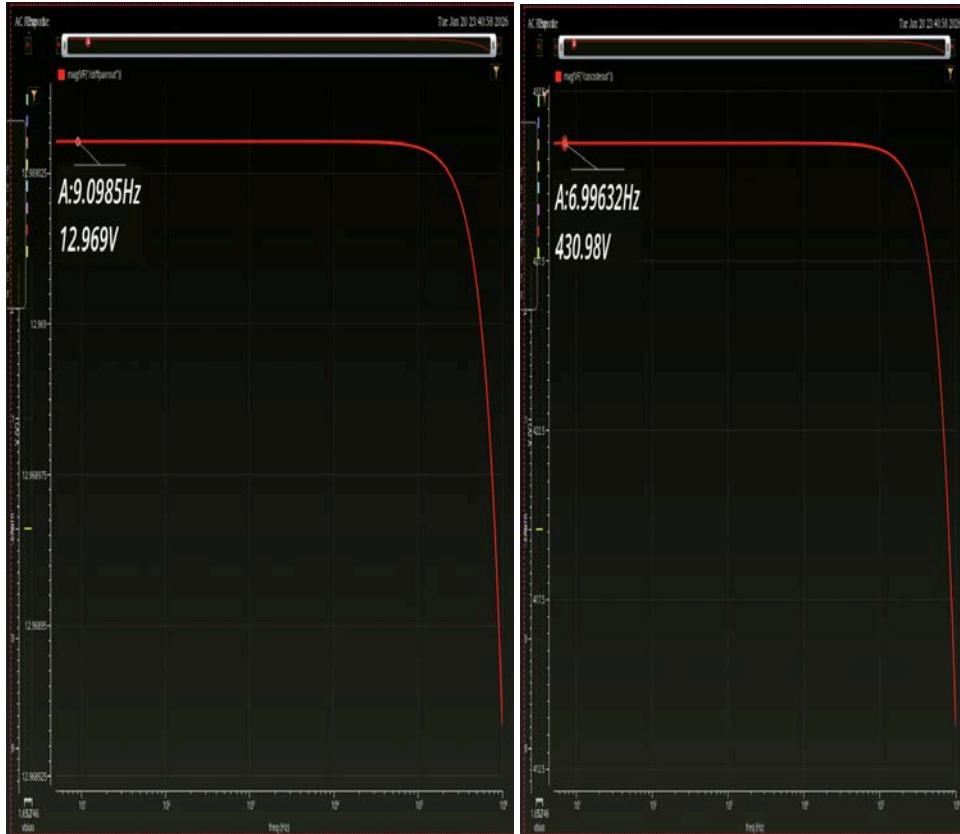Measured gain through regular AC gain simulation:



Diff pair gain: 12.969 V/V

Cascode gain = 430.98 V/V

The gains from both methods match