

Once again let me point out that W/L dimensions should be separated and clearly annotated in the schematic itself. I'm commenting w.r.t. final project writeup. One should really separately draw the schematic with W/L dimensions (even clearly hand drawn is fine). If you do not separately draw up the schematic, you should at least figure out a way to invert the schematic so there is no black background (and eliminate the miscellaneous annotations that might be useful for simulation but not useful for reviewing the writeup).

ECE 423 HW 4

 


Figure 1: Folded Cascode Circuit

	Specifications	27°C	100°C	-40°C
DC Gain	> 50 dB	51.89 dB	51.19 dB	52.45 dB
Unity-Gain BW	> 200 MHz	341 MHz	252 MHz	503.187 MHz
Phase Margin	> 60°	82°	84°	80°
Output Swing	> 0.5 Vpp	0.8 Vpp	0.9 Vpp	0.86 Vpp
Power Consumption	< 12 mW	5.73 mW	5.89 mW	5.55 mW
Systematic Offset	< 3 mV	1.436 mV	1.785 mV	1.171 mV

 


Figure 2: Gain & Phase Margin for 27°C & 6pF Capacitor

The **27°** temperature gave a gain of **51.89 dB**, phase margin of **82°**, unity-gain bandwidth of **341 MHz** and pulled a current of **3.1844 mA** causing a **5.73 mW** power consumption. Meeting all of the specifications wanted in the problem statement.

 


Figure 3: Gain & Phase Margin for 100°C & 7.2pF Capacitor

The **100°** temperature gave a gain of **51.18 dB**, phase margin of **84°**, unity-gain bandwidth of **252 MHz** and pulled a current of **3.2761 mA** causing a **5.89 mW** power consumption. Meeting all of the specifications wanted in the problem statement. For a high temperature, the gain and UGB went down while everything else went up.

 


Figure 4: Gain & Phase Margin for -40°C & 4.8pF Capacitor

The **-40°** temperature gave a gain of **52.45 dB**, phase margin of **80°**, unity-gain bandwidth of **503 MHz** and pulled a current of **3.0845 mA** causing a **5.55 mW** power consumption. Meeting all of the specifications wanted in the problem statement. For a low temperature, the gain, phase margin, power consumption, systematic offset, and UGB went down while everything else went up.

 


Figure 5: Systematic Offset for 27°C & 6pF Capacitor

The input-referred systematic offset for 27° was $900\text{mV} - 898.564\text{ mV} = 1.436\text{ mV}$.

 


Figure 6: Systematic Offset for 100°C & 7.2pF Capacitor

The input-referred systematic offset for 100° was $900\text{mV} - 898.215\text{ mV} = 1.785\text{ mV}$.

 


Figure 7: Systematic Offset for -40°C & 4.8pF Capacitor

The input-referred systematic offset for -40° was $900\text{mV} - 898.829 \text{ mV} = 1.436 \text{ mV}$.

 


Figure 8: Testbench for Output Swing

Figure 8 shows the testbench set up I used to graph and calculate the output swing for each temperature and capacitor value.

 


Figure 9: Measurements Taken to Plot Output Swing

After running a DC sweep for the offset from -10 mV to 10 mV and an AC analysis, I plotted the DC voltage and took the db20 of the derivative of it. Combining these two graphs together, I utilized the Y vs. Y function on the graph to get the output swing curve.

 


Figure 10: Output Swing Graph for 27° & 6pF Capacitor

For 27° I marked a line at -3 dB from the peak (51.89 dB) gain to get the output swing of **0.8 V**.

 


Figure 10: Output Swing Graph for 100° & 7.2pF Capacitor

For **100°** I marked a line at -3 dB from the peak (51.19 dB) gain to get the output swing of **0.9 V**.

 


Figure 10: Output Swing Graph for -40° & 4.8pF Capacitor

For -40° I marked a line at -3 dB from the peak (52.45 dB) gain to get the output swing of **0.86 V**.