

Second and Higher-Order Delta-Sigma Modulators

MEAD March 2008

Richard Schreier

Richard.Schreier@analog.com



R. SCHREIER

ANALOG DEVICES, INC.

Overview

1 MOD2: The 2nd-Order Modulator


- MOD2 from MOD1
- NTF (predicted & actual)
- SQNR performance
- Stability
- Deadbands, Distortion & Tones (audio demo)
- Topological Variants

2 Higher-Order Modulators

- MODN from MOD1
- NTF Zero Optimization
- Stability
- SQNR limits for binary and multi-bit modulators
- Topology Overview

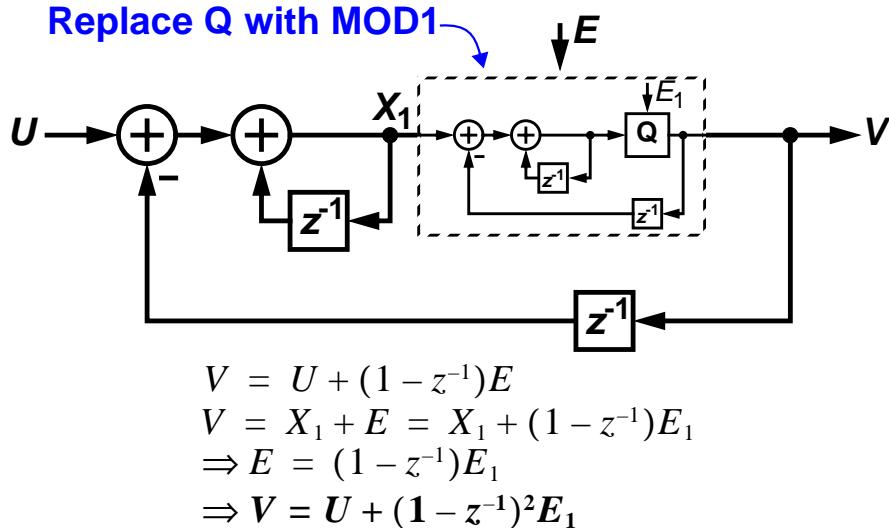1. MOD2 from MOD1


- Replace the quantizer in MOD1 with another copy of MOD1 in a recursive fashion:



3

Simplified Diagram

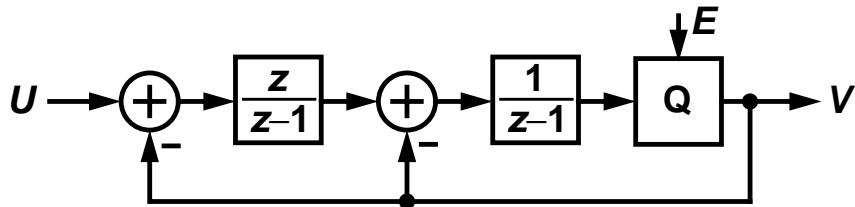
- Combine feedback paths, absorb feedback delay into second integrator...



$$V(z) = z^{-1}U(z) + (1 - z^{-1})^2E(z)$$

- $NTF(z) = (1 - z^{-1})^2$ and the STF is $STF(z) = z^{-1}$
- MOD2's NTF is the *square* of MOD1's NTF

NTF Comparison

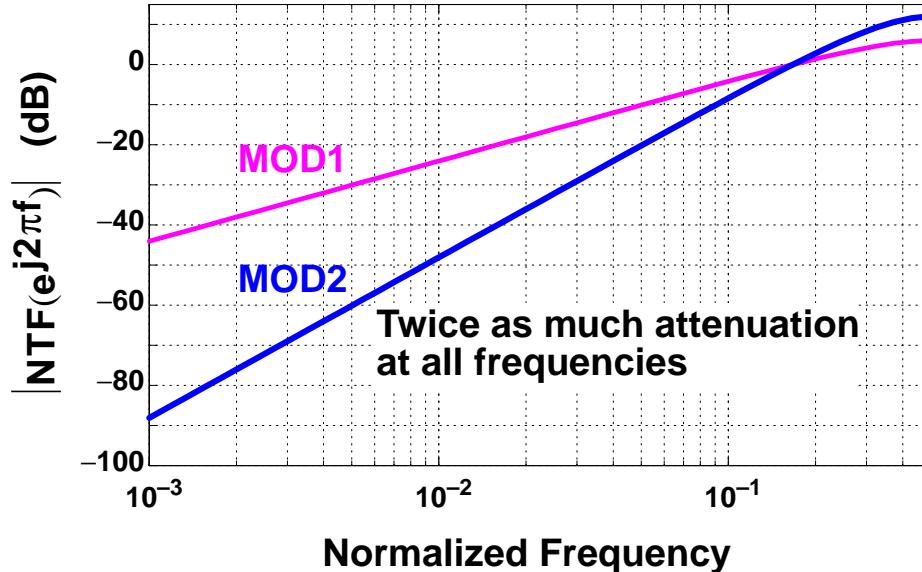

5

Predicted Performance

- In-band quantization noise power


$$\begin{aligned}
 IQNP &= \int_0^{1/(2 \cdot OSR)} |NTF(e^{j2\pi f})|^2 \cdot S_{ee}(f) df \\
 &\approx \int_0^{1/(2 \cdot OSR)} (2\pi f)^4 \cdot 2\sigma_e^2 df \\
 &= \frac{\pi^4 \sigma_e^2}{5(OSR)^5} \quad \times
 \end{aligned}$$

- Quantization noise drops as the 5th power of OSR!

SQNR increases at 15 dB per octave increase in OSR.

6

Predicted SQNR vs. OSR

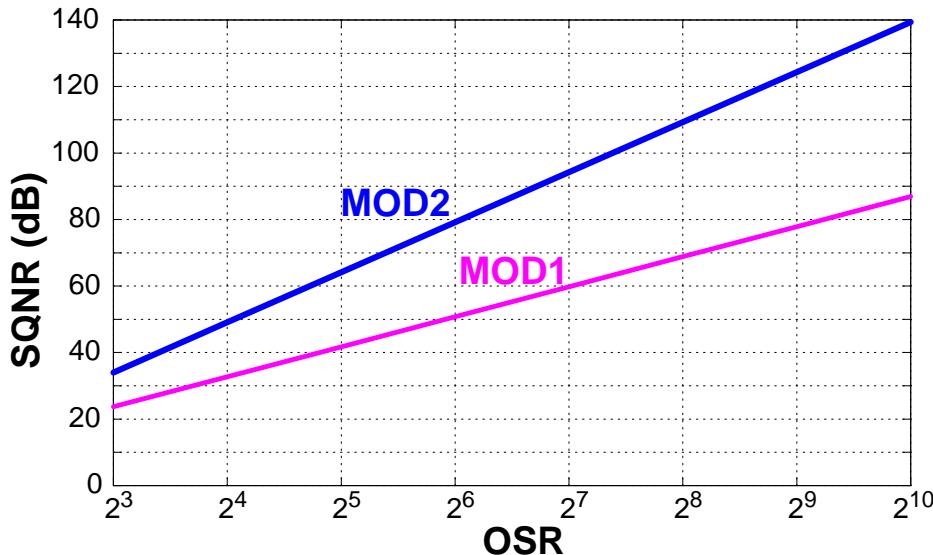


- For $OSR = 128$ and binary quantization, the predicted SQNR of MOD2 is 94.2 dB

7

MOD2 Simulated PSD

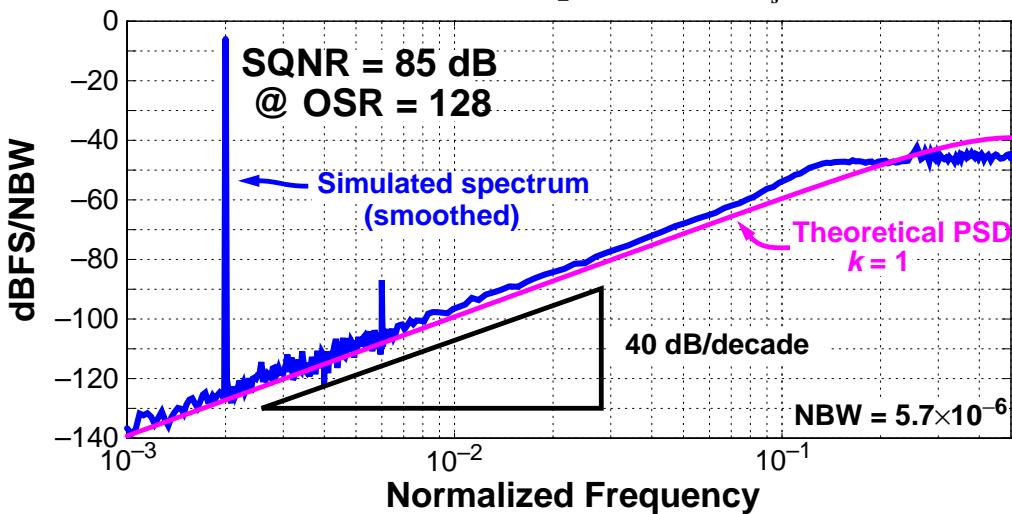Half-scale sine-wave input with $f \approx f_s/500$




- Observed PSD similar to theory (40 dB/decade slope)
But 3rd harmonic is visible and in-band PSD is slightly higher.

8

Gain of the Quantizer in MOD2


- The effective quantizer gain can be computed from the simulation data using
$$k = \frac{\langle v, y \rangle}{\langle y, y \rangle} = \frac{E[|y|]}{E[y^2]} \quad [\text{S&T Eq. 2.5}]$$
- For the preceding simulation, $k = 0.63$.
- $k \neq 1$ alters the NTF:
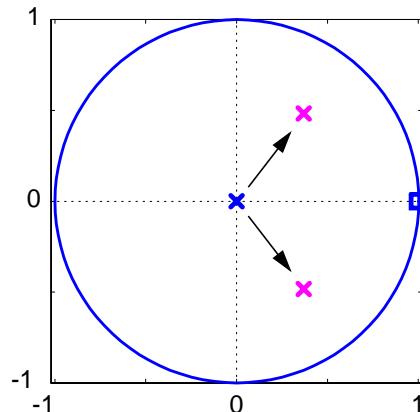
$$NTF_k(z) = \frac{NTF_1(z)}{k + (1-k)NTF_1(z)}$$



9

Revised PSD Prediction

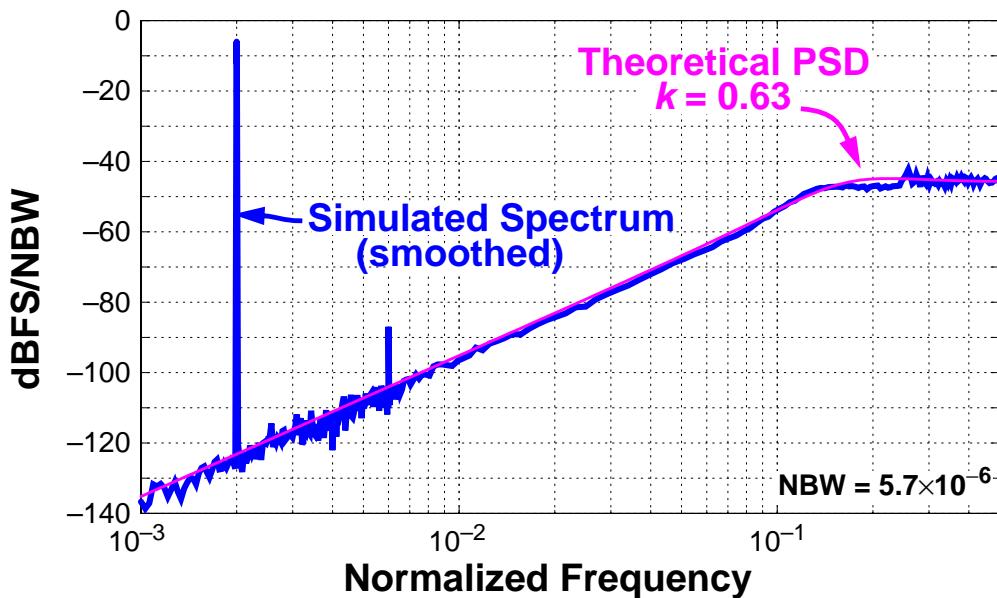


- Agreement is now excellent

Variable Quantizer Gain

- When the input is small (below -12 dBFS), the effective gain of the quantizer is $k = 0.75$
- The “small-signal NTF” is thus
$$NTF(z) = \frac{(z-1)^2}{z^2 - 0.5z + 0.25}$$
- This NTF has 2.5 dB less quantization noise suppression than the $(1-z^{-1})^2$ NTF derived from the assumption that $k = 1$
Thus the SQNR should be about 2.5 dB lower than \times .
- As the input signal increases, k decreases and the suppression of quantization noise degrades
SQNR increases less quickly than the signal power, and eventually the SQNR saturates and then decreases as the signal power is increased.

11

Simulated SQNR of MOD2

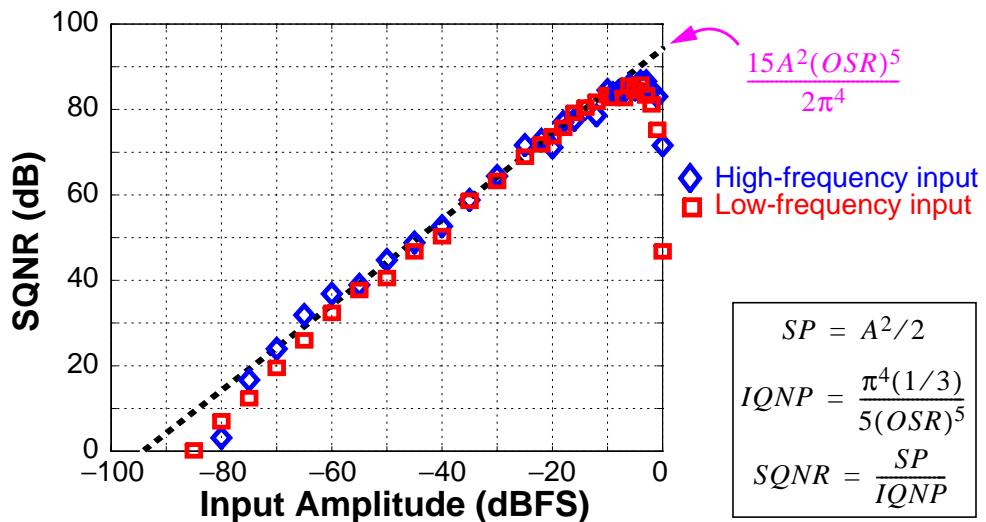

- Well-modeled by ideal formula; less erratic than MOD1
Saturation at high signal levels due to decreased quantizer gain and altered NTF. (Worse with low-frequency inputs.)

12

Stability of MOD2


- Known to be stable with DC inputs up to full-scale, but the state bounds blow up as $|u| \rightarrow 1$

Hein [ISCAS 1991]: $|u| \leq 1 \Rightarrow$

$$|x_1| \leq |u| + 2 \text{ (output of 1st integrator)}$$

$$|x_2| \leq \frac{(5 - |u|)^2}{8(1 - |u|)} \text{ (output of 2nd integrator)}$$

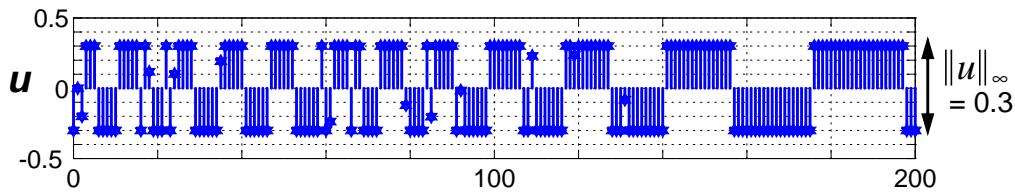
- However, with a hostile input (whose magnitude is less than 30% of full-scale) MOD2 can be driven unstable!



- As a result of this input-dependent stability, it is wise to keep the input below 70-90% of full-scale

Deadbands, Distortion & Tones

Audio Comparison of MOD1 and MOD2

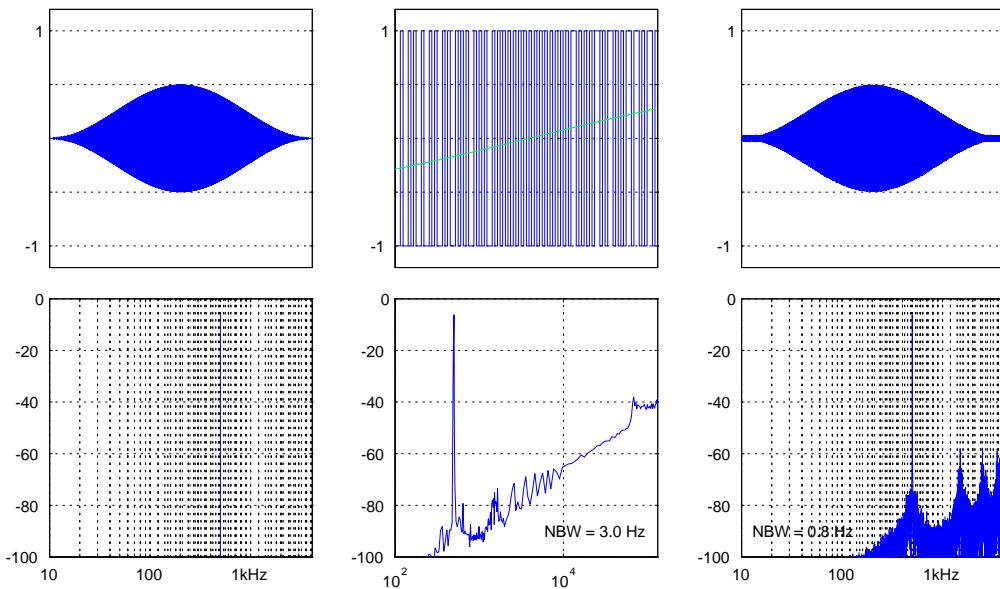

Observations

Tones


- **Quantization noise of MOD1 is distinctly non-white**
Audible tones when input is near zero, or near other simple rational fractions of full-scale.
- **MOD2 is better than MOD1 in terms of its tendency toward tonal behavior**

Dead-bands

- **MOD1 has dead-bands whose widths are proportional to $1/A$, where A is the gain of the internal op-amp**
- **MOD2 has dead-bands whose widths are proportional to $1/A^2$**
- **Dead-band behavior is less problematic in MOD2**

15

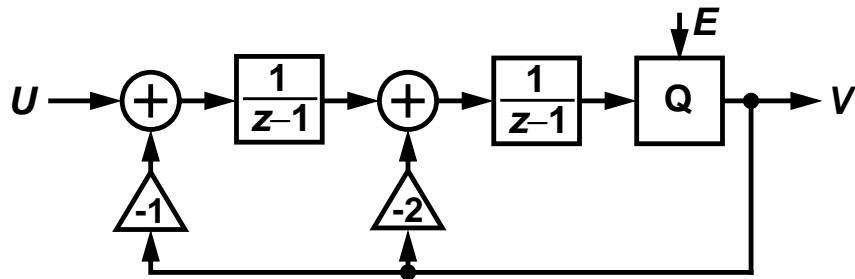Topological Variant– Delaying Integrators




$$NTF(z) = (1 - z^{-1})^2 \quad STF(z) = z^{-2}$$

- + **Delaying integrators reduce the settling requirements**
Can decouple the integration phase from the driving phase

16

Topological Variant– Feed-Forward

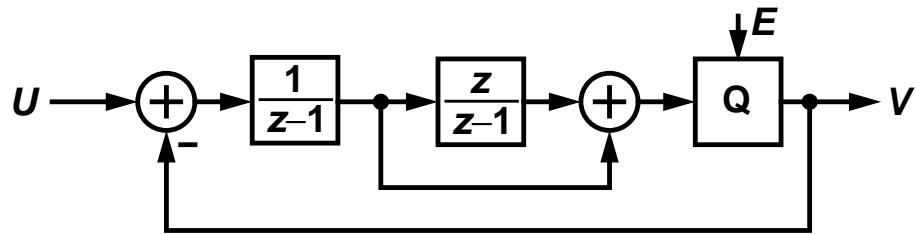


$$NTF(z) = (1 - z^{-1})^2 \quad STF(z) = 2z^{-1} - z^{-2}$$

- + **Output of first integrator has no DC component**
Dynamic range requirements of this integrator are relaxed.
- **Although $|STF| \approx 1$ near $\omega = 0$, $|STF| = 3$ for $\omega = \pi$**
Instability is more likely.

17

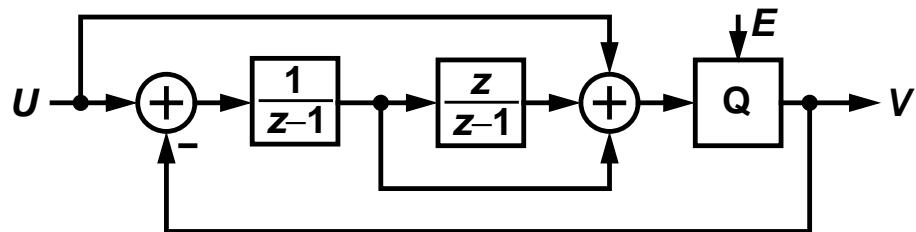Topological Variant– Feed-Forward with Extra Input Feed-In




$$NTF(z) = (1 - z^{-1})^2 \quad STF(z) = 1$$

- + **No DC component in either integrator's output**
Reduced dynamic range requirements in both integrators.
- + **Perfectly flat STF**
No increased risk of instability.

18

Topological Variant– Error Feedback

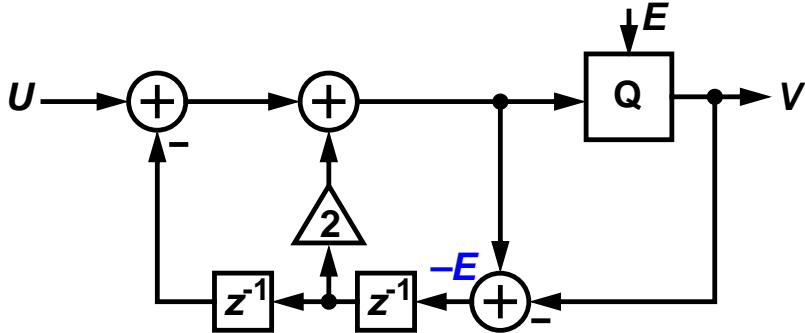


$$NTF(z) = (1 - z^{-1})^2 \quad STF(z) = 1$$

+ Simple

– Very sensitive to gain errors

Only suitable for digital implementations.

2. MODN from MOD2

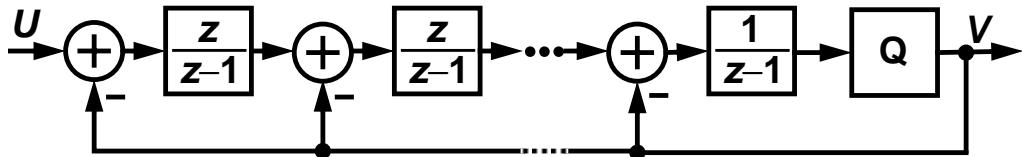

$$V = E + \frac{1}{z-1} \left(-V + \frac{z}{z-1} \left(-V + \dots + \frac{z}{z-1} (-V + U) \right) \right)$$

$$(1 - z^{-1})^N V = (1 - z^{-1})^N E - ((1 - z^{-1})^{N-1} + (1 - z^{-1})^{N-2} + \dots + 1) z^{-1} V + z^{-1} U$$


$$(1 - z^{-1})^N V = (1 - z^{-1})^N E - \left(\frac{(1 - z^{-1})^N - 1}{1 - z^{-1} - 1} \right) z^{-1} V + z^{-1} U$$

$$(1 - z^{-1})^N V = (1 - z^{-1})^N E - \left(\frac{(1 - z^{-1})^N - 1}{z^{-1}} \right) z^{-1} V + z^{-1} U$$

$$\therefore V(z) = z^{-1} U(z) + (1 - z^{-1})^N E(z)$$

- NTF of MODN is the N^{th} power of MOD1's NTF

NTF Comparison

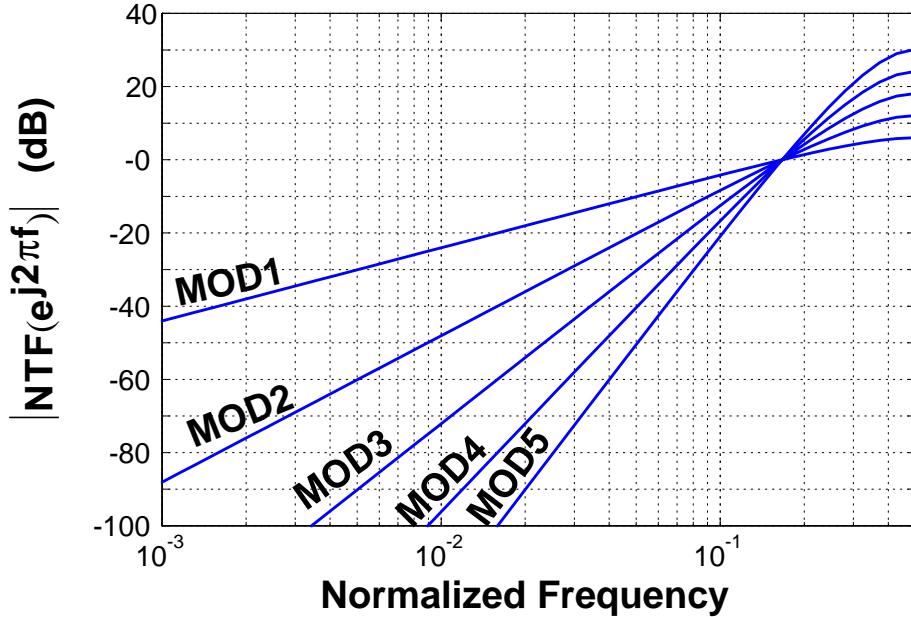

21

Predicted Performance

- In-band quantization noise power

$$\begin{aligned}
 IQNP &= \int_0^{1/(2 \cdot OSR)} |NTF(e^{j2\pi f})|^2 \cdot S_{ee}(f) df \\
 &\approx \int_0^{1/(2 \cdot OSR)} (2\pi f)^{2N} \cdot 2\sigma_e^2 df \\
 &= \frac{\pi^{2N}}{(2N+1)(OSR)^{2N+1}} \sigma_e^2
 \end{aligned}$$


- Quantization noise drops as the $(2N+1)^{\text{th}}$ power of OSR!

SQNR increases at $(6N+3)$ dB per octave increase in OSR.

22

Improving NTF Performance— Zero Optimization

- Minimize the rms in-band value of H by finding the a_i which minimize the integral of $|H|^2$ over the passband.
Normalize passband edge to 1 for ease of calculation.

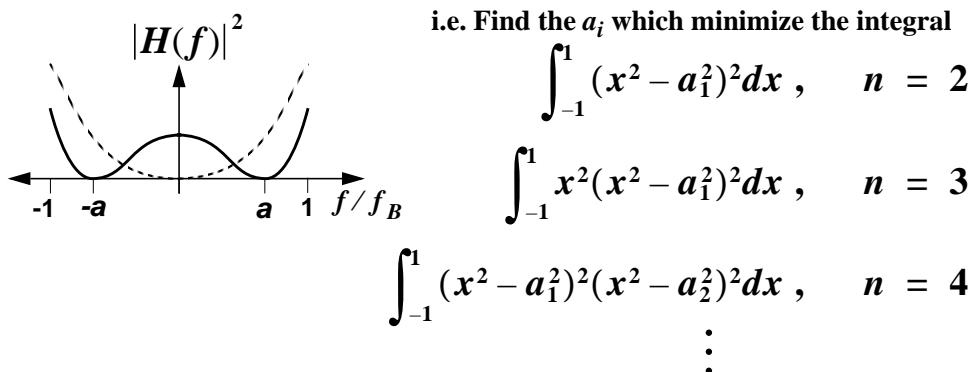

23

Solutions Up to Order = 8


Order	Optimal Zero Placement Relative to f_B	SQNR Improvement
1	0	0 dB
2	$\pm \frac{1}{\sqrt{3}}$	3.5 dB
3	$0, \pm \sqrt{\frac{3}{5}}$	8 dB
4	$\pm \sqrt{\frac{3}{7}} \pm \sqrt{\left(\frac{3}{7}\right)^2 - \frac{3}{35}}$	13 dB
5	$0, \pm \sqrt{\frac{5}{9}} \pm \sqrt{\left(\frac{5}{9}\right)^2 - \frac{5}{21}}$ [Y. Yang]	18 dB
6	$\pm 0.23862, \pm 0.66121, \pm 0.93247$	23 dB
7	$0, \pm 0.40585, \pm 0.74153, \pm 0.94911$	28 dB
8	$\pm 0.18343, \pm 0.52553, \pm 0.79667, \pm 0.96029$	34 dB

24

Topological Implication

- Apply feedback around pairs integrators:

2 Delaying Integrators

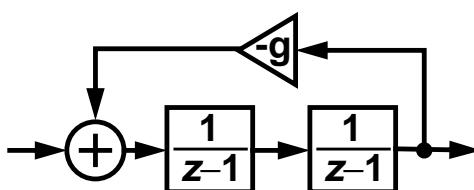


Poles are the roots of

$$1 + g \left(\frac{1}{z-1} \right)^2 = 0$$

i.e. $z = 1 \pm j\sqrt{g}$

Not quite on the unit circle,
but fairly close if $g \ll 1$.

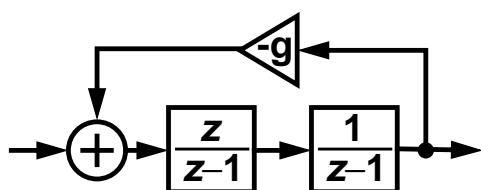Non-delaying + Delaying Integrators (LDI Loop)



Poles are the roots of

$$1 + \frac{gz}{(z-1)^2} = 0$$


i.e. $z = e^{\pm j\theta}$, $\cos\theta = 1 - g/2$

Precisely on the unit circle,
regardless of the value of g .

25

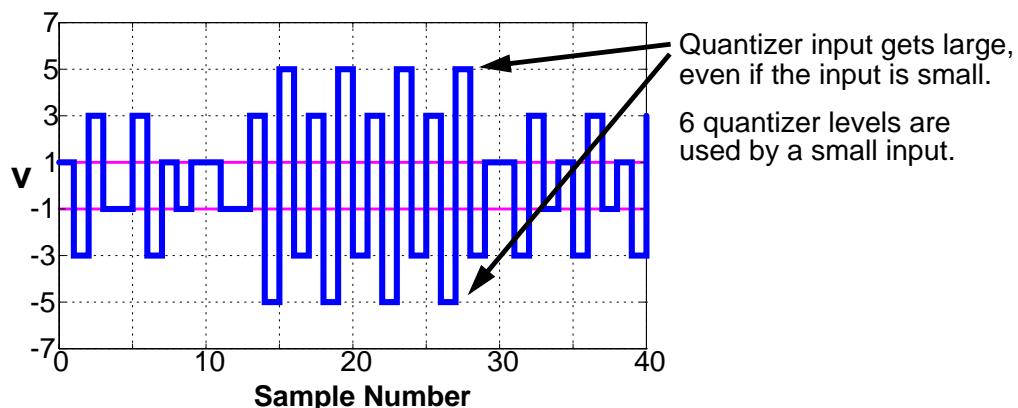
Problem: High-Order Modulators Want Multi-bit Quantizers

e.g. a 3rd-Order Modulator
with an Infinite Quantizer and Zero Input



26

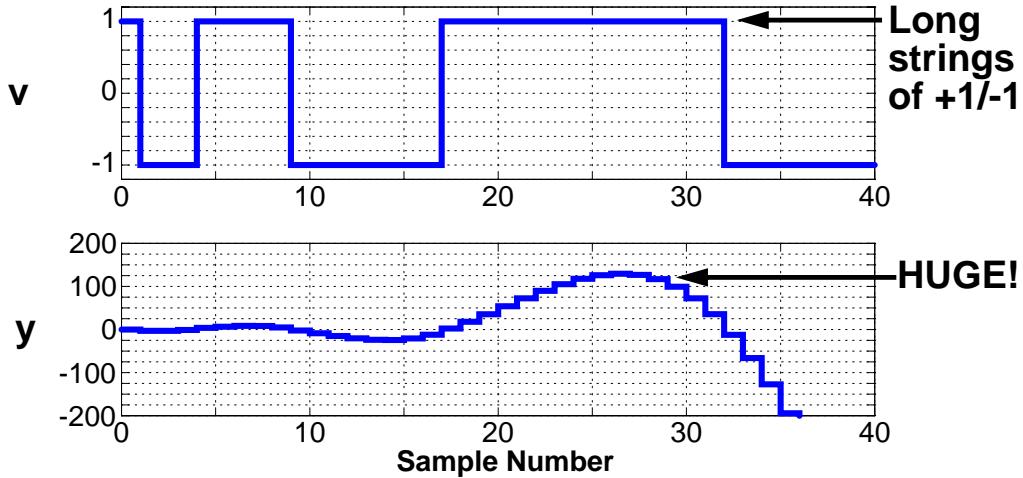The 3rd-Order Modulator is Unstable with a Binary Quantizer



- The quantizer input grows without bound
The modulator is unstable, even with an arbitrarily small input.

27

Solutions to the Stability Problem

Historical Order

1 Use multi-bit quantization

Originally considered undesirable because the inherent linearity of a 1-bit DAC is lost when a multi-bit quantizer is used.

Less of an issue now that mismatch-shaping is available.

2 Use a more general NTF (not pure differentiation)

Lower the NTF gain so that quantization error is amplified less.

A common rule of thumb is to limit the maximum NTF gain to ~1.5.

Unfortunately, limiting the NTF gain reduces the amount by which quantization noise is attenuated.

3 Use a multi-stage (MASH) architecture

More on this later in the course.

- Combinations of the above are possible

28

Multi-bit Quantization

- Can show that a modulator with NTF H and unity STF is guaranteed to be stable if $|u| < u_{max}$ at all times, where $u_{max} = nlev + 1 - \|h\|_1$ and $\|h\|_1 = \sum_{i=0}^{\infty} |h(i)|$
- In MODN,
 $H(z) = (1 - z^{-1})^N$, so
 $h(n) = \{1, -a_1, a_2, -a_3, \dots, (-1)^N a_N, 0 \dots\}$, where $a_i > 0$ and thus $\|h\|_1 = H(-1) = 2^N$.
- Thus $nlev = 2^N$ implies $u_{max} = nlev + 1 - \|h\|_1 = 1$.
MODN is guaranteed to be stable with an n -bit quantizer if the input magnitude is less than $\Delta/2$.
This result is extremely conservative.
- Similarly, $nlev = 2^{N+1}$ guarantees the modulator is stable for inputs up to 50% of full-scale.

29

Proof of $\|h\|_1$ Criterion By Induction

- Assume STF = 1 and $(\forall n)(|u(n)| \leq u_{max})$.
- Assume $|e(i)| \leq 1$ for $i < n$. [Induction Hypothesis]

Then

$$\begin{aligned} |y(n)| &= \left| u(n) + \sum_{i=1}^{\infty} h(i)e(n-i) \right| \\ &\leq u_{max} + \sum_{i=1}^{\infty} |h(i)||e(n-i)| \\ &\leq u_{max} + \sum_{i=1}^{\infty} |h(i)| = u_{max} + \|h\|_1 - 1 \end{aligned}$$

- Thus $(u_{max} \leq nlev + 1 - \|h\|_1) \Rightarrow (|y(n)| \leq nlev) \Rightarrow (|e(n)| \leq 1)$
- And by induction $|e(i)| \leq 1$ for all $i > 0$. QED

30

The Lee Criterion for Stability in a 1-bit Modulator: $\|H\|_\infty \leq 2$

[Wai Lee, 1987]

- The measure of the “gain” of H is the maximum magnitude of H (over frequency), otherwise known as the *infinity-norm* of H :

$$\|H\|_\infty \equiv \max_{\omega \in [0, 2\pi]} (H(e^{j\omega}))$$

Q: Is the Lee criterion necessary for stability?

For MOD2, $H(z) = (1 - z^{-1})^2$ and so $\|H\|_\infty = H(-1) = 4$.

Since MOD2 is known to be stable, the Lee criterion is not necessary.


Q: Is the Lee criterion sufficient to ensure stability?

No. There are lots of counter-examples, but $\|H\|_\infty \leq 1.5$ often works.

- Let’s look at some examples

The NTF Family Used by the $\Delta\Sigma$ Toolbox

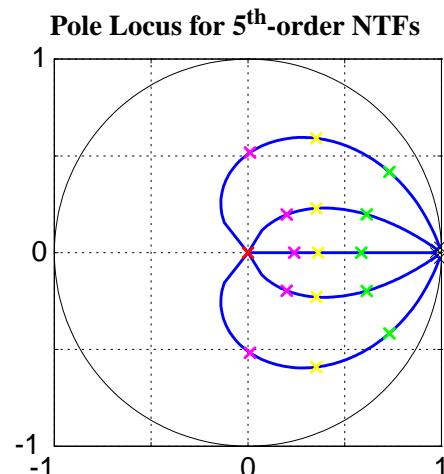
- Poles chosen such that $1/\text{den}(H(z))$ is a maximally flat transfer function.



For lowpass modulators, the pole placement is similar to a Butterworth transfer function. Yields a flat STF for both lowpass and bandpass modulators employing the CRFB topology with one feed-in.


σ_e VS. $\|H\|_\infty$

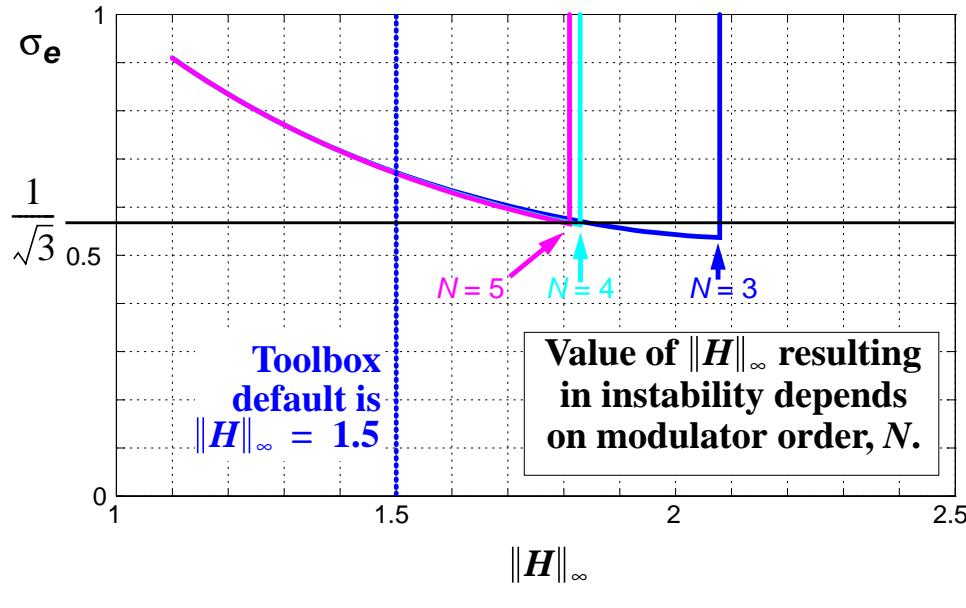Binary modulators of order $N = 3, 4, 5$ with a small input



33


Two 5th-Order Binary Modulators

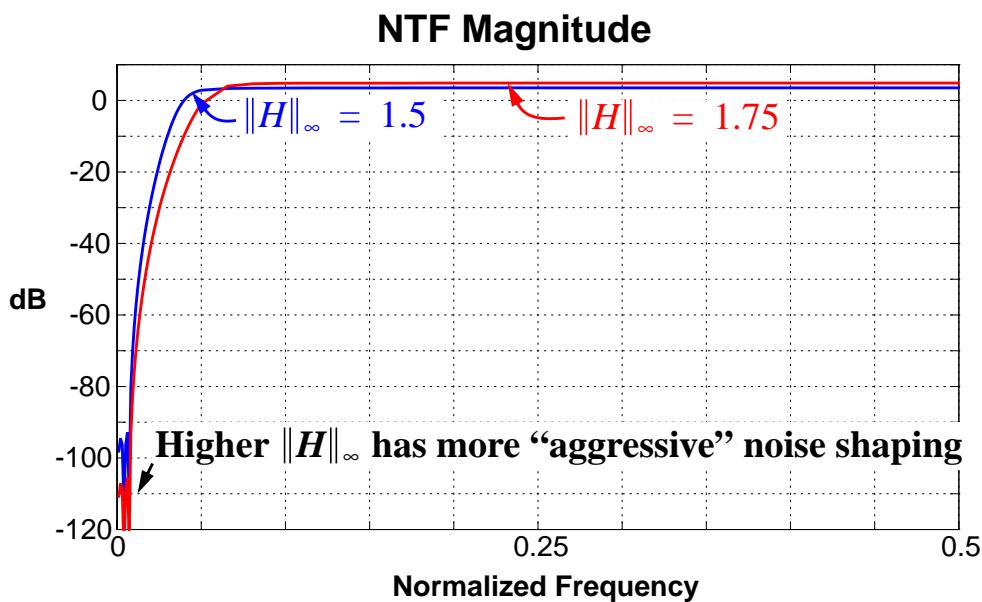

34

σ_e VS. u_{DC}


For the two 5th-order modulators

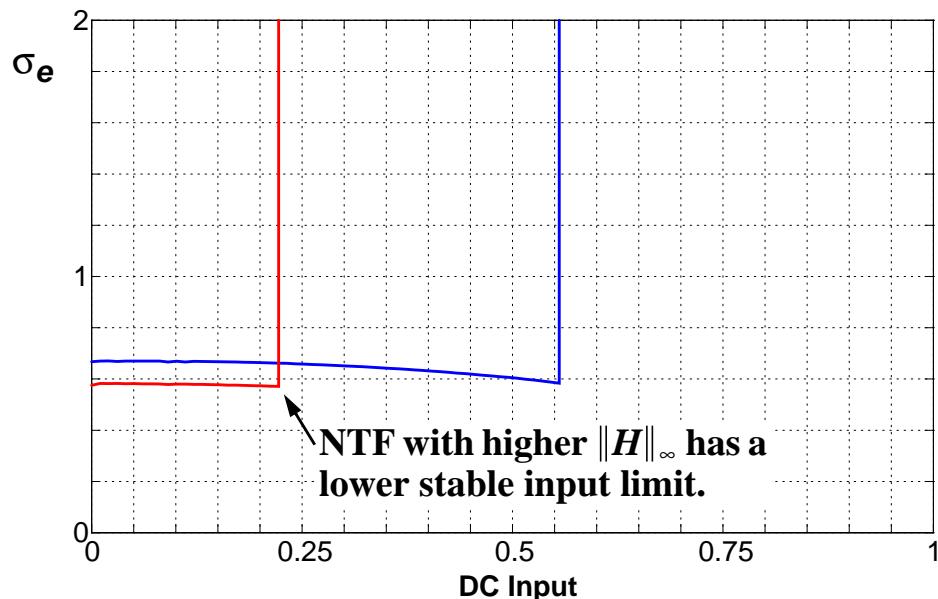

35


SQNR vs. $\|H\|_\infty$

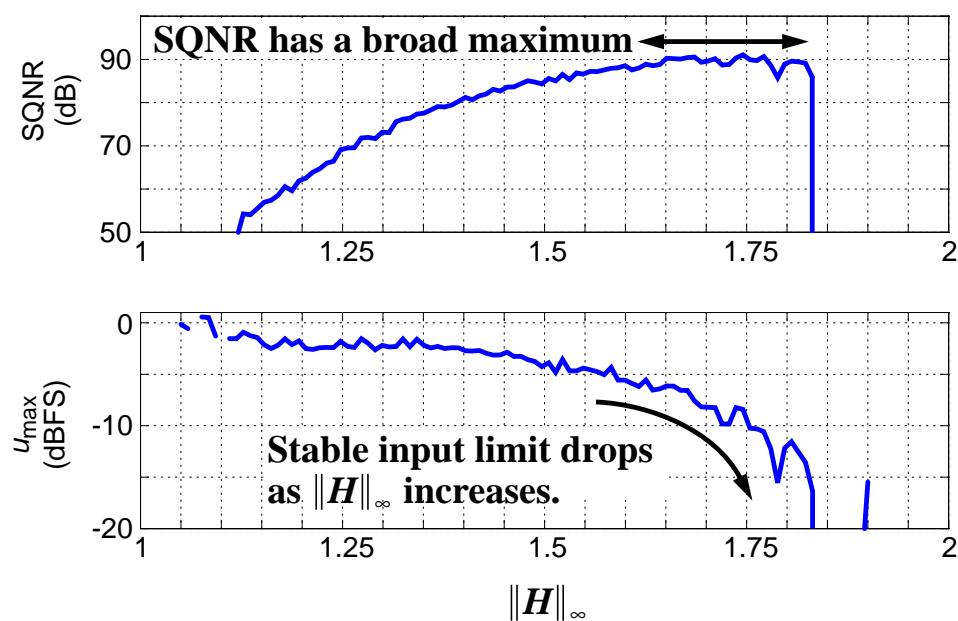5th-Order NTFs, Binary Quantization, OSR = 32




36

SQNR Limits for Binary Modulators

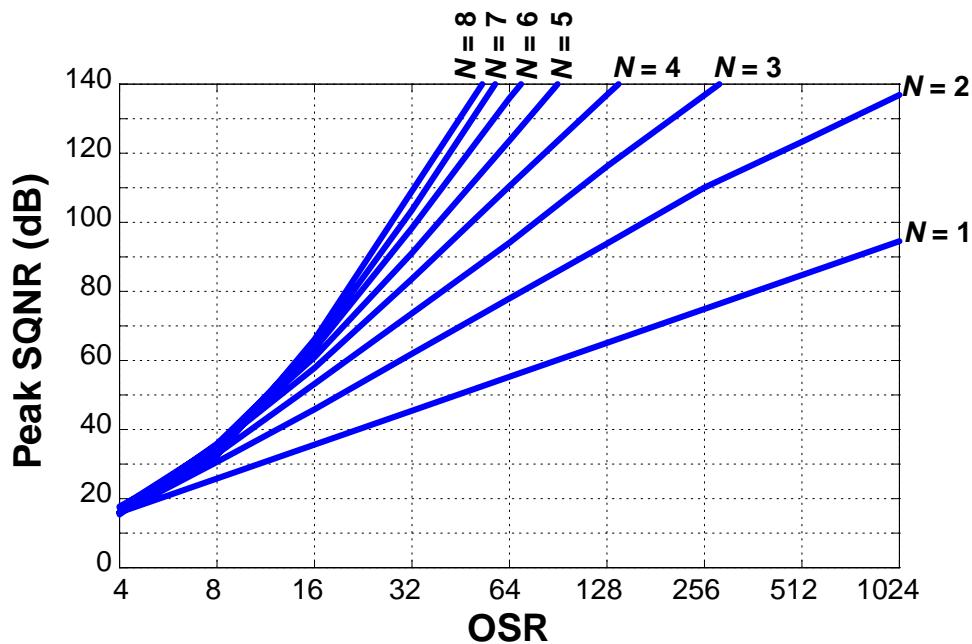


37

SQNR Limits for 2-bit Modulators

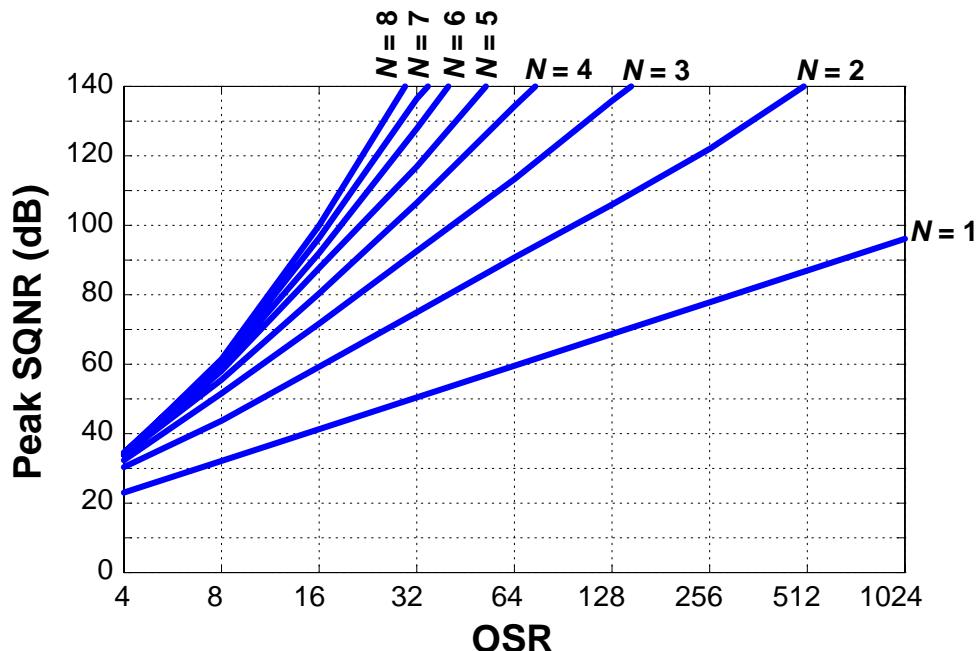


38

SQNR Limits for 3-bit Modulators

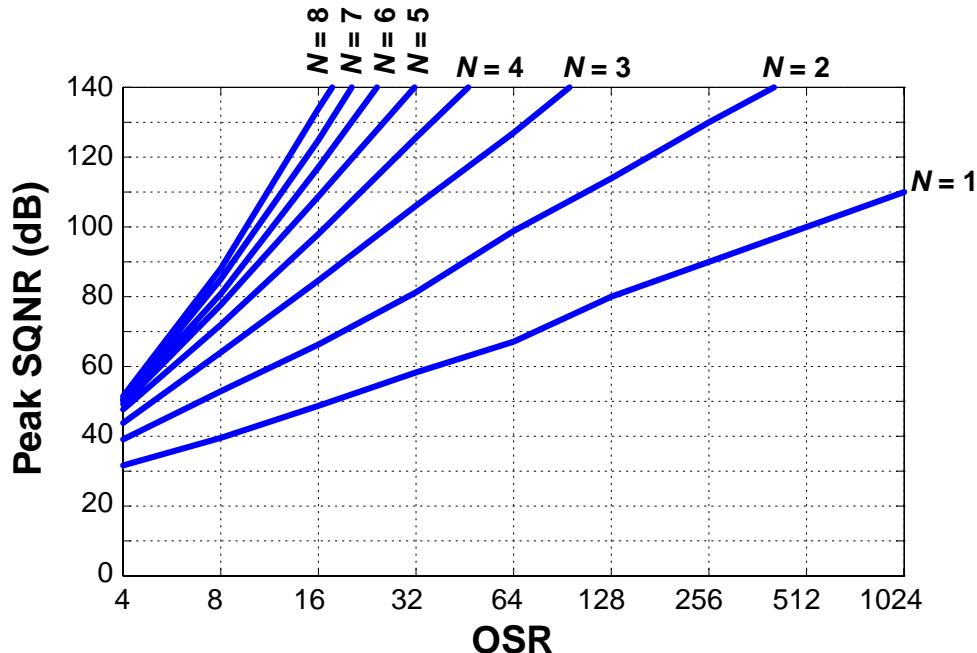

39

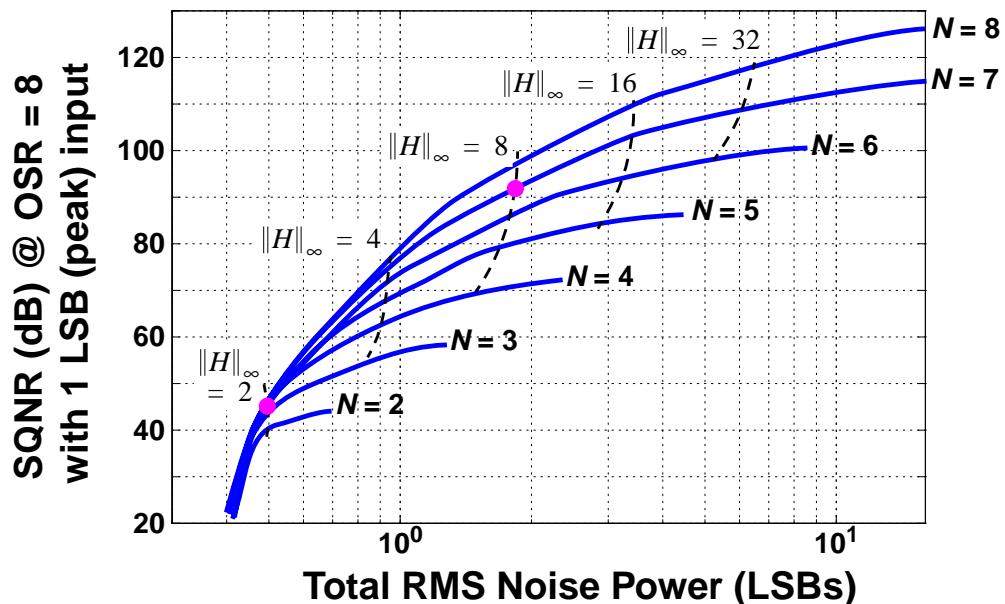
Theoretical SQNR Limits for Multi-Bit Modulators



40

Example Waveforms


7th-order 17-level modulator, $\|H\|_\infty = 2$

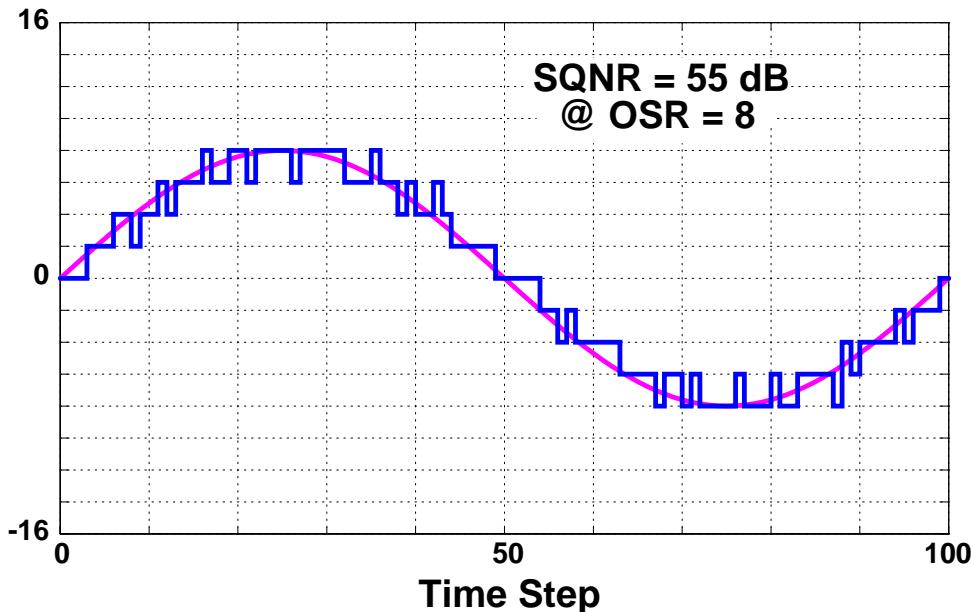

41


Example Waveforms

7th-order 17-level modulator, $\|H\|_\infty = 8$

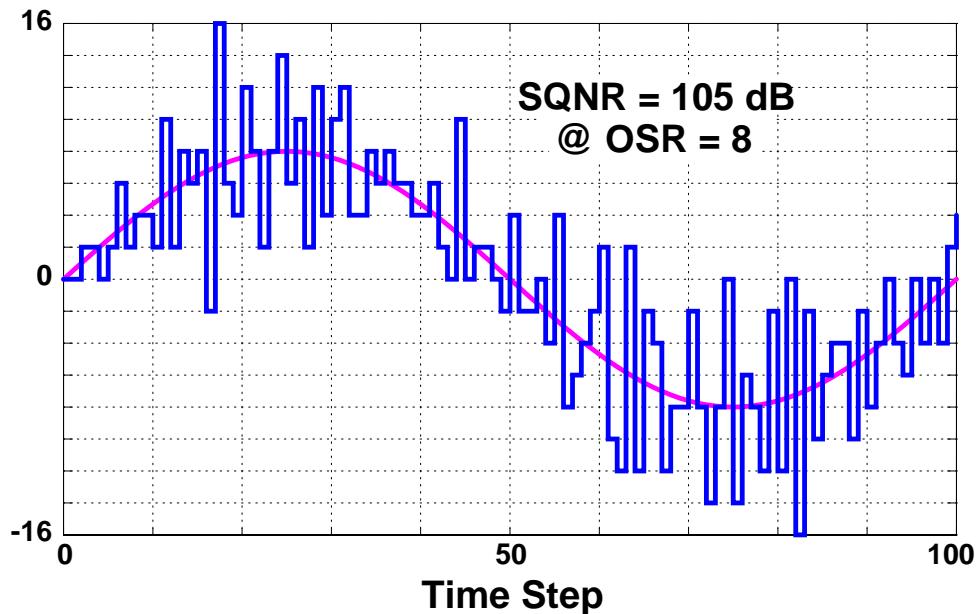


42

Spectra

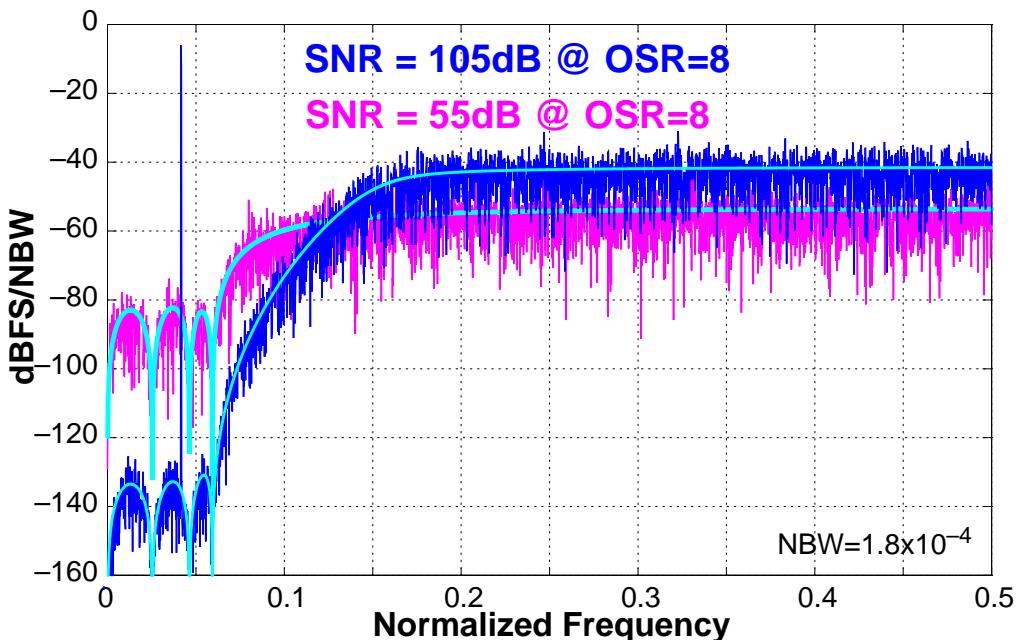


43

SNR Curves

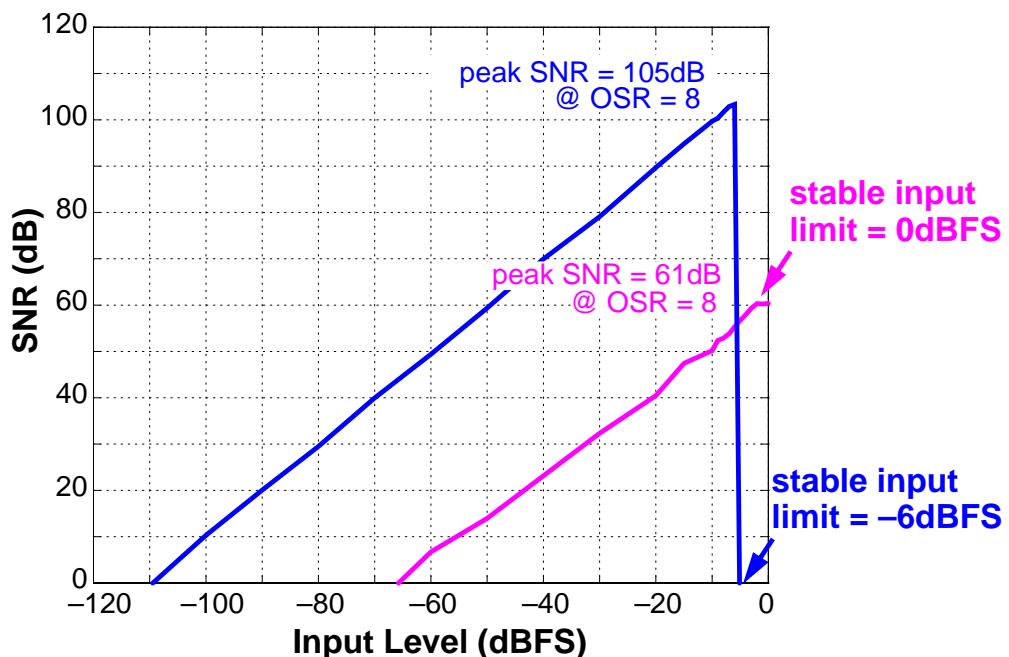

44


Example Topology– Feedback

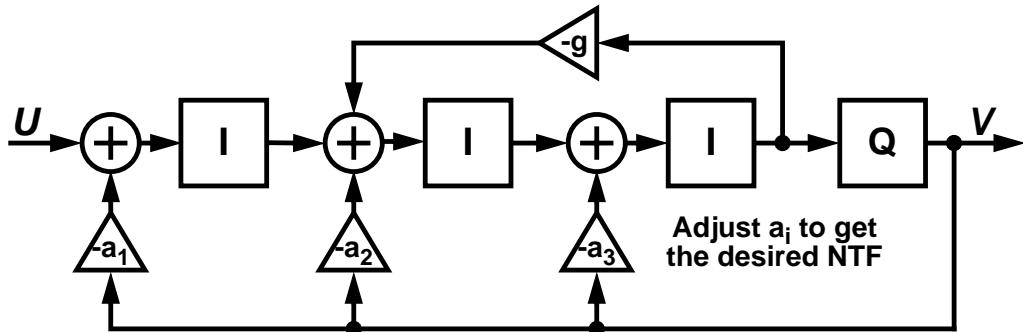

- N integrators precede the quantizer
- Feedback from the quantizer to the input of each integrator (via a DAC)
- Local feedback around pairs of integrators is possible
- Multiple input feed-in branches are also possible

45

Example Topology– Feedforward

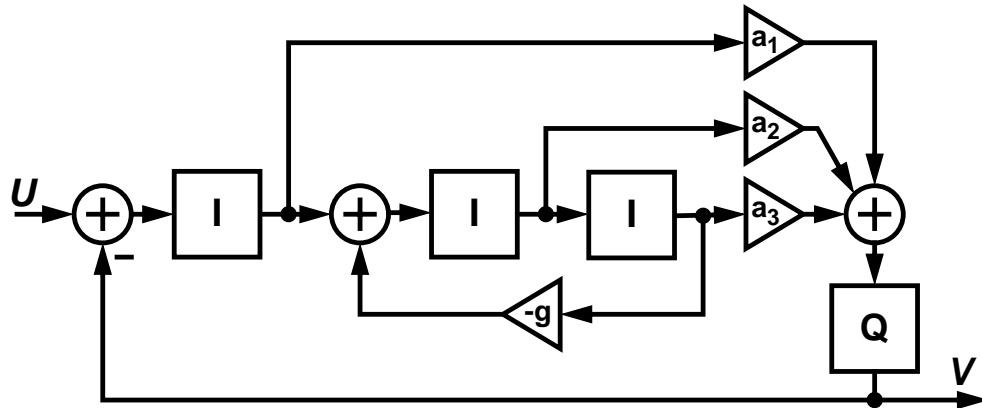


- N integrators in a row
- Each integrator output is fed forward to the quantizer
- Local feedback around pairs of integrators is possible
- Multiple input feed-in branches are also possible

46

General Single-Quantizer $\Delta\Sigma$ Modulator

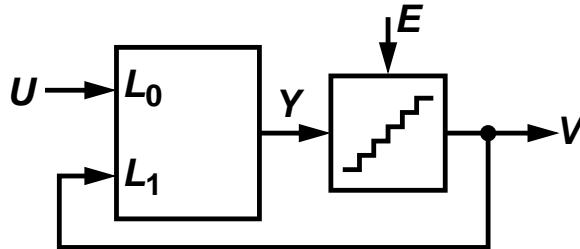- The input to the quantizer is some linear combination of the input to the modulator and the fed-back output



$$\begin{aligned} Y &= L_0 U + L_1 V \\ V &= Y + E \end{aligned} \quad \Rightarrow \quad \begin{aligned} V &= GU + HE, \text{ where} \\ H &= \frac{1}{1 - L_1} \quad \& \quad G = L_0 H \end{aligned}$$

Inverse Relations:
 $L_1 = 1 - 1/H, L_0 = G/H$

47

Summary

- MOD2 is better than MOD1**
 - Higher SQNR
 - Whiter quantization noise
 - Smaller deadbands
- MODN is better than MOD2**
 - Even higher SQNR
 - Tonal behavior unlikely
 - Deadbands virtually eliminated
- BUT high-order modulators must deal with instability**
 - Modify the NTF, reduce the input range, and/or use multi-bit quantization

48