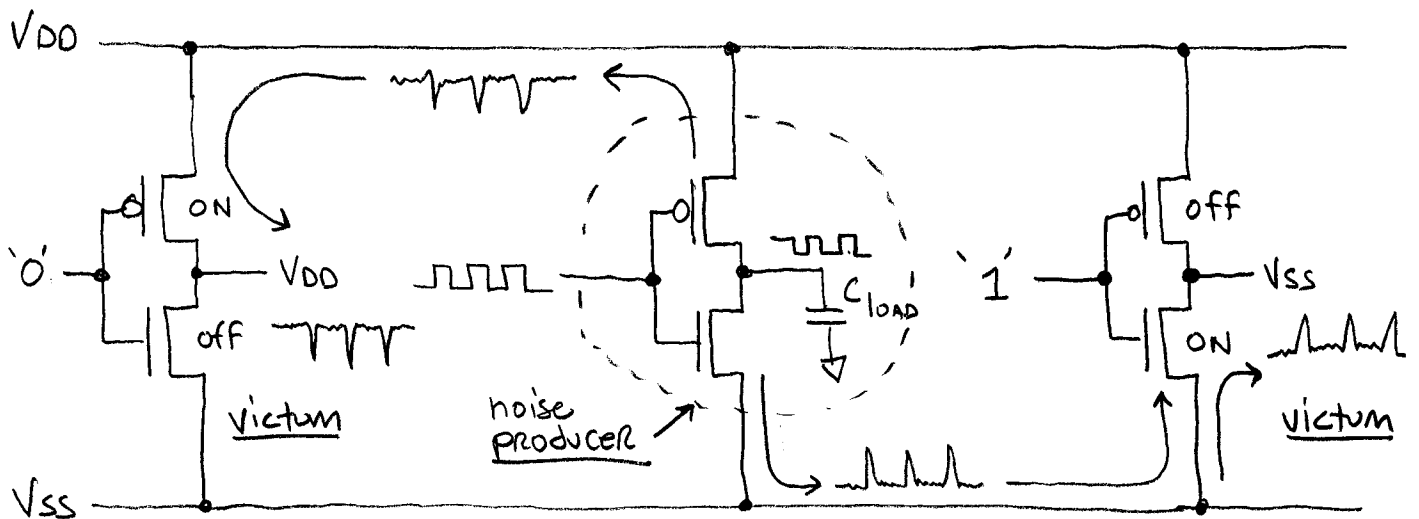



Simultaneous Switching Outputs

Description of Problem

- High density, high speed VLSI devices have many drivers that may switch simultaneously
- The combined current from all the output drivers can produce significant power and ground noise called ΔI noise. This noise can cause several different flavors of malfunction.
- Single driver scenario



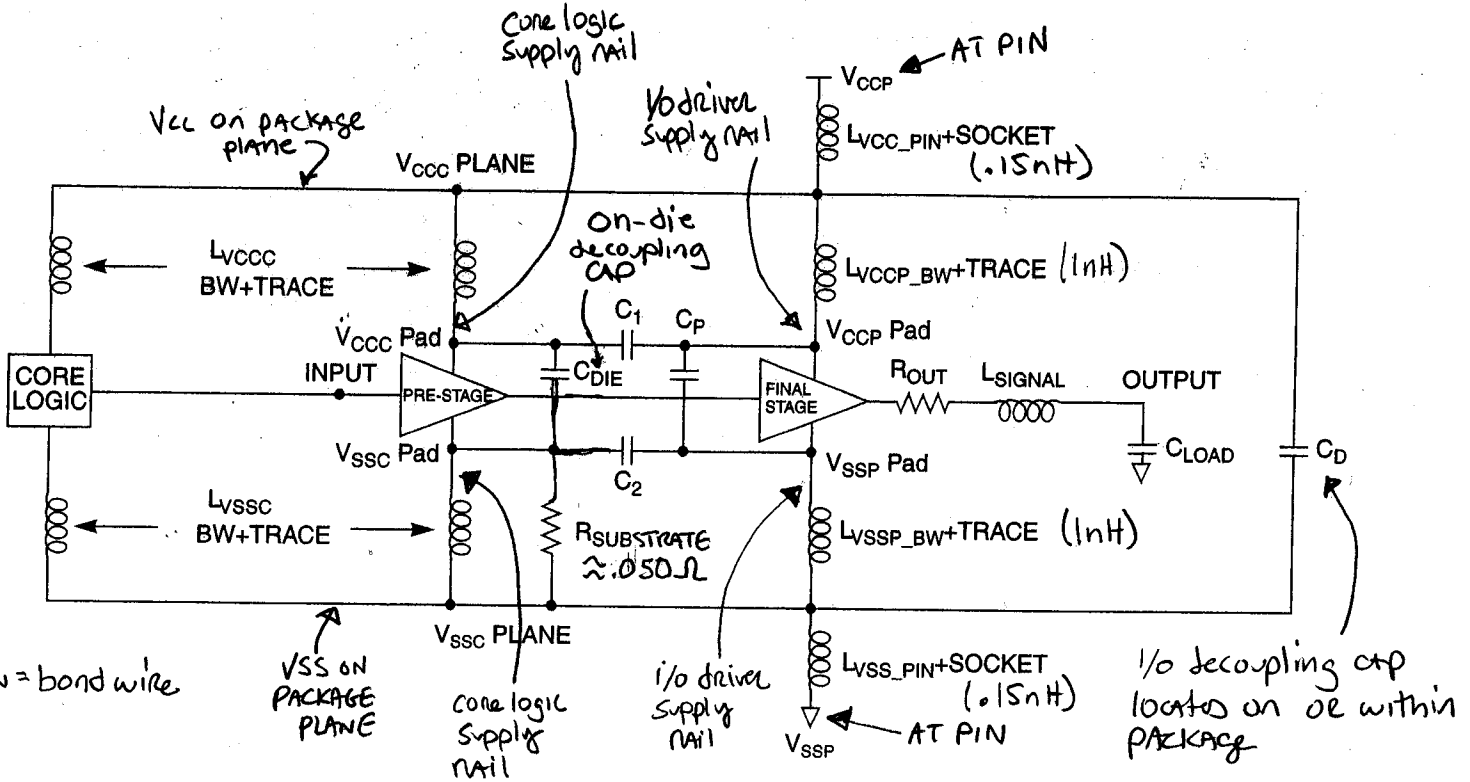
- When P-channel xistor is "on", output is connected to V_{DD} through a small resistor
- When N-channel xistor is "on" output is connected to V_{SS} .
- Therefore, noise on either power rail is directly coupled to an active output.



I/O buffer and PGA circuit

Core + i/o supplies are shorted together at the pins

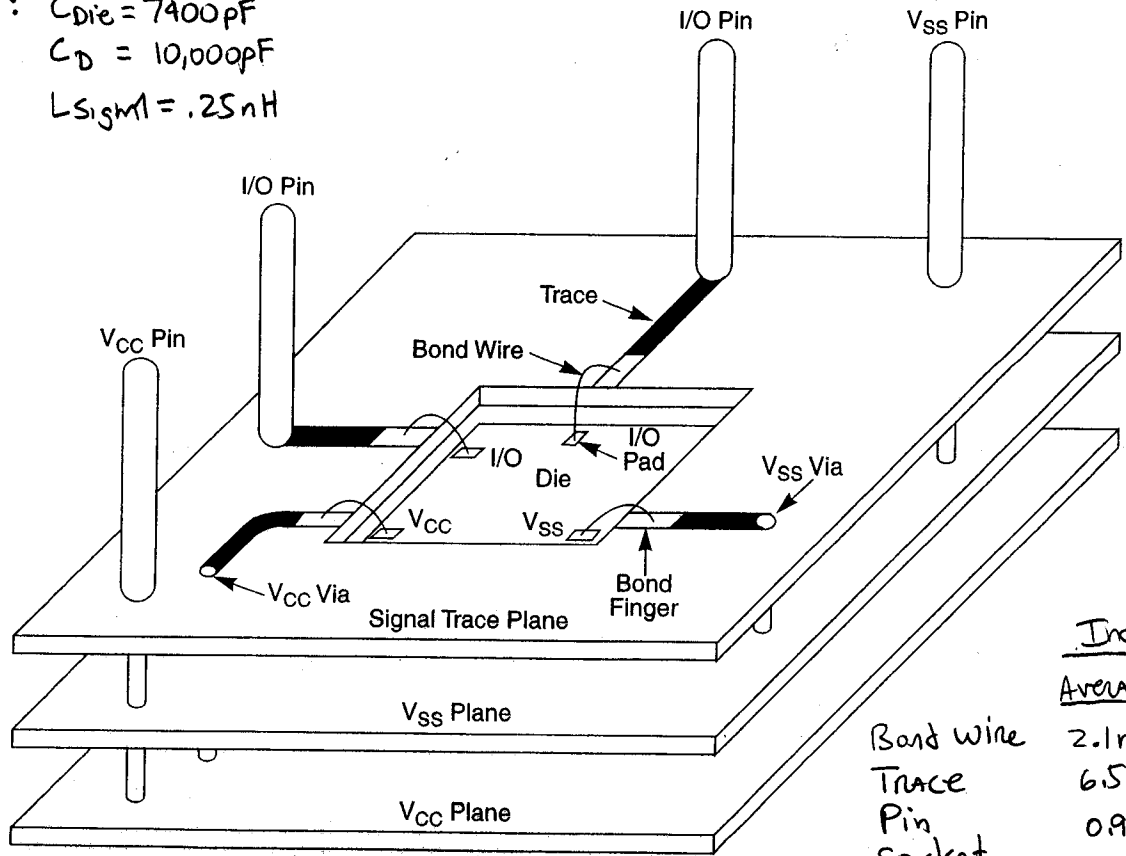
For i486: C_{die} = 7400pF
 C_D = 10,000pF
 L_{signal} = .25nH



Simplified view of the multilayer PGA

	Inductance	
	Average	MAX
Bond Wire	2.1nH	2.7nH
Trace	6.5nH	11.4nH
Pin socket	0.9nH	1.4nH
<u>L_{eff}</u>	<u>4nH</u>	<u>4nH</u>
	13.5nH	19.5nH

- Simultaneous output buffers

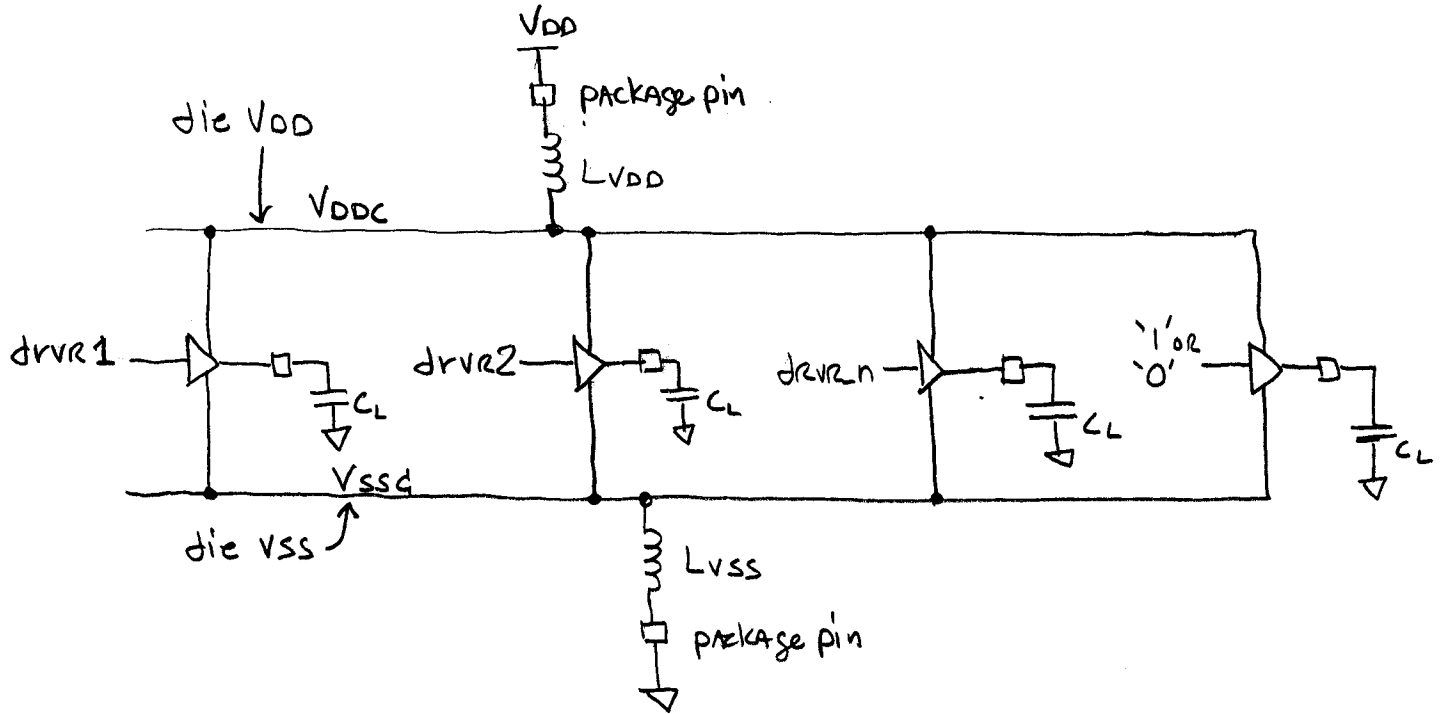

- An SDO situation occurs when several drivers switch at once. The worst case is when all drivers switch towards the same level. $0000_H \rightarrow FFFF_H \rightarrow 0000_H$

- The current path for all drivers is shared at the package pins through some inductance.

- When the outputs switch, the transient current creates a voltage across L_{VSS} or L_{VDD} . This voltage is:

$$V_L = L \left(\frac{di}{dt} \right) \cdot n$$

V_L = voltage across inductor

L = inductance in current path


di = instantaneous current drawn

dt = rise or fall time of output

n = number of output drivers switching to same level

if $L = 15nH$
 load is 50Ω , capacitive
 $di = 100mA$ (SV system)
 $dt = 1ns$
 $V_L = 1.5V!$

 
- Resultant waveform is superimposed on quiet outputs by $V_{L_{VSS}}$ or $V_{L_{VDD}}$.



- V_{DD} droop is usually less of an issue because of greater V_H noise immunity levels


These internal perturbations can cause malfunctions:

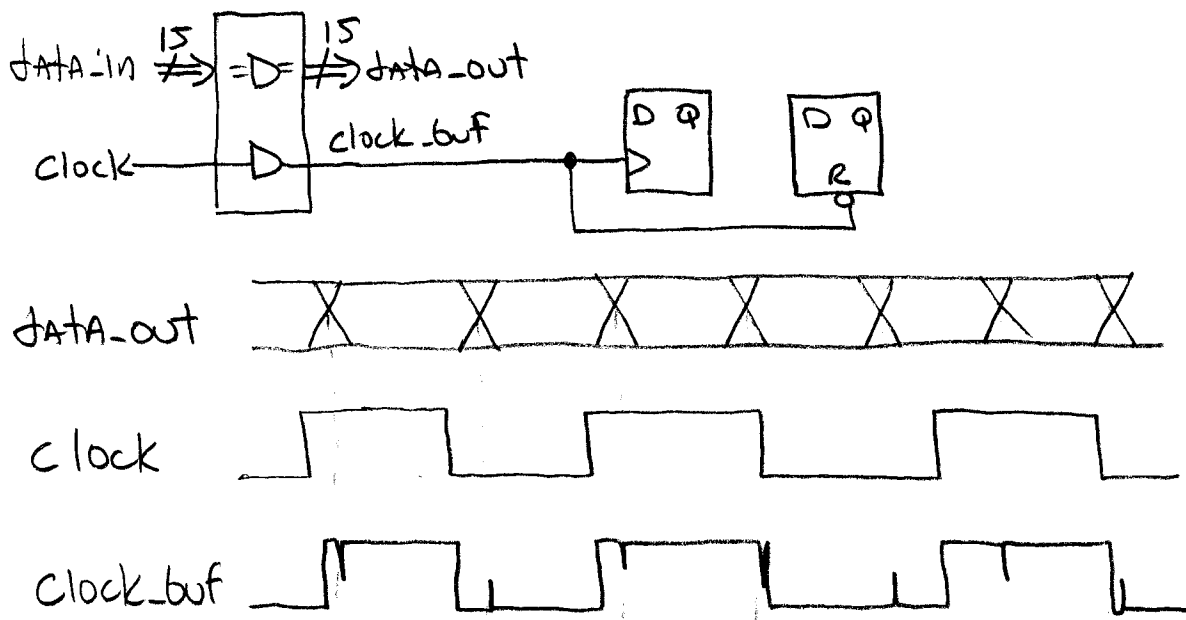- glitching outputs
- increased propagation delays
- false triggering due to dynamic threshold shift





- Glitching outputs to asynchronous inputs

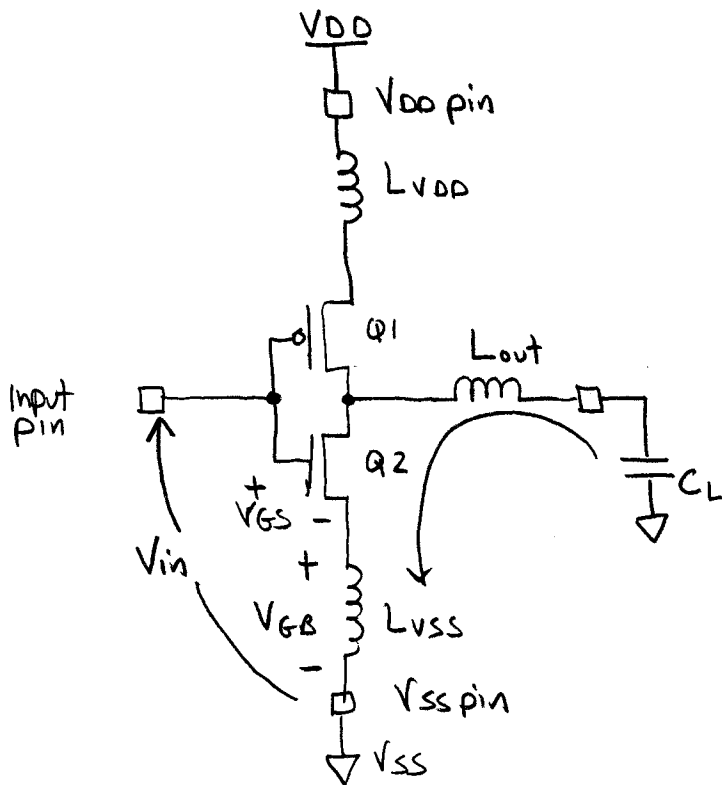- Increased propagation delay can occur if SSO scenario occurs because output buffer current starving



- In the case where Q2 is turning on, the ground bounce voltage "VGB" is subtracted from Vin thus lowering VGS. Thus $V_{DS(on)}$ increases which reduces the rate at which the output voltage can change. This effectively increases t_{pd} .

  
- Dynamic threshold shifting causes input signals to be interpreted incorrectly.




- The ground bounce voltage effectively shifts the input threshold of the input buffer momentarily.

Solutions to the SSO problem


- Reduce L , reduce di/dt
- Reducing L helps but not as much as expected.
- Reducing L also increases the current available to the output buffer when switching. This offsets the improvement somewhat.
- Center pin V_{DD} , V_{SS} (1 pin each) reduces ground bounce $\approx 10-15\%$.
- Reducing L_{VSS} , L_{VDD} by 1 order of magnitude reduces ground bounce by $\approx 30\%$
- This approach is most successful when used in conjunction with di/dt reduction.

 

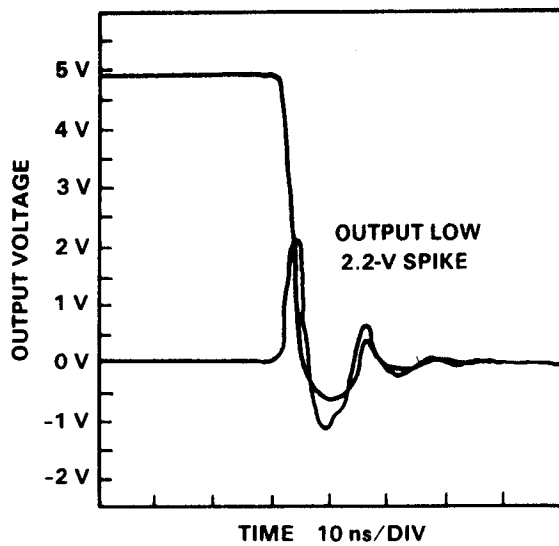Pin Inductance for a 24-Pin Package, End-Pin Configuration




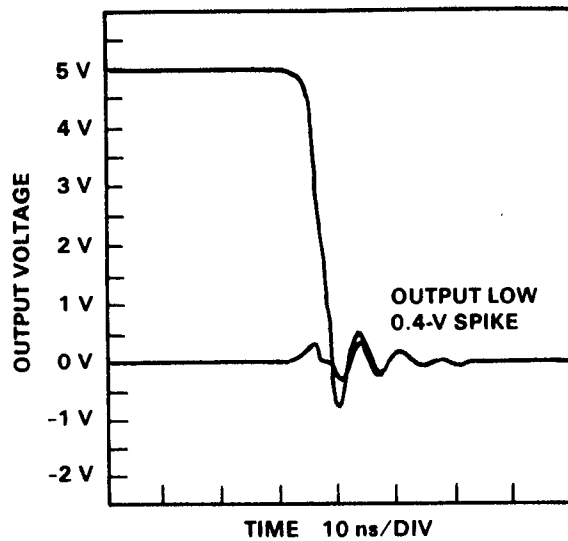Vendor A Advanced CMOS '244 20-Pin Plastic DIP,
1 V_{CC}/1 GND, End-Pin Package



NOTE: Ground looping was not taken into account.

 
Texas Instruments 'AC11244 24-Pin Plastic DIP,
2 V_{CC}/4 GND, Center-Pin Package




Flow-Through Pinout Architecture for an 'AC11240 Device

Output Edge Rate Control

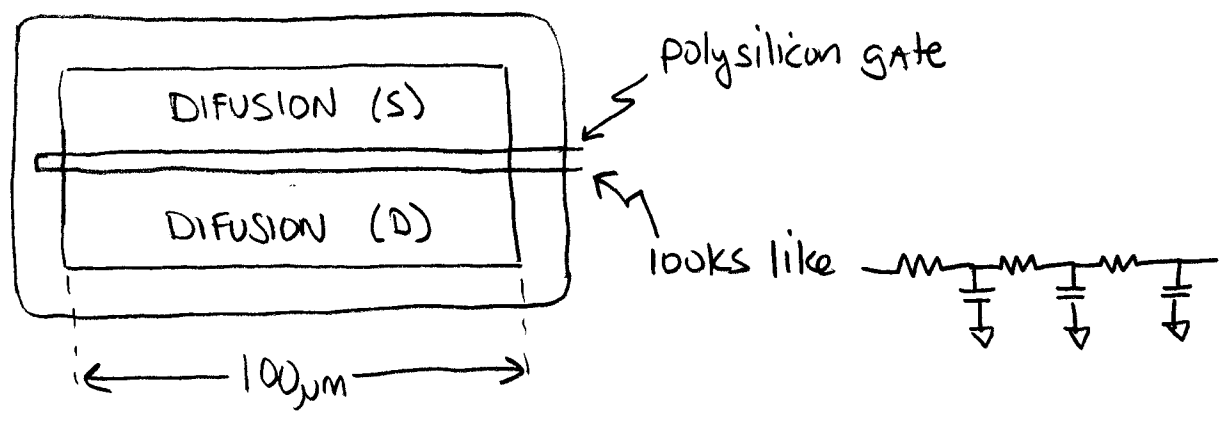- Addresses di/dt issue
- Gradually turn output transistors on and off
- A staged turn-on buffer





 - uses distributed RC delay of polysilicon
- poly $20\Omega/\text{sq}$, $C'_{\text{gox}} \approx 3\text{fF}/\text{sq}$ (1.5nm CMOS)
- $RC \approx 0.06\text{ps}/\text{sq}^2$, For $w/L = 100 \Rightarrow RC = 600\text{ps}$
- TI distributed transistor solution (w/fast turn-off)




(b) DISTRIBUTED TRANSISTOR WITH ADDED PULL-DOWNS

-TI Solution cont'd

  

(b) SERPENTINE ARRANGEMENT

CMOS Transistor Gate Layout

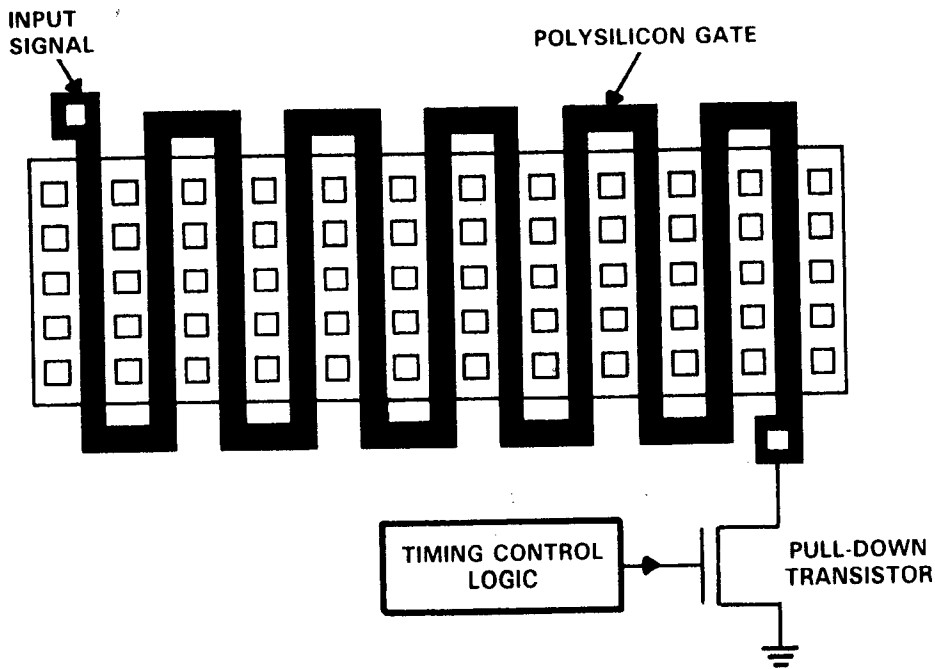

"Distributed" N-Channel with Gate Voltage Control

What can you do to limit SSO issues?

- Switch fewer outputs simultaneously
 - stagger outputs
 - Use serial interface?
- Avoid lumped capacitive load, push load away from IC with T-line
- Keep sensitive output pins near ground pin
- Lower V_{DD}
- encode data (starvation coding)
- use lowest strength buffer possible
- use series source terminations