

SECTION 1: SINUSOIDAL STEADY-STATE ANALYSIS

ENGR 202 – Electrical Fundamentals II


2

Sinusoids

Sinusoidal Signals

3

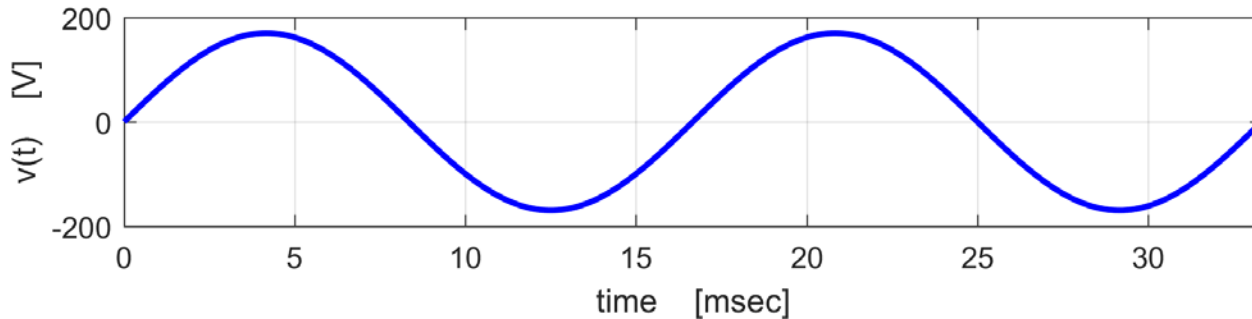- ***Sinusoidal*** signals are of particular interest in the field of electrical engineering



$$v(t) = V_p \cos(\omega t + \phi) = V_p \cos(2\pi \cdot f \cdot t + \phi)$$


- Sinusoidal signals defined by three parameters:
 - ▣ ***Amplitude:*** V_p
 - ▣ ***Frequency:*** ω or f
 - ▣ ***Phase:*** ϕ

Amplitude

4

- **Amplitude** of a sinusoid is its **peak** voltage, V_p
- **Peak-to-peak voltage**, V_{pp} , is twice the amplitude
 - ▣ $V_{pp} = 2V_p$
 - ▣ $V_{pp} = V_{max} - V_{min}$
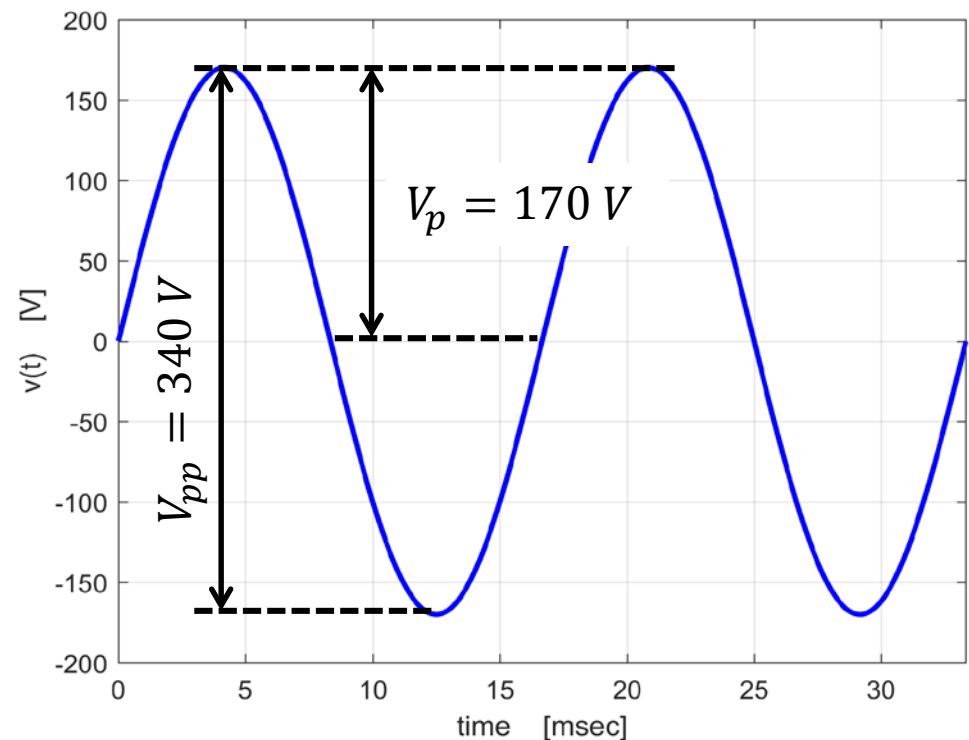
$$v(t) = V_p \cdot \sin(\omega t + \phi) = V_p \cdot \sin(2\pi f t + \phi)$$



Frequency

5

- **Period (T)**

- ▣ Duration of one cycle

- **Frequency (f)**

- ▣ Number of periods per second

$$f = \frac{1}{T}$$


- **Ordinary frequency, f**

- ▣ Units: hertz (Hz), sec^{-1} , cycles/sec

- **Angular frequency, ω**

- ▣ Units: rad/sec
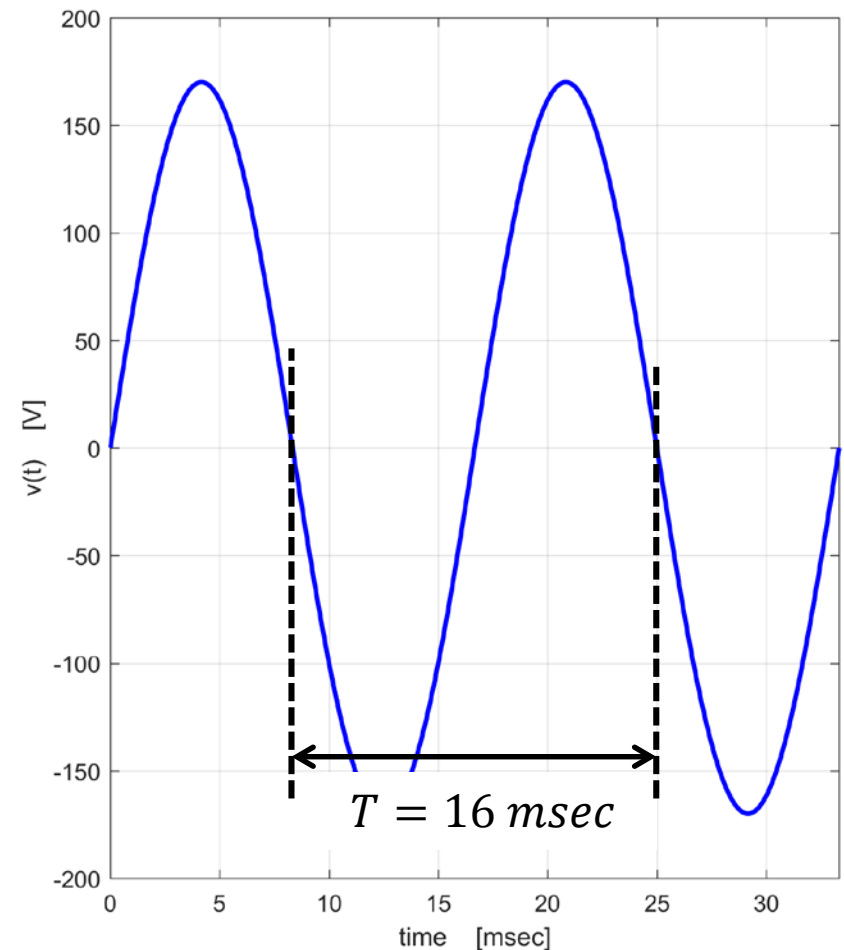
$$\omega = 2\pi f, \quad f = \frac{\omega}{2\pi}$$



Phase

6

□ **Phase**

- Angular constant in signal expression, ϕ

$$v(t) = V_p \sin(\omega t + \phi)$$

□ Requires a time reference

- Interested in relative, not absolute, phase


□ Here,

- $v_1(t)$ leads $v_2(t)$
- $v_2(t)$ lags $v_1(t)$

□ Units: radians

- Not technically correct, but OK to express in degrees, e.g.:

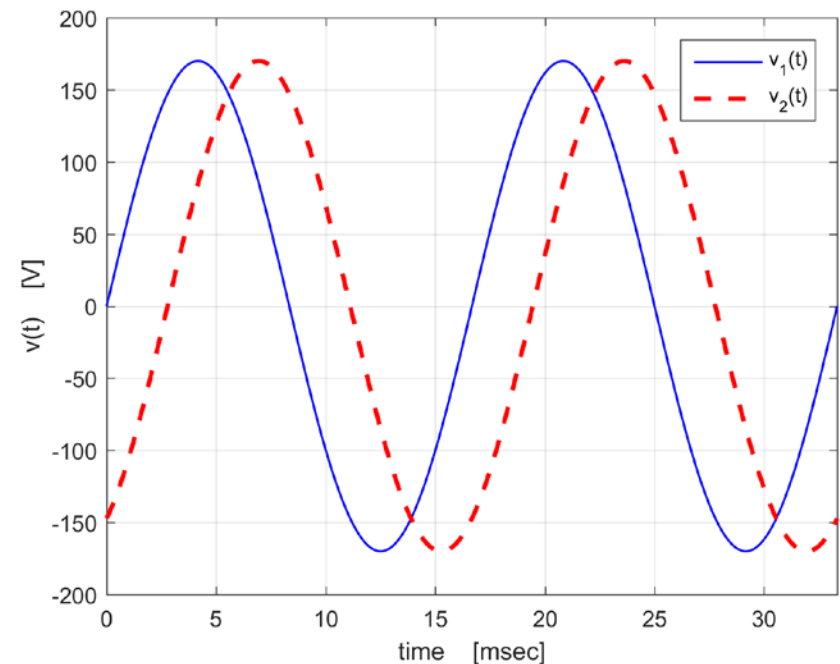
$$v(t) = 170 \text{ V} \sin(2\pi \cdot 60\text{Hz} \cdot t + 34^\circ)$$



Sinusoidal Steady-State Analysis

7

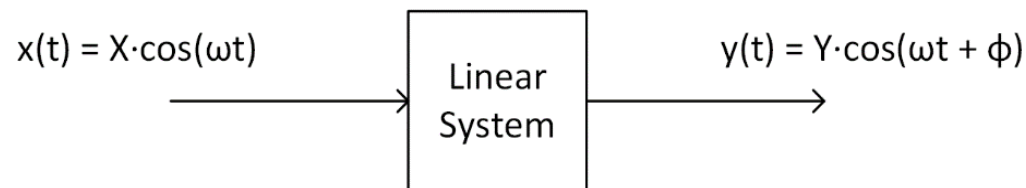- Often interested in the response of linear systems to ***sinusoidal inputs***
 - ▣ Voltages and currents in electrical systems
 - ▣ Forces, torques, velocities, etc. in mechanical systems
- For ***linear systems*** excited by a sinusoidal input
 - ▣ Output is sinusoidal
 - ***Same frequency***
 - In general, ***different amplitude***
 - In general, ***different phase***



- We can simplify the analysis of linear systems by using ***phasor representation*** of sinusoids

Phasors

8

□ **Phasor**

- A **complex number** representing the **amplitude** and **phase** of a sinusoidal signal
- Frequency is not included
 - Remains constant and is accounted for separately
 - System characteristics (frequency-dependent) evaluated at the frequency of interest as first step in the analysis

□ Phasors are **complex numbers**

- Before applying phasors to the analysis of electrical circuits, we'll first review the properties of complex numbers

9

Complex Numbers

Complex Numbers

10

- A complex number can be represented as

$$z = x + jy$$

- x : real part (a real number)
 - y : imaginary part (a real number)
 - $j = \sqrt{-1}$ is the imaginary unit
- Complex numbers can be represented three ways:
 - **Cartesian** form: $z = x + jy$
 - **Polar** form: $z = r\angle\phi$
 - **Exponential** form: $z = re^{j\phi}$

Complex Numbers as Vectors


11

- A complex number can be represented as a ***vector in the complex plane***
- Complex plane
 - ▣ ***Real axis*** – horizontal
 - ▣ ***Imaginary axis*** – vertical
- A vector from the origin to z
 - ▣ Real part, x
 - ▣ Imaginary part, y

$$z = x + jy$$

- ▣ Vector has a ***magnitude***, r
- ▣ And an ***angle***, θ

$$z = r \angle \theta$$

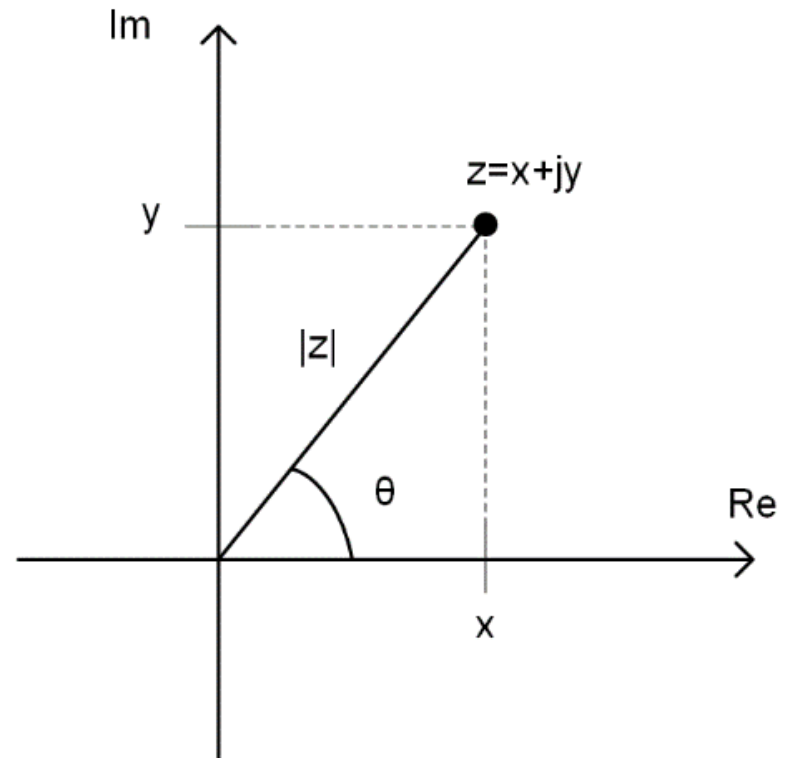

Cartesian Form \leftrightarrow Polar Form

12

□ Cartesian form \rightarrow Polar form

$$z = x + jy = r\angle\theta$$

$$r = |z| = \sqrt{x^2 + y^2}$$


$$\theta = \arg(z) = \angle z$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right)$$

□ Polar form \rightarrow Cartesian form

$$x = r \cos(\theta)$$

$$y = r \sin(\theta)$$

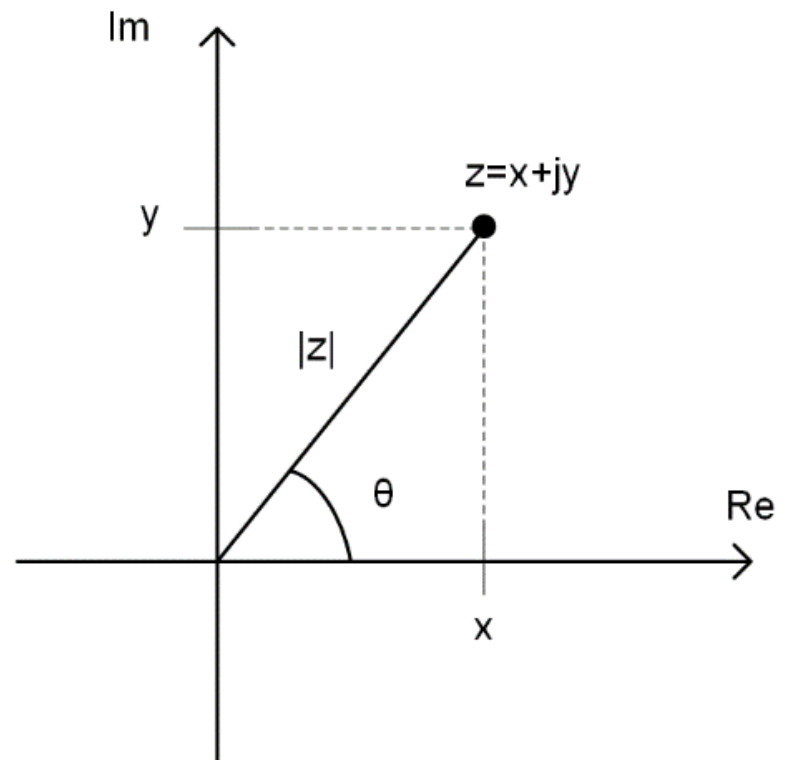

Complex Numbers – Addition/Subtraction

13

- ***Addition and subtraction*** of complex numbers
 - ▣ Best done in ***Cartesian*** form
 - ▣ Real parts add/subtract
 - ▣ Imaginary parts add/subtract
- For example:

$$z_1 = x_1 + jy_1$$

$$z_2 = x_2 + jy_2$$

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Complex Numbers – Multiplication/Division

14

- ***Multiplication and division*** of complex numbers
 - ▣ Best done in ***polar*** form
 - ▣ Magnitudes multiply/divide
 - ▣ Angles add/subtract
- For example:

$$z_1 = r_1 \angle \theta_1$$

$$z_2 = r_2 \angle \theta_2$$

$$z_1 \cdot z_2 = r_1 r_2 \angle (\theta_1 + \theta_2)$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

Complex Conjugate

15

- **Conjugate** of a complex number
 - ▣ Number that results from ***negating the imaginary part***


$$z = x + jy$$

$$z^* = x - jy$$

- ▣ Or, equivalently, from ***negating the angle***

$$z = r\angle\theta$$

$$z^* = r\angle -\theta$$

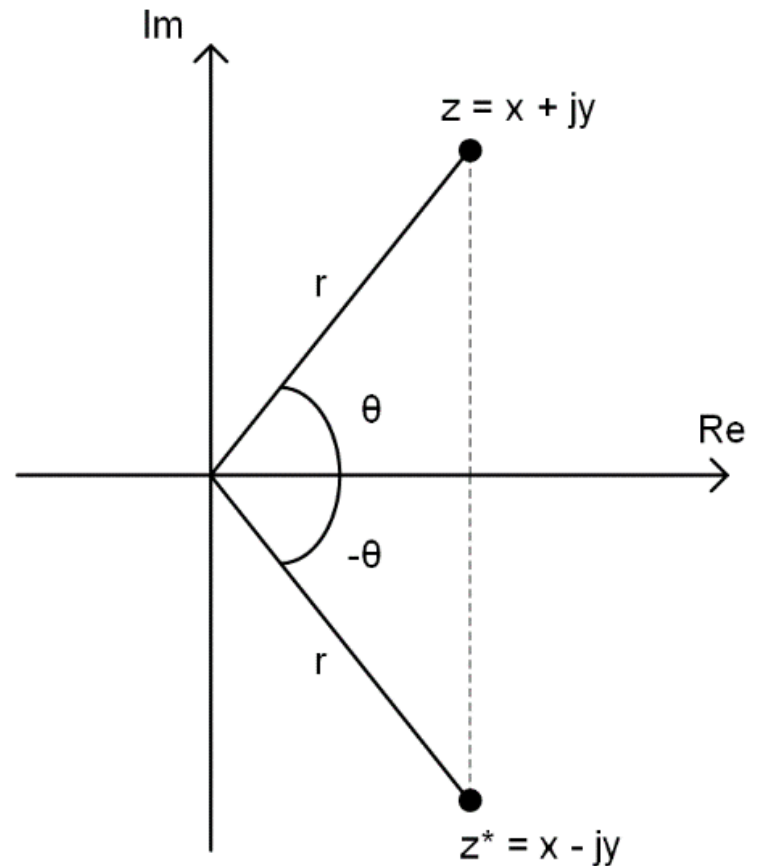

Complex Fractions

16

- Multiplying a number by its complex conjugate yields the ***squared magnitude*** of that number

- ▣ ***A real number***

$$z \cdot z^* = (x + jy)(x - jy) = x^2 + y^2$$

$$z \cdot z^* = r\angle\theta \cdot r\angle-\theta = r^2\angle\theta - \theta = r^2$$

- ***Rationalizing the denominator*** of a complex fraction:

- ▣ Multiply numerator and denominator by the ***complex conjugate of the denominator***

$$z = \frac{x_1 + jy_1}{x_2 + jy_2} \cdot \frac{x_2 - jy_2}{x_2 - jy_2}$$

$$z = \frac{x_1x_2 + y_1y_2}{x_2^2 + y_2^2} + j \frac{(x_2y_1 - x_1y_2)}{x_2^2 + y_2^2}$$

Complex Fractions

17

- **Fractions** or **ratios** are, of course, simply division
 - ▣ Very common form, so worth emphasizing
- **Magnitude** of a ratio of complex numbers

$$z = \frac{z_1}{z_2} \rightarrow |z| = \frac{|z_1|}{|z_2|}$$

- **Angle** of a ratio of complex numbers

$$z = \frac{z_1}{z_2} \rightarrow \angle z = \angle z_1 - \angle z_2$$

-
- **Calculators and complex numbers**
 - ▣ Manipulation of complex numbers by hand is tedious and error-prone
 - ▣ Your calculators can perform complex arithmetic
 - ▣ They will operate in both Cartesian and polar form, and will convert between the two
 - ▣ Learn to use them – correctly

18

Phasors

Euler's Identity

19

- Fundamental to phasor notation is ***Euler's identity***:

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

where j is the imaginary unit, and ω is angular frequency

- It follows that

$$\cos(\omega t) = \operatorname{Re}\{e^{j\omega t}\}$$

$$\sin(\omega t) = \operatorname{Im}\{e^{j\omega t}\}$$

and

$$\cos(\omega t) = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$$\sin(\omega t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

Phasors

20

- Consider a sinusoidal voltage

$$v(t) = V_p \cos(\omega t + \phi)$$

- Using Euler's identity, we can represent this as

$$v(t) = \text{Re}\{V_p e^{j(\omega t + \phi)}\} = \text{Re}\{V_p e^{j\phi} e^{j\omega t}\}$$

where

- V_p represents magnitude
 - $e^{j\phi}$ represents phase
 - $e^{j\omega t}$ represents a sinusoid of frequency ω
- Grouping the first two terms together, we have

$$v(t) = \text{Re}\{\mathbf{V} e^{j\omega t}\}$$

where \mathbf{V} is the phasor representation of $v(t)$

Phasors


21

$$v(t) = \text{Re}\{\mathbf{V}e^{j\omega t}\}$$

- The phasor representation of $v(t)$

$$\mathbf{V} = V_p e^{j\phi}$$

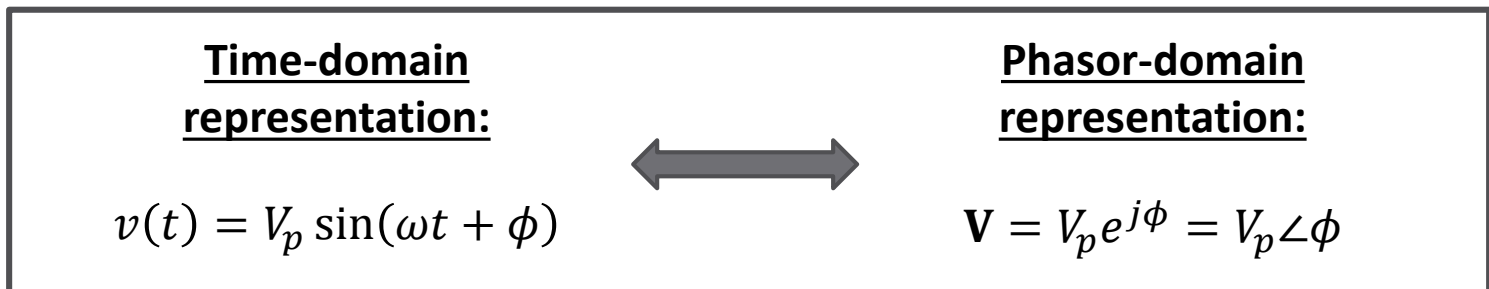- A representation of magnitude and phase only
- Time-harmonic portion ($e^{j\omega t}$) has been dropped



- Phasors greatly simplify sinusoidal steady-state analysis
 - Messy trigonometric functions are eliminated
 - Differentiation and integration transformed to algebraic operations

Voltage & Current in the Phasor Domain

22

- We will use phasors to simplify analysis of electrical circuits
 - ▣ Need an understanding of electrical component behavior in the phasor domain
 - ▣ Relationships between **voltage phasors** and **current phasors** for Rs, Ls, and Cs

□ **Resistor**

- ▣ Voltage across a resistor given by

$$v(t) = i(t)R$$

$$i(t) = I_p \cos(\omega t + \phi)$$


- ▣ Converting to phasor form

$$\mathbf{V} = (I_p e^{j\phi})R$$

$$\mathbf{V} = \mathbf{I}R$$

$$\mathbf{I} = \frac{\mathbf{V}}{R}$$

- ▣ **Ohm's law** in phasor form

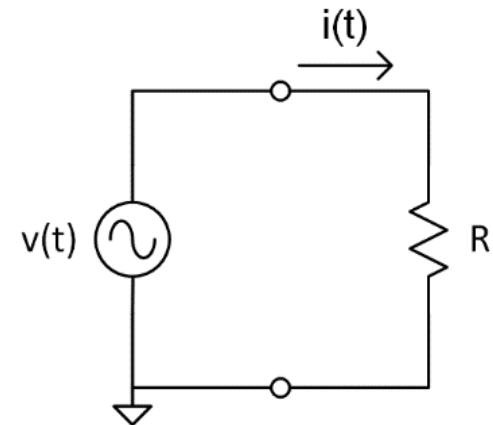

V-I Relationships in the Phasor Domain

23

□ **Capacitor**

- Current through the capacitor given by

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = C \frac{d}{dt} [V_p \cos(\omega t + \phi)]$$

$$i(t) = -\omega C V_p \sin(\omega t + \phi)$$

- Applying a trig identity:


$$-\sin(A) = \cos(A + 90^\circ)$$

gives

$$i(t) = \omega C V_p \cos(\omega t + \phi + 90^\circ)$$

- Converting to **phasor form**
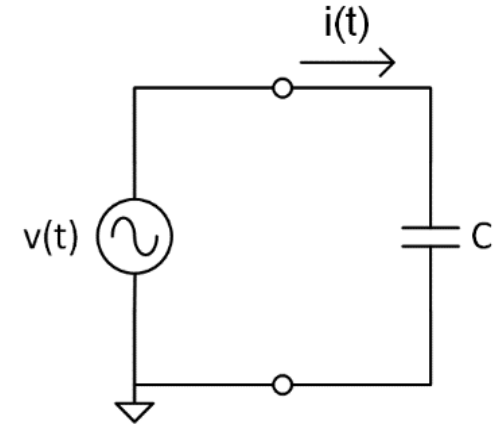
$$\mathbf{I} = \omega C V_p e^{j(\phi + 90^\circ)} = \omega C V_p e^{j\phi} e^{j90^\circ}$$



V-I Relationships - Capacitor

24

□ Current phasor

$$\mathbf{I} = \omega C V_p e^{j(\phi + 90^\circ)} = \omega C V_p e^{j\phi} e^{j90^\circ}$$

▣ Voltage phasor is

$$\mathbf{V} = V_p e^{j\phi}$$


so

$$\mathbf{I} = \omega C \mathbf{V} e^{j90^\circ}$$

▣ Recognizing that $e^{j90^\circ} = j$, we have

$$\mathbf{I} = j\omega C \mathbf{V}$$
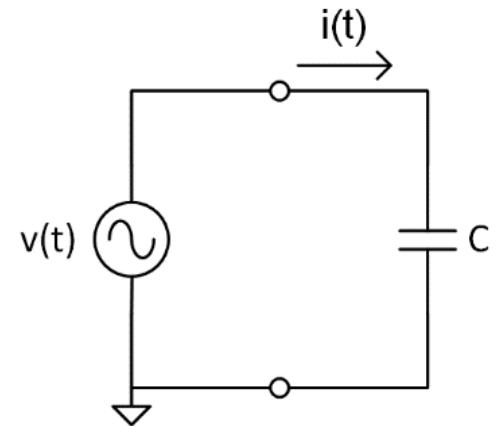
$$\mathbf{V} = \frac{1}{j\omega C} \mathbf{I}$$



V-I Relationships - Inductor

25


□ **Inductor**

- ▣ Voltage across an inductor given by

$$v(t) = L \frac{di}{dt}$$

$$v(t) = L \frac{d}{dt} [I_p \cos(\omega t + \phi)]$$
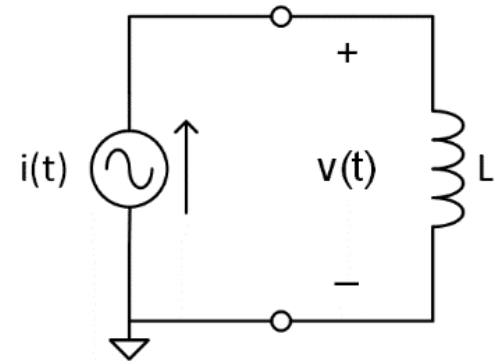
$$v(t) = -\omega L I_p \sin(\omega t + \phi) = \omega L I_p \cos(\omega t + \phi + 90^\circ)$$



- ▣ Converting to **phasor form**

$$\mathbf{V} = \omega L I_p e^{j(\phi + 90^\circ)} = \omega L I_p e^{j\phi} e^{j90^\circ}$$

- ▣ Again, recognizing that $e^{j90^\circ} = j$, gives

$$\mathbf{V} = j\omega L \mathbf{I}$$

$$\mathbf{I} = \frac{1}{j\omega L} \mathbf{V}$$

26

Impedance

Impedance

27

- For resistors, Ohm's law gives the ratio of the **voltage phasor** to the **current phasor** as

$$\frac{V}{I} = R$$

- R is, of course, **resistance**
 - A special case of **impedance**
- **Impedance, Z**

$$Z = \frac{V}{I}$$

- The **ratio** of the **voltage phasor** to the **current phasor** for a component or network
- Units: ohms (Ω)
- In general, complex-valued

Impedance

28

- **Resistor impedance:**

$$Z = \frac{V}{I} = R$$

- **Capacitor impedance:**

$$Z = \frac{V}{I} = \frac{1}{j\omega C}$$

- **Inductor impedance:**

$$Z = \frac{V}{I} = j\omega L$$

- In general, **Ohm's law** can be applied to any component or network in the **phasor domain**

$$V = IZ$$

$$I = \frac{V}{Z}$$

29

Capacitor Impedance


Capacitor Impedance

30

$$Z = \frac{1}{j\omega C} = \frac{1}{\omega C} e^{-j90^\circ}$$

$$\mathbf{V} = \mathbf{I}Z = \frac{\mathbf{I}}{\omega C} e^{-j90^\circ}$$
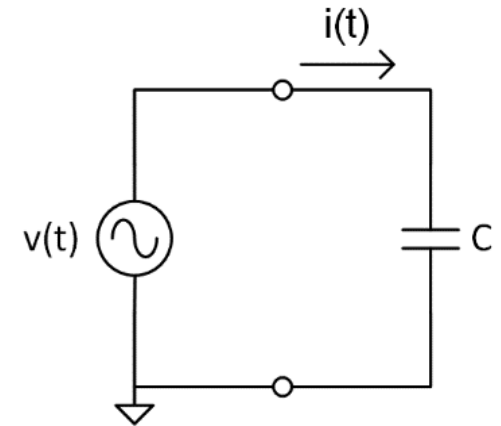
$$\mathbf{I} = \omega C \mathbf{V} e^{j90^\circ}$$



- In the time domain, this translates to

$$v(t) = V_p \cos(\omega t + \phi)$$



$$i(t) = V_p \omega C \cos(\omega t + \phi + 90^\circ)$$

- ***Current through a capacitor leads the voltage across a capacitor by 90°***

Capacitor Impedance – Phasor Diagram

31

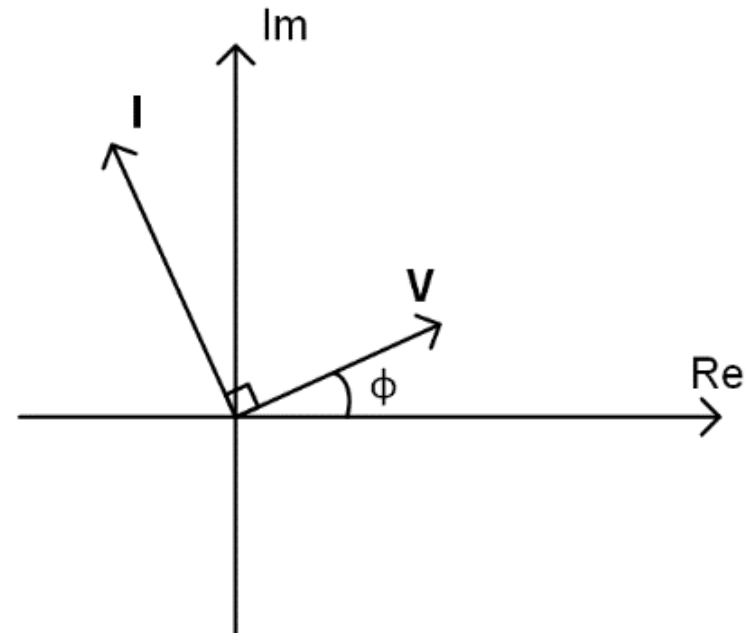
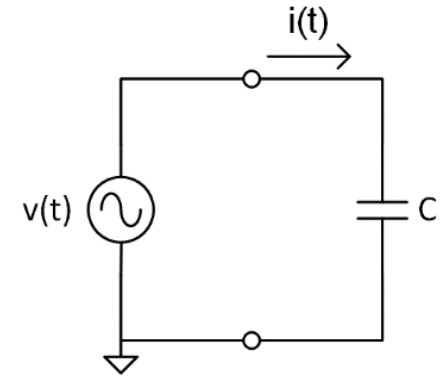
- **Phasor diagram** for a capacitor
 - ▣ Voltage and current phasors drawn as vectors in the complex plane
 - ▣ Current always leads voltage by 90°



Capacitor Impedance – Time Domain


32

- Current leads voltage by 90°

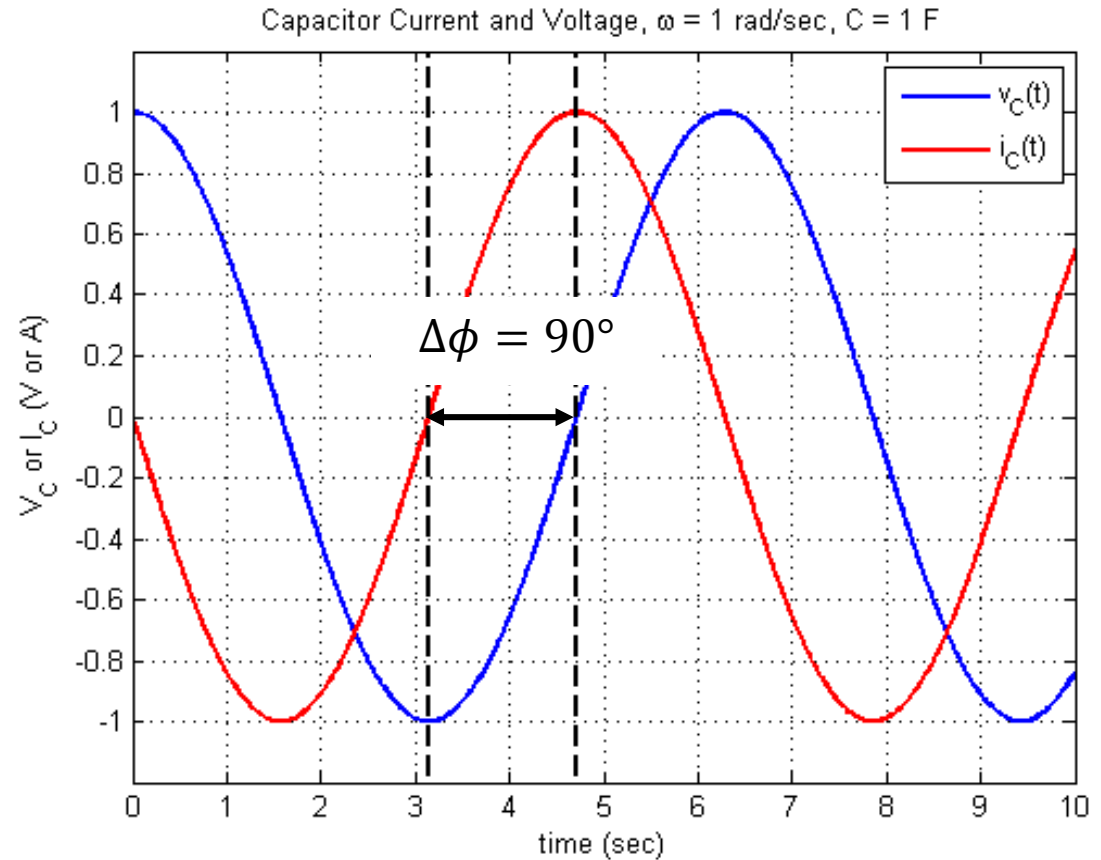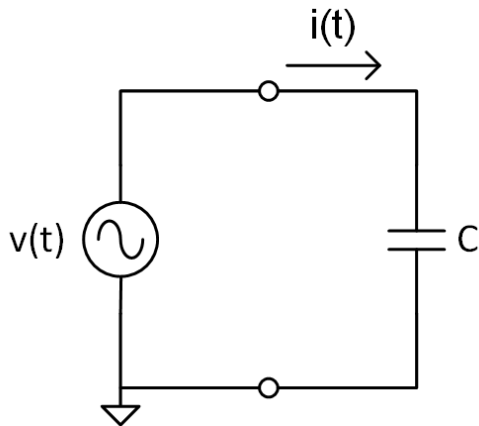

Capacitor Impedance – Frequency Domain

33

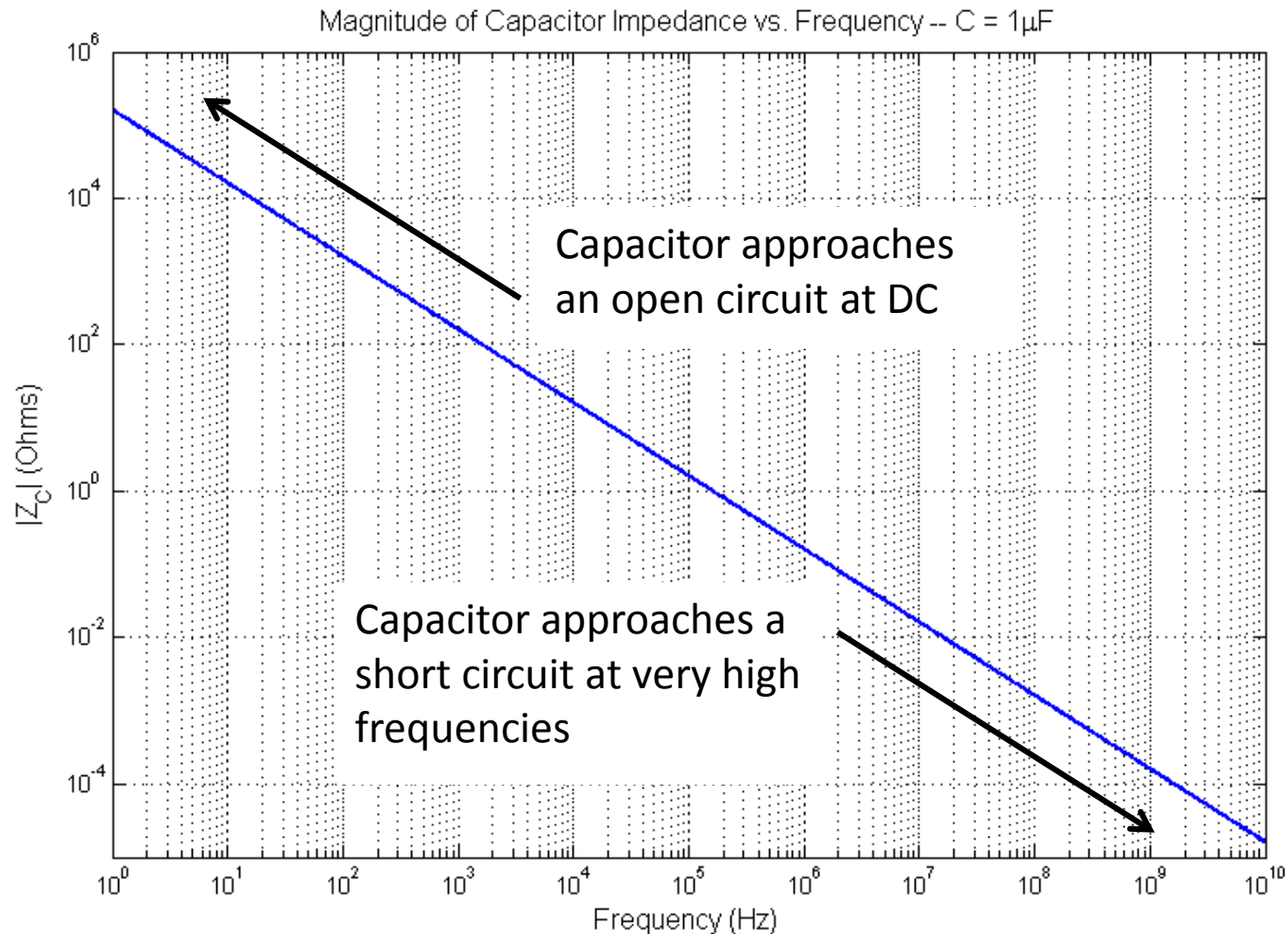

34

Inductor Impedance

Inductor Impedance

35

$$Z = j\omega L = \omega L e^{j90^\circ}$$

$$\mathbf{V} = \mathbf{I}Z = \mathbf{I}\omega L e^{j90^\circ}$$


$$\mathbf{I} = \frac{\mathbf{V}}{\omega L} e^{-j90^\circ}$$

- In the time domain, this translates to

$$v(t) = V_p \cos(\omega t + \phi)$$

$$i(t) = \frac{V_p}{\omega L} \cos(\omega t + \phi - 90^\circ)$$


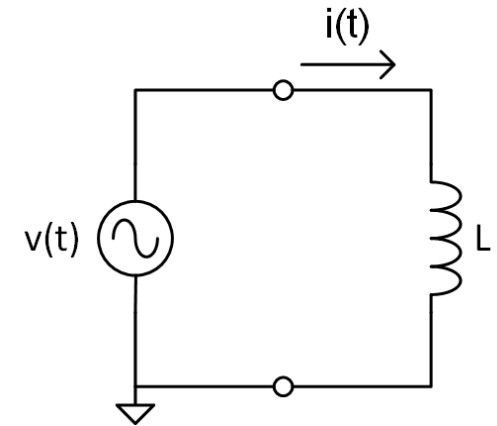
- ***Current through an inductor lags the voltage across an inductor by 90°***



Inductor Impedance – Phasor Diagram

36

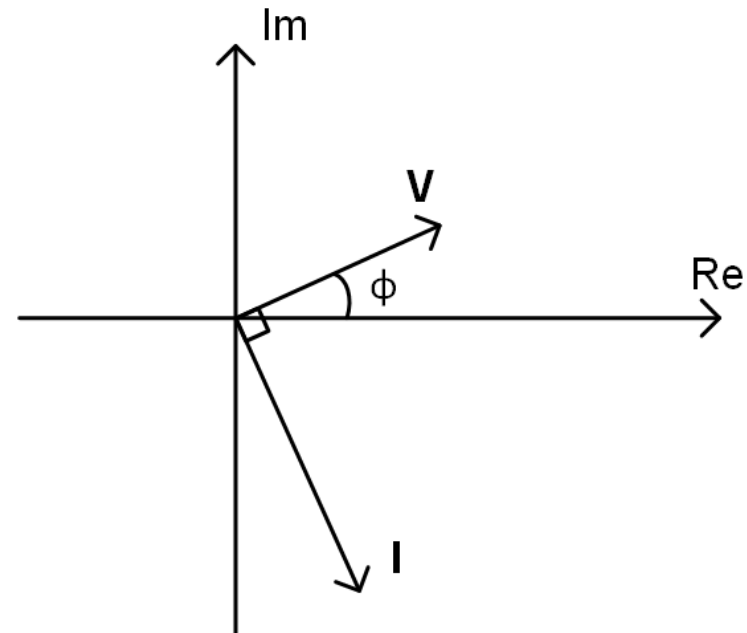
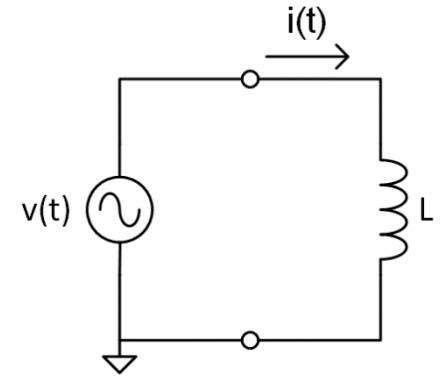
- ***Phasor diagram*** for an inductor
 - ▣ Voltage and current phasors drawn as vectors in the complex plane
 - ▣ Current always lags voltage by 90°



Inductor Impedance – Time Domain


37

- Current lags voltage by 90°

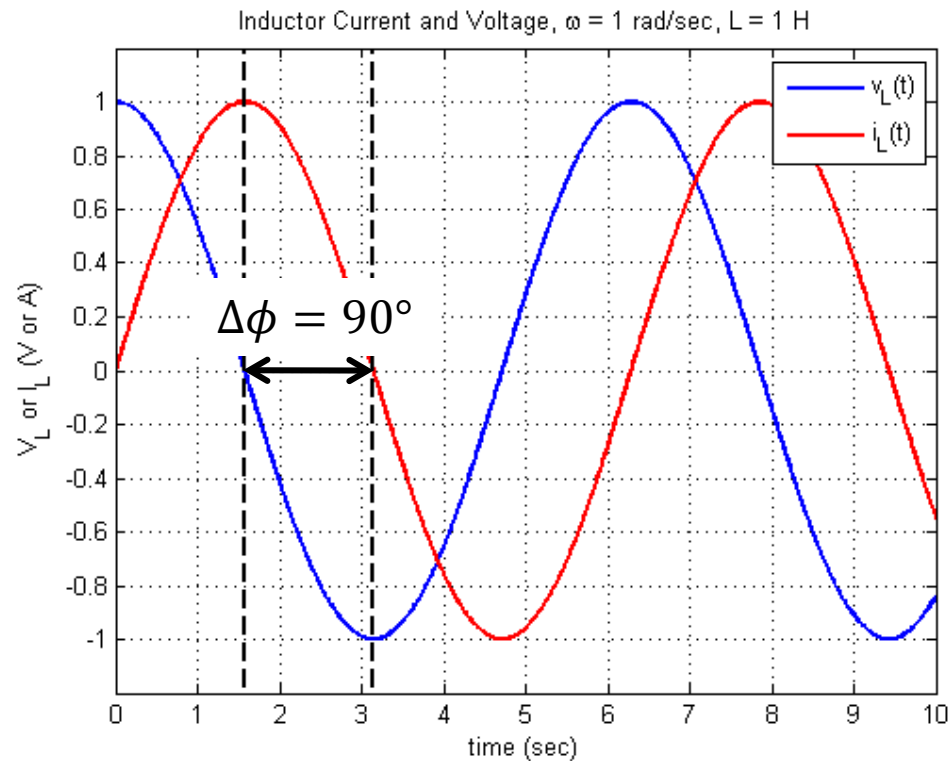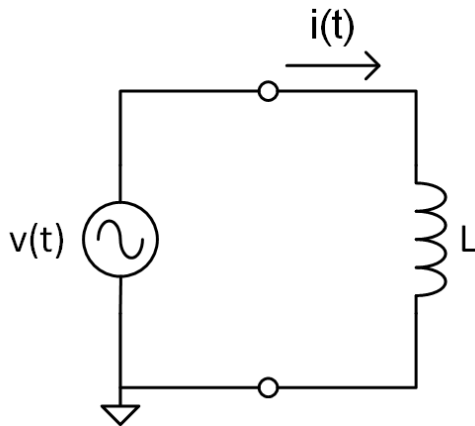

Inductor Impedance – Frequency Domain

38

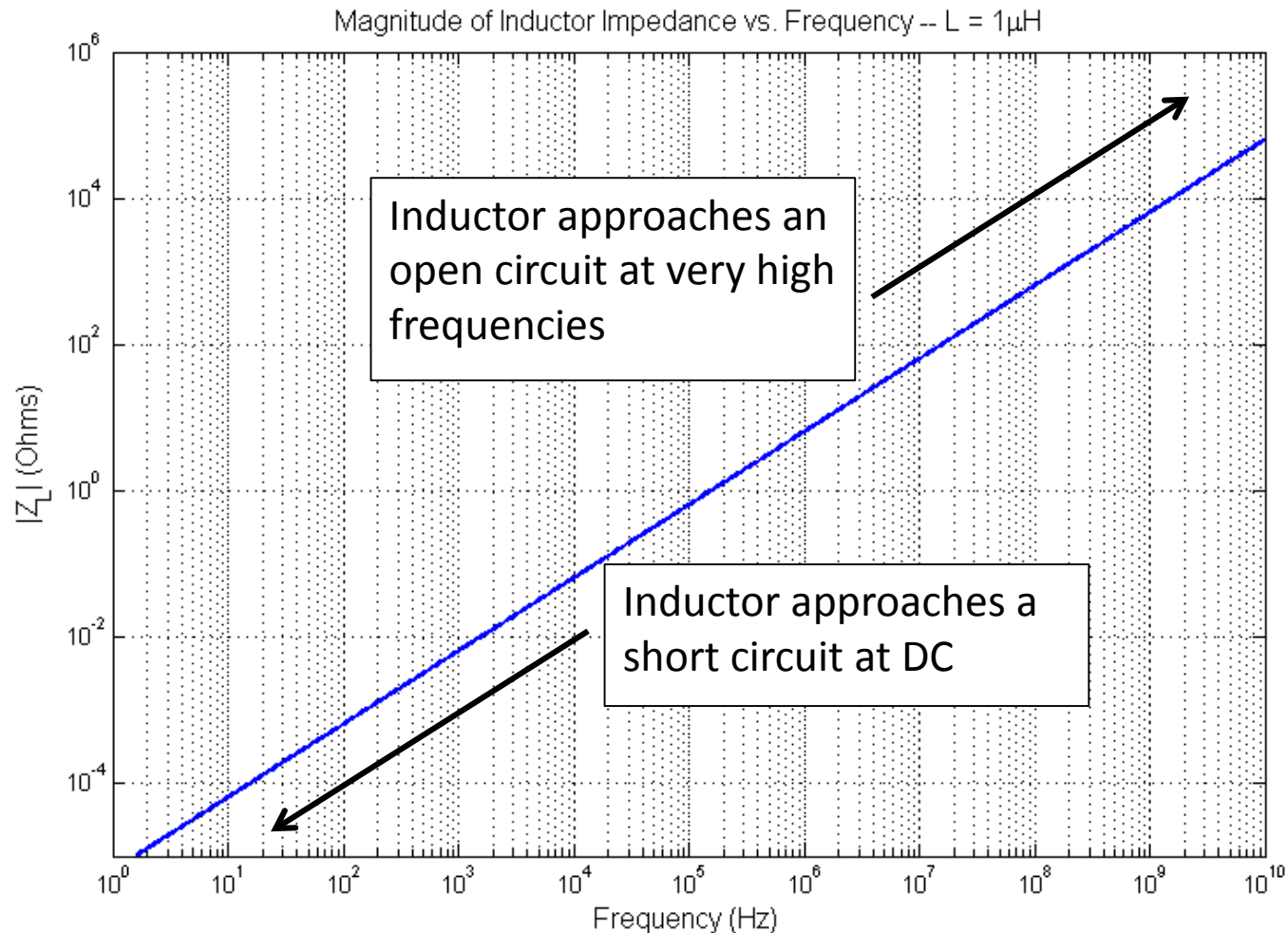

Summary

39

Capacitor

- ▣ Impedance:

$$Z_c = \frac{1}{j\omega C}$$

- ▣ V-I phase relationship:

Current leads voltage by 90°

$$v(t) = V_p \cos(\omega t)$$

$$i(t) = V_p \omega C \cos(\omega t + 90^\circ)$$

Inductor

- ▣ Impedance:

$$Z_L = j\omega L$$

- ▣ V-I phase relationship:

Current lags voltage by 90°

$$v(t) = V_p \cos(\omega t)$$

$$i(t) = \frac{V_p}{\omega L} \cos(\omega t - 90^\circ)$$

ELI the ICE Man


40

- Mnemonic for phase relation between current (I) and voltage (E) in inductors (L) and capacitors (C)

E L I

Voltage
leads
in an inductor


current

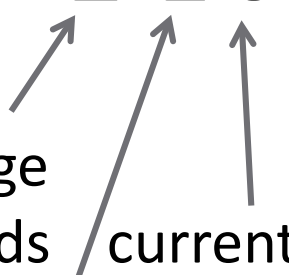

the **I C E** man

Current
leads
in a capacitor

voltage

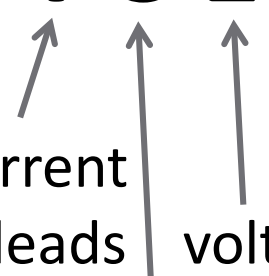

41 Impedance of Arbitrary Networks

Impedance

42

- So far, we've looked at impedance of individual components

- ***Resistors***

$$Z = R$$

- Purely real

- ***Capacitors***

$$Z = \frac{1}{j\omega C}$$

- Purely imaginary, ***purely reactive***

- ***Inductors***

$$Z = j\omega L$$

- Purely imaginary, ***purely reactive***

Impedance

43

- Also want to be able to characterize the impedance of electrical networks
 - ▣ Multiple components
 - ▣ Some resistive, some reactive
- In general, impedance is a complex value

$$Z = R + jX$$

where

- ▣ R is **resistance**
- ▣ X is **reactance**
- So, in ENGR 201 we dealt with impedance all along
 - ▣ **Resistance** is an impedance whose reactance (imaginary part) is zero
 - ▣ A **purely real** impedance

Reactance

44

- For **capacitor** and **inductors**, impedance is **purely reactive**
 - ▣ Resistive part is zero

$$Z_c = jX_c \quad \text{and} \quad Z_L = jX_L$$

where X_c is **capacitive reactance**

$$X_c = -\frac{1}{\omega C}$$

and X_L is **inductive reactance**

$$X_L = \omega L$$

- ▣ Note that **reactance** is a **real** quantity
 - It is the **imaginary part** of impedance
- ▣ Units of reactance: ohms (Ω)

Admittance

45

- **Admittance**, Y , is the inverse of impedance

$$Y = \frac{1}{Z} = G + jB$$

where

G is **conductance** – the real part

B is **susceptance** – the imaginary part

$$Y = \frac{1}{R + jX} = \left(\frac{R}{R^2 + X^2} \right) + j \left(\frac{-X}{R^2 + X^2} \right)$$

- **Conductance**

$$G = \frac{R}{R^2 + X^2}$$

- Note that $G \neq 1/R$ unless $X = 0$

- **Susceptance**


$$B = \frac{-X}{R^2 + X^2}$$

- Units of Y , G , and B : Siemens (S)

Impedance of Arbitrary Networks

46

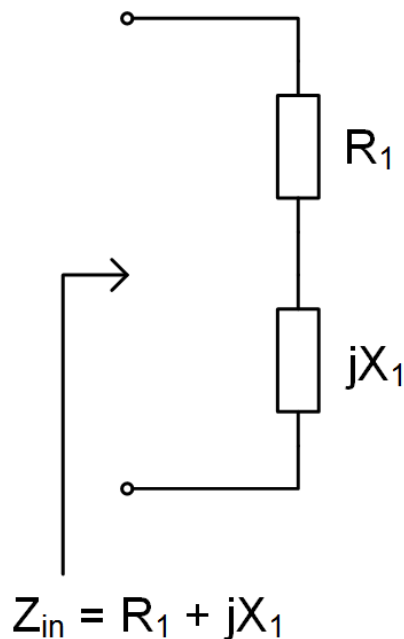- In general, the impedance of arbitrary networks may be both resistive and reactive



where

$$Z = R_1 + jX_1$$

$$Z = |Z| \angle \theta$$

$$|Z| = \sqrt{R_1^2 + X_1^2}$$


and

$$\theta = \tan^{-1} \left(\frac{X_1}{R_1} \right)$$

Impedances in Series

47

□ ***Impedances in series add***

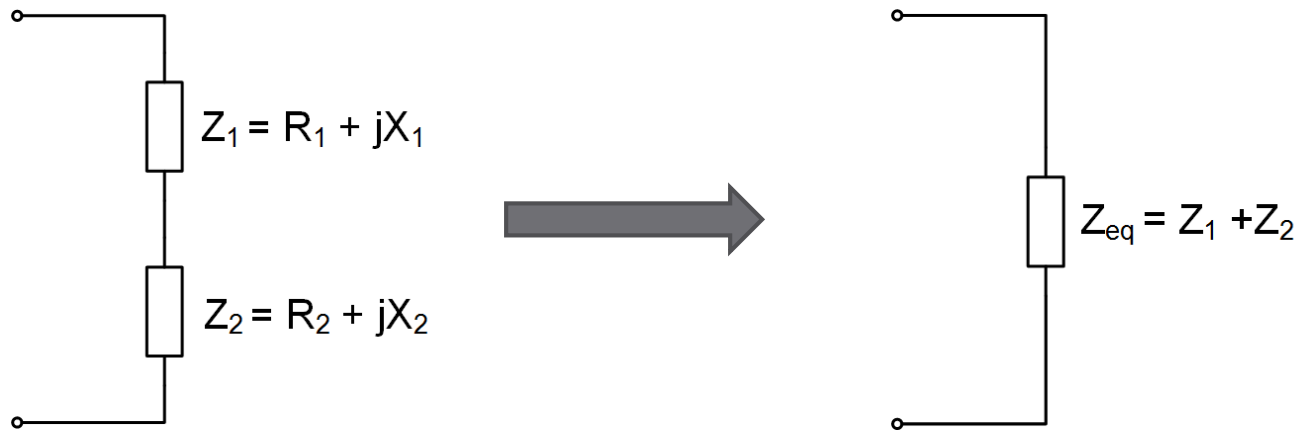


$$Z_{eq} = Z_1 + Z_2$$

$$Z_{eq} = (R_1 + R_2) + j(X_1 + X_2)$$

Impedances in Parallel

48

□ *Admittances in parallel add*

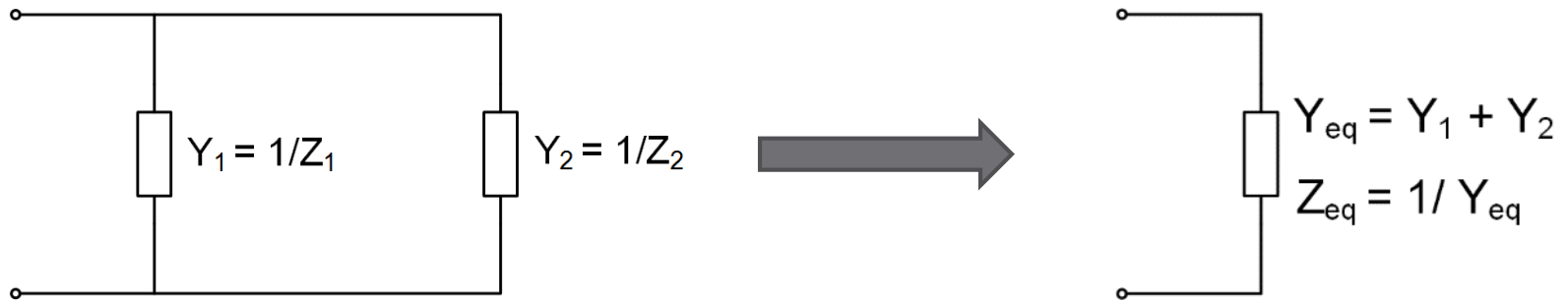

$$Y_{eq} = Y_1 + Y_2$$

$$Z_{eq} = \frac{1}{Y_{eq}} = \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right)^{-1}$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

49

Sinusoidal Steady-State Analysis

Sinusoidal Steady-State Analysis – Ex. 1

50

- Determine the current, $i(t)$

$$v_s(t) = 1 \text{ V} \cos(2\pi \cdot 1 \text{ MHz} \cdot t)$$

-
- First, convert the circuit to the **phasor domain**

- Express the source voltage as a phasor



$$\mathbf{V}_s = 1 \text{ V} \angle 0^\circ$$

- Evaluate impedances at 1 MHz

$$R = 10 \, \Omega$$

$$Z_c = \frac{1}{j\omega C} = -\frac{j}{2\pi \cdot 1 \text{ MHz} \cdot 10 \text{ nF}}$$

$$Z_c = -j15.9 \, \Omega$$

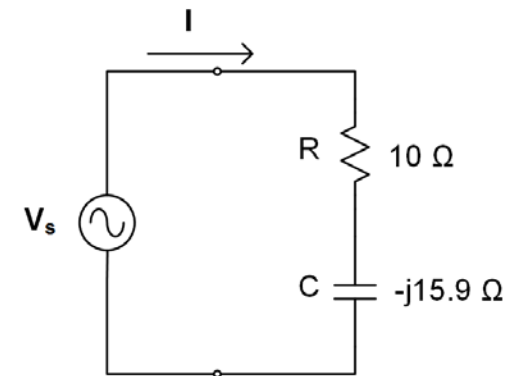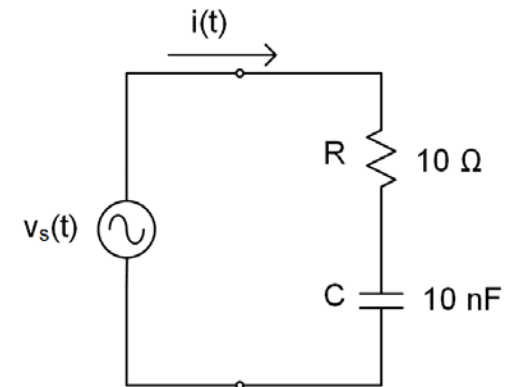

Sinusoidal Steady-State Analysis – Ex. 1

51

- The load impedance is

$$Z = R + jX_c = (10 - j15.9) \Omega$$

$$Z = 18.8 \angle -57.8^\circ \Omega$$


- Apply Ohm's law to calculate the current phasor

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{1 \text{ V} \angle 0^\circ}{18.8 \angle -57.8^\circ \Omega}$$

$$\mathbf{I} = 53.2 \angle 57.8^\circ \text{ mA}$$

- Finally, convert to the **time domain**

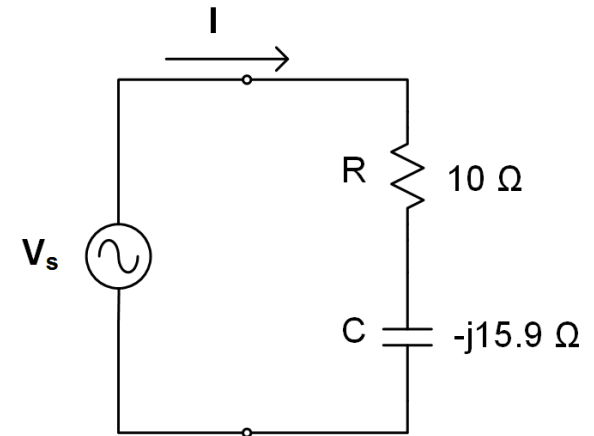
$$i(t) = 53.2 \text{ mA} \cos(2\pi \cdot 1\text{MHz} \cdot t + 57.8^\circ)$$



Sinusoidal Steady-State Analysis – Ex. 2

52

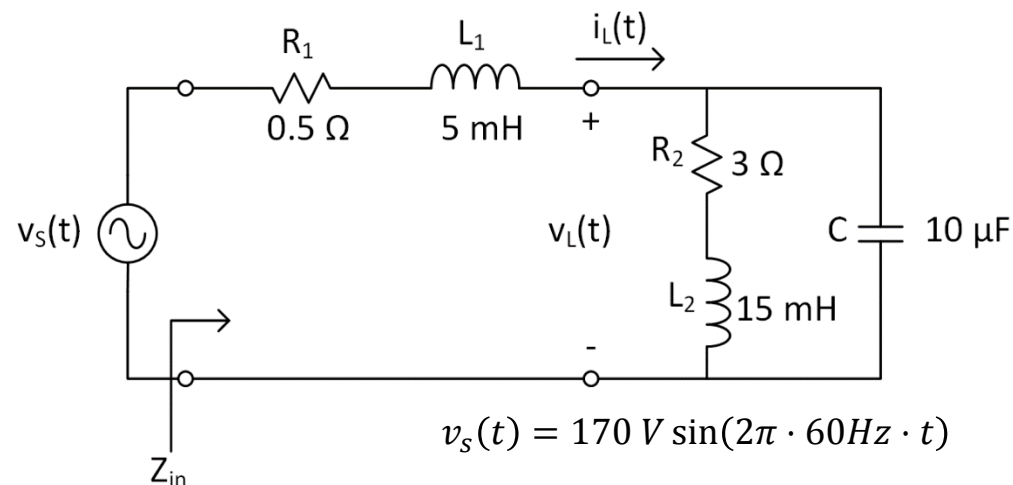- Consider the following circuit, modeling a source driving a load through a transmission line




- Determine:
 - ▣ The impedance, Z_{in} , at 60 Hz
 - ▣ Voltage across the load, $v_L(t)$
 - ▣ Current delivered to the load, $i_L(t)$

Sinusoidal Steady-State Analysis – Ex. 2

53

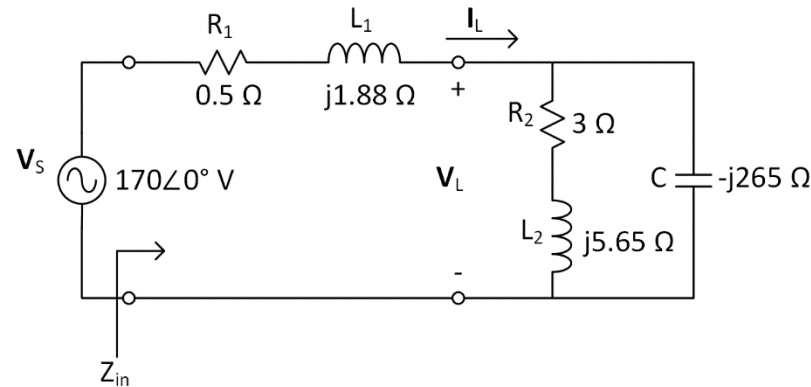- First, convert to the phasor domain and evaluate impedances at 60 Hz



- The line impedance is

$$Z_{line} = R_1 + j\omega L_1 = 0.5 + j1.88 \Omega$$

- The load impedance is

$$Z_{load} = (R_2 + j\omega L_2) \parallel \frac{1}{j\omega C} = (3 + j5.65 \Omega) \parallel -j265 \Omega$$

$$Z_{load} = \left(\frac{1}{3 + j5.65 \Omega} + \frac{1}{-j265 \Omega} \right)^{-1} = 3.13 + j5.74 \Omega$$

Sinusoidal Steady-State Analysis – Ex. 2

54

- The impedance seen by the source is

$$Z_{in} = Z_{line} + Z_{load}$$

$$Z_{in} = (0.5 + j1.88 \, \Omega) + (3.13 + j5.74 \, \Omega)$$

$$Z_{in} = 3.63 + j7.62 \, \Omega$$

- In polar form:

$$Z_{in} = 8.44 \angle 64.5^\circ \, \Omega$$

- The impedance driven by the source looks resistive and inductive
 - ▣ Resistive: non-zero resistance, $\angle Z_{in} \neq \pm 90^\circ$
 - ▣ Inductive: positive reactance, positive angle

Sinusoidal Steady-State Analysis – Ex. 2


55

- Apply **voltage division** to determine the voltage across the load

$$\mathbf{V}_L = \mathbf{V}_S \frac{Z_{load}}{Z_{line} + Z_{load}}$$

$$\mathbf{V}_L = 170\angle 0^\circ V \frac{3.13 + j5.74 \Omega}{3.63 + j7.62 \Omega}$$
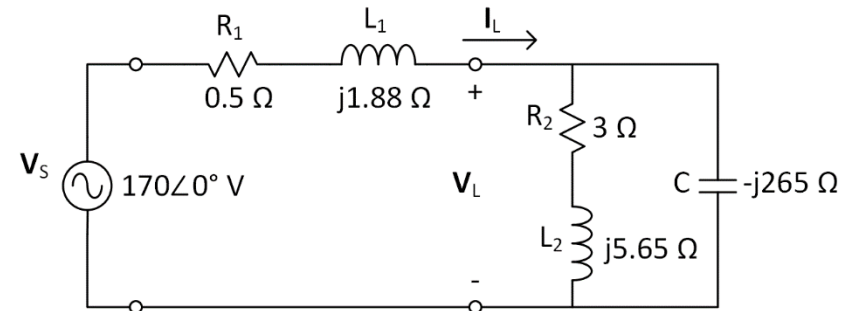
$$\mathbf{V}_L = 170\angle 0^\circ V \frac{6.54\angle 61.4^\circ \Omega}{8.44\angle 64.5^\circ \Omega} = 132\angle -3.1^\circ V$$



- Converting to **time-domain** form

$$v_L(t) = 132 V \sin(2\pi \cdot 60\text{Hz} \cdot t - 3.1^\circ)$$

Sinusoidal Steady-State Analysis – Ex. 2

56

- Finally, calculate the current delivered to the load

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{Z_{load}}$$

$$\mathbf{I}_L = \frac{132\angle -3.1^\circ \text{ V}}{6.54\angle 61.4^\circ \Omega}$$

$$\mathbf{I}_L = 20.1\angle -64.5^\circ \text{ A}$$

- In time-domain form:

$$i_L(t) = 20.1 \text{ A} \sin(2\pi \cdot 60\text{Hz} \cdot t - 64.5^\circ)$$

