

# SECTION 3: SECOND-ORDER FILTERS

ENGR 202 – Electrical Fundamentals II

2

# Introduction

# Second-Order Circuits

3

- **Order** of a circuit (or system of any kind)
  - ▣ **Number of independent energy-storage elements**
  - ▣ **Order of the differential equation** describing the system
  
- **Second-order circuits**
  - ▣ Two energy-storage elements
  - ▣ Described by second-order differential equations
  
- We will primarily be concerned with **second-order RLC circuits**
  - ▣ Circuits with a resistor, an inductor, and a capacitor

# Second-Order Circuits

4

- In this and the following section of notes, we will look at second-order RLC circuits from two distinct perspectives:
  - Section 3
    - Second-order *filters*
    - *Frequency-domain* behavior
  - Section 4
    - Second-order *transient response*
    - *Time-domain* behavior

5

# Second-Order Filters

# Second-Order Filters

6

## □ ***First-order filters***

- Roll-off rate: ***20 dB/decade***

## □ This roll-off rate determines ***selectivity***

- Spacing of pass band and stop band

- Spacing of *passed* frequencies and *stopped* or *filtered* frequencies

## □ ***Second-order filters***

- Roll-off rate: ***40 dB/decade***

## □ In general:

- Roll-off =  $N \cdot 20 \text{ dB/dec}$ , where  $N$  is the filter order

# Resonance

7

## □ **Resonance**

- Tendency of a system to oscillate at certain frequencies – ***resonant frequencies*** – often with larger amplitude than any input
- Phenomenon that occurs in all types of dynamic systems (mechanical, electrical, fluid, etc.)

---

## □ Examples of resonant mechanical systems:

- Mass on a spring
- Pendulum, playground swing
- Tacoma Narrows Bridge



# Electrical Resonance

8

- **Electrical resonance**
  - Cancellation of **reactances** (or **susceptances**), resulting in purely resistive network impedance
  - Occurs at **resonant frequencies**
  - Second- and higher-order circuits
- **Reactances (susceptances) cancel** – sum to zero ohms (siemens)
  - Inductive reactance is positive – (susceptance is negative)
  - Capacitive reactance is negative – (susceptance is positive)
- Voltages/currents in the circuit may be much larger than source voltages/currents
- We'll take a look at resonance in two classes of circuits:
  - **Series** resonant circuits
  - **Parallel** resonant circuits



9


# Series Resonant Circuits

# Series Resonant RLC Circuit

10

- Series RLC circuit
  - ▣ Second-order – one capacitor, one inductor
  - ▣ Circuit will exhibit resonance

## Impedance of the network:

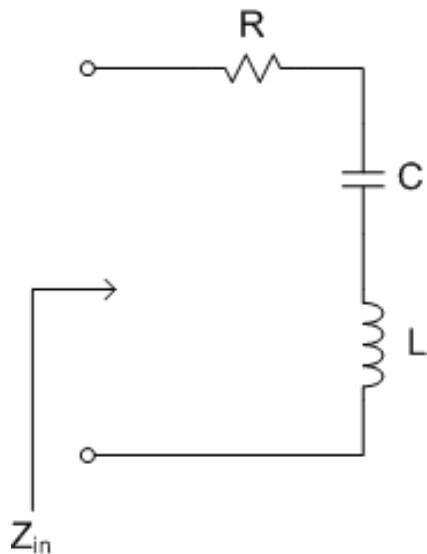

$$Z_{in}(\omega) = R + \frac{1}{j\omega C} + j\omega L = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

At the resonant frequency,  $\omega_0$  or  $f_0$ :

$$X_L + X_C = 0 \rightarrow X_L = -X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C} \rightarrow \omega_0^2 = \frac{1}{LC}$$

so

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{and}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

and

$$Z_{in}(\omega_0) = R$$

# Series RLC Circuit – Quality Factor

11

## □ **Quality factor, $Q_s$**

- ▣ Ratio of inductive reactance *at the resonant frequency* to resistance

$$Q_s = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$$


- ▣ At resonance, inductive and capacitive reactances (magnitudes) are equal, so

$$Q_s = \frac{1}{\omega_0 RC} = \frac{1}{2\pi f_0 RC}$$

- ▣ The ratio of voltage magnitude across the inductor or capacitor to the voltage across the whole RLC network *at resonance*
- ▣ A measure of the *sharpness* of the resonance

# Series RLC Circuit – $Z_{in}$ vs. $Q_s$

12

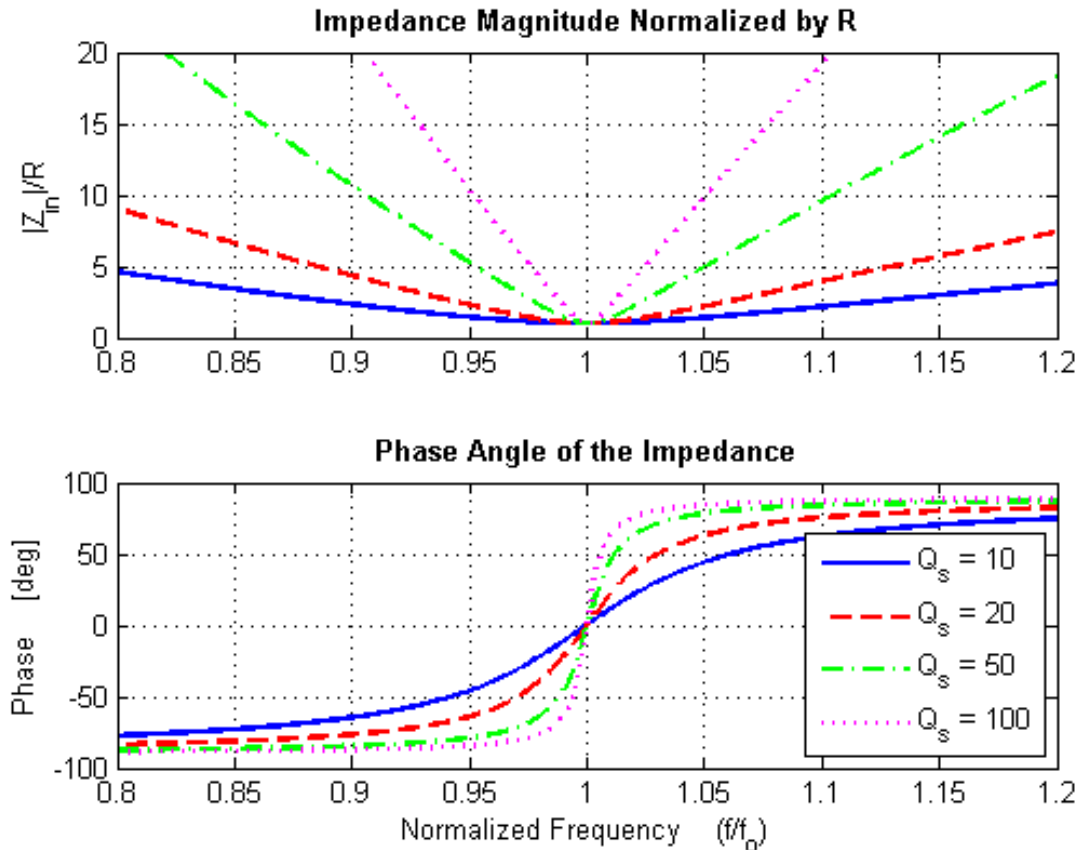

- At  $f = f_0$ 
  - ▣  $|Z_{in}| = R$
  - ▣  $\angle Z_{in} = 0^\circ$
- $Q$  determines *sharpness* of the resonance
  - ▣ Higher  $Q$  yields faster transition from capacitive, through resistive, to inductive regions
- To increase  $Q$ :
  - ▣ Increase  $L$
  - ▣ Reduce  $R$  and/or  $C$

# Series RLC Circuit – $Z_{in}$


## Understanding the impedance of a series resonant circuit

Capacitor impedance goes up as  $f$  goes down.

$f = f_0$ :  
 $Z_{in} = R$   
 $Z_{in}$  is real  
 $\angle Z_{in} = 0^\circ$


$f \ll f_0$ :  
 $\angle Z_{in} = -90^\circ$   
 $Z_{in}$  looks capacitive

Impedance Magnitude Normalized by R

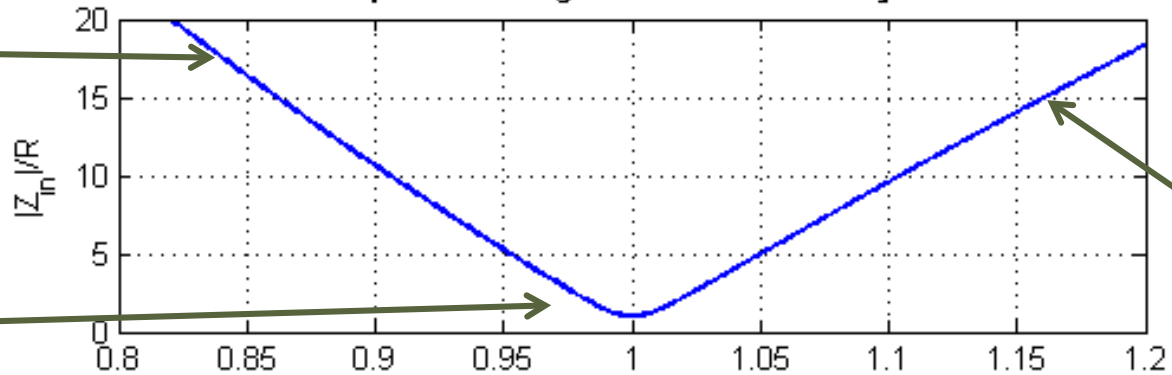

Inductor impedance goes up as  $f$  goes up.


Phase Angle of the Impedance

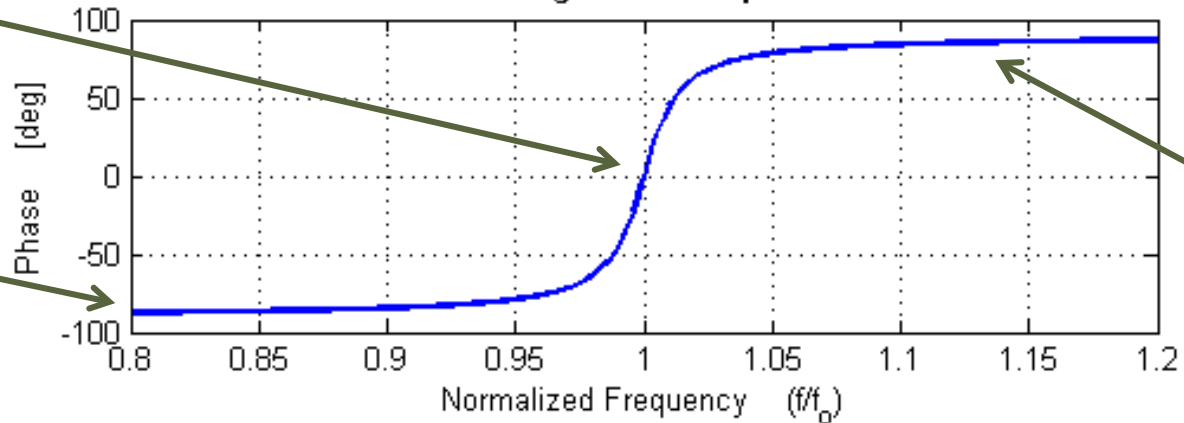

$f \gg f_0$ :  
 $\angle Z_{in} = +90^\circ$   
 $Z_{in}$  looks inductive

# Series RLC Circuit – Voltages and Currents

14

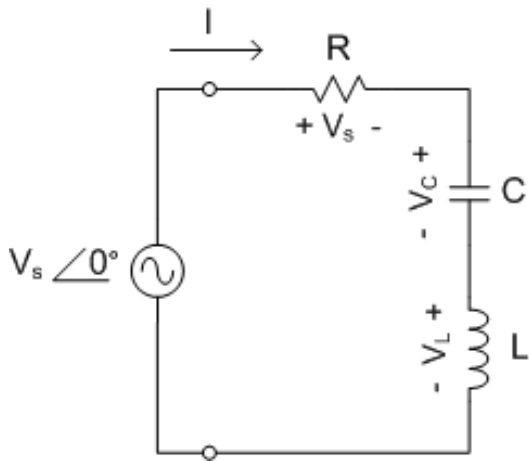

- At  $\omega_0$ ,  $Z_{in} = R$ , so the current phasor is

$$\mathbf{I} = \frac{\mathbf{V}_S}{R} = \frac{V_S}{R} \angle 0^\circ$$

- **Capacitor voltage** at resonance:

$$\mathbf{V}_C = \frac{\mathbf{I}}{j\omega_0 C} = \frac{V_S \angle 0^\circ}{\omega_0 RC \angle 90^\circ} = \frac{V_S}{\omega_0 RC} \angle -90^\circ$$


- Recalling the expression for quality factor of a series resonant circuit, we have

$$\mathbf{V}_C = Q_S \cdot V_S \angle -90^\circ$$

- The voltage across the capacitor is the source voltage multiplied by the quality factor and phase shifted by  $-90^\circ$

# Series RLC Circuit – Voltages and Currents

15

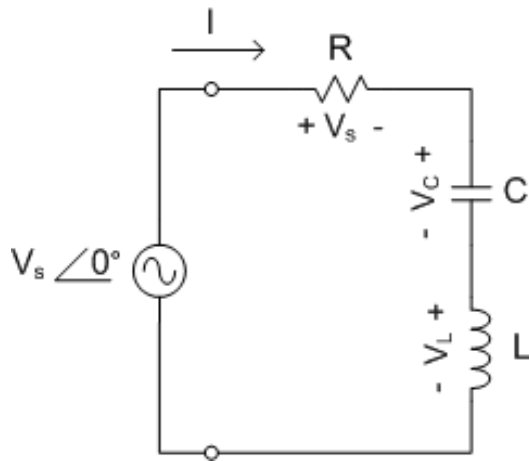

- The **inductor voltage** at resonance:

$$\mathbf{V}_L = \mathbf{I} \cdot j\omega_0 L = \frac{V_s \angle 0^\circ \cdot \omega_0 L \angle 90^\circ}{R}$$

$$\mathbf{V}_L = \frac{V_s \cdot \omega_0 L \angle 90^\circ}{R}$$

- Again, substituting in the expression for quality factor gives

$$\mathbf{V}_L = Q_s \cdot V_s \angle +90^\circ$$

- The voltage across the inductor is the source voltage multiplied by the quality factor and phase shifted by  $+90^\circ$
- Capacitor and inductor voltage at resonance:
  - Equal magnitude
  - $180^\circ$  out of phase – opposite sign – they cancel

# Series RLC Circuit – Voltages and Currents

16

- Now assign component values

- ▣ The resonant frequency is


$$\omega_0 = \frac{1}{\sqrt{LC}} = 100 \frac{\text{krad}}{\text{sec}}$$

- ▣ The quality factor is

$$Q_s = \frac{\omega_0 L}{R} = \frac{100 \frac{\text{krad}}{\text{sec}} \cdot 1 \text{ mH}}{10 \Omega} = 10$$

- The current phasor at the resonant frequency is

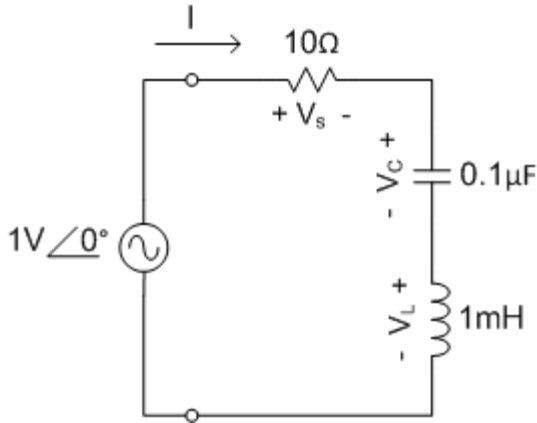
$$\mathbf{I} = \frac{\mathbf{V}_s}{R} = \frac{1 \text{ V} \angle 0^\circ}{10 \Omega} = 100 \angle 0^\circ \text{ mA}$$





# Series RLC Circuit – Voltages and Currents

17

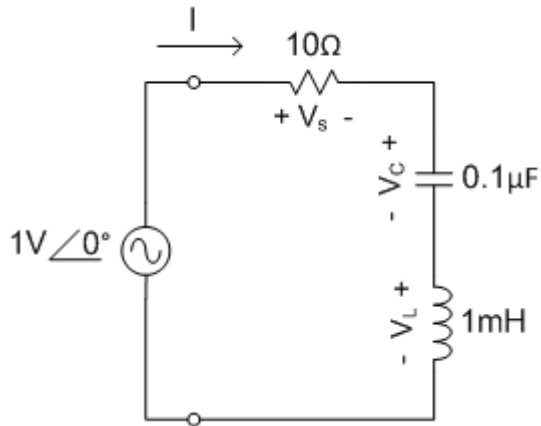

- The capacitor voltage at the resonant frequency is

$$\mathbf{V}_C = \frac{\mathbf{I}}{j\omega_0 C} = \frac{V_s}{\omega_0 RC} \angle -90^\circ = Q_s \cdot V_s \angle -90^\circ$$

$$\mathbf{V}_C = 10 \cdot 1 V \angle -90^\circ$$

$$\mathbf{V}_C = 10 V \angle -90^\circ$$

- The inductor voltage at the resonant frequency:


$$\mathbf{V}_L = \mathbf{I} \cdot j\omega_0 L = \frac{V_s \cdot \omega_0 L \angle 90^\circ}{R} = Q_s \cdot V_s \angle +90^\circ$$

$$\mathbf{V}_L = 10 \cdot 1 V \angle +90^\circ$$


$$\mathbf{V}_L = 10 V \angle +90^\circ$$

# Series RLC Circuit – Voltages and Currents

18

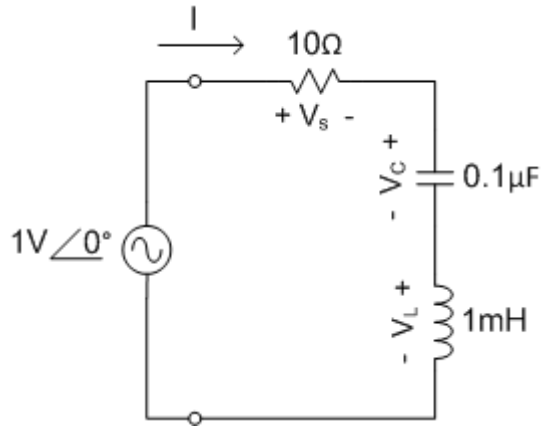

- $|V_S| = 1 V$
- $\angle I = 0^\circ$
- $|V_C| = |V_L| = Q_s |V_S| = 10 V$
- $|V_C|$  and  $|V_L|$  are  $180^\circ$  out of phase
  - ▣ They cancel
  - ▣ KVL is satisfied

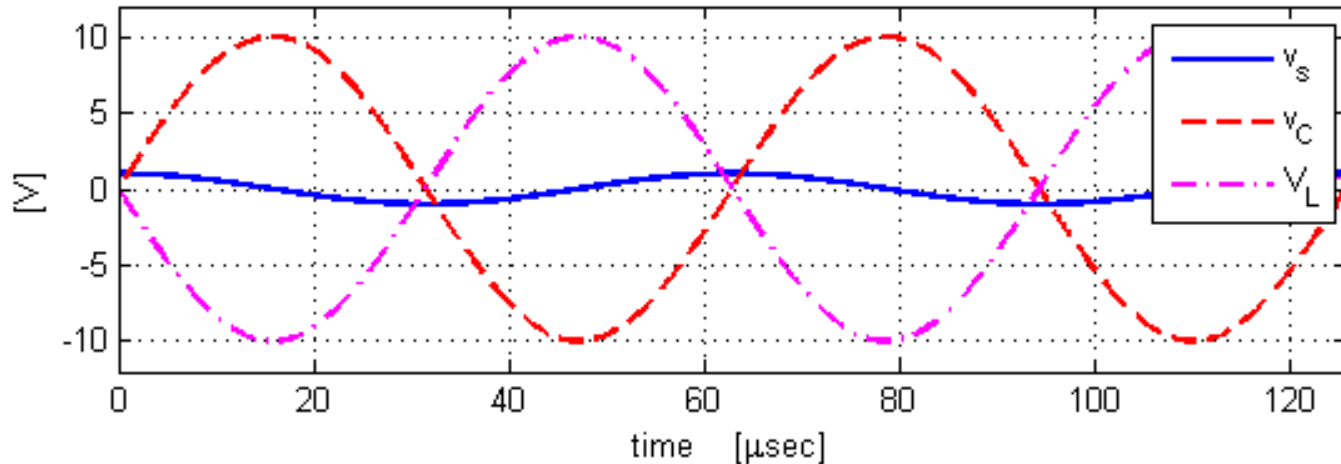

19

# Parallel Resonant Circuits

# Parallel Resonant RLC Circuit

20

- Parallel RLC circuit
  - ▣ Second-order – one capacitor, one inductor
  - ▣ Circuit will exhibit resonance

## Impedance of the network:

$$Z_{in}(\omega) = \left[ \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right]^{-1} = \left[ \frac{1}{R} + j \left( \omega C - \frac{1}{\omega L} \right) \right]^{-1}$$

At the resonant frequency,  $\omega_0$  or  $f_0$ :

$$B_C + B_L = 0 \rightarrow B_C = -B_L$$

$$\omega_0 C = \frac{1}{\omega_0 L} \rightarrow \omega_0^2 = \frac{1}{LC}$$

so


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

and

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

and

$$Z_{in}(\omega_0) = R$$

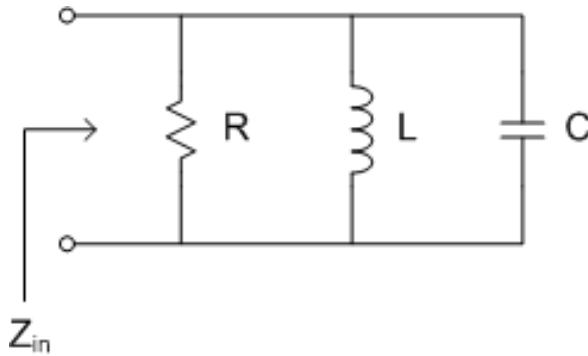

# Parallel RLC Circuit – Quality Factor

21

## □ **Quality factor, $Q_p$**

- Ratio of inductive susceptance *at the resonant frequency* to conductance

$$Q_p = \frac{1/\omega_0 L}{1/R} = \frac{R}{\omega_0 L} = \frac{R}{2\pi f_0 L}$$


- At resonance, inductive and capacitive susceptances (magnitudes) are equal, so

$$Q_p = \omega_0 RC = 2\pi f_0 RC$$

- The ratio of current magnitude through the inductor or capacitor to the current through the whole RLC network *at resonance*
- A measure of the *sharpness* of the resonance

# Parallel RLC Circuit – $Z_{in}$ vs. $Q_p$

22

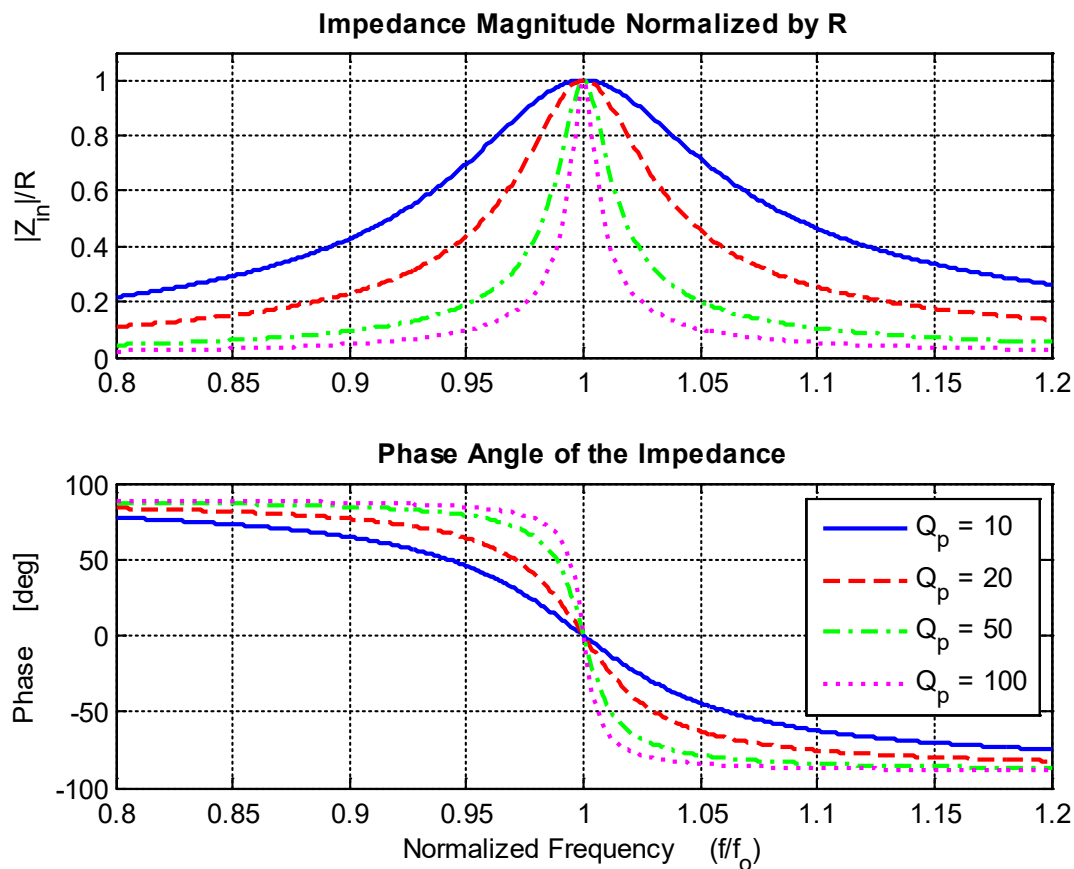

- At  $f = f_0$ 
  - ▣  $|Z_{in}| = R$
  - ▣  $\angle Z_{in} = 0^\circ$
- $Q$  determines *sharpness* of the resonance
  - ▣ Higher  $Q$  yields faster transition from inductive, through resistive, to capacitive regions
- To increase  $Q$ :
  - ▣ Reduce  $L$
  - ▣ Increase  $R$  and/or  $C$

# Parallel RLC Circuit – $Z_{in}$

23

## Understanding the impedance of a parallel resonant circuit


$f = f_0$ :  
 $Z_{in} = R$   
 $Z_{in}$  is real

Inductor tends  
toward a short  
as  $f \rightarrow 0$

$f \ll f_0$ :  
 $\angle Z_{in} = +90^\circ$   
 $Z_{in}$  looks  
inductive


$f = f_0$ :  
 $Z_{in}$  is real  
 $\angle Z_{in} = 0^\circ$

Impedance Magnitude Normalized by R

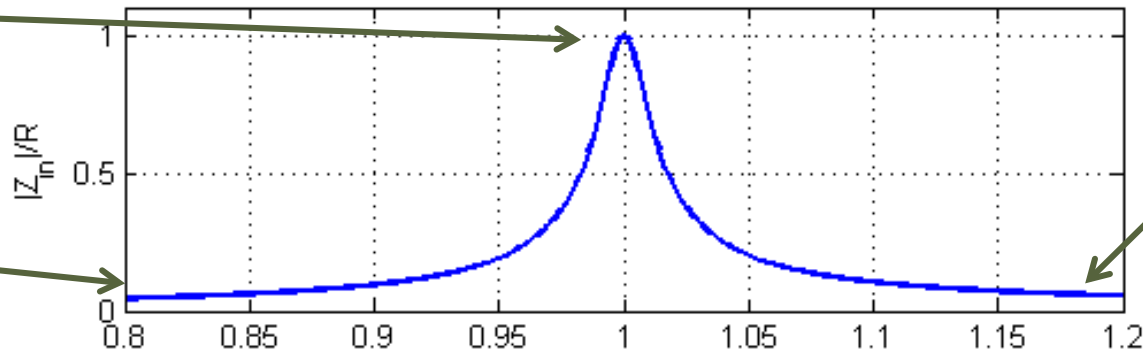

Capacitor  
tends  
toward a  
short as  
 $f \rightarrow \infty$


Phase Angle of the Impedance

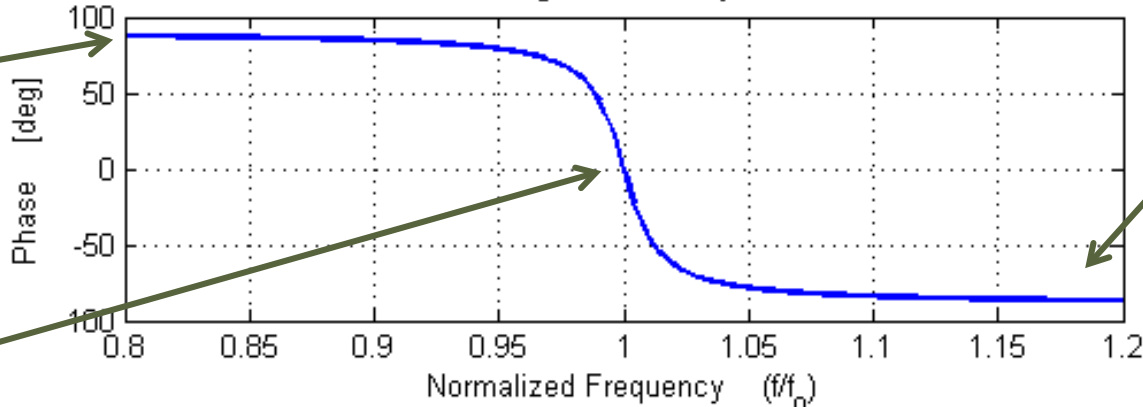

$f \gg f_0$ :  
 $\angle Z_{in} = -90^\circ$   
 $Z_{in}$  looks  
capacitive

# Parallel RLC Circuit – Voltages and Currents

24

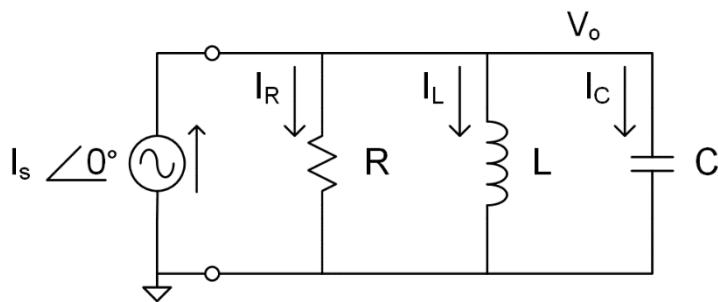

- Sinusoidal current source,  $\mathbf{I}_s$
- At resonance,  $Z_{in} = R$ , so the voltage across the network is:

$$\mathbf{V}_o = \mathbf{I}_s R = I_s \angle 0^\circ \cdot R$$

- Current through the **capacitor** at resonance:

$$\mathbf{I}_C = \mathbf{V}_o \cdot j\omega_0 C = I_s R \cdot \omega_0 C \angle 90^\circ$$

- Recalling the expression for quality factor of the parallel resonant circuit, we have


$$\mathbf{I}_C = Q_p \cdot I_s \angle 90^\circ$$

- The current through the capacitor is the source current multiplied by the quality factor and phase shifted by  $90^\circ$



# Parallel RLC Circuit – Voltages and Currents

25

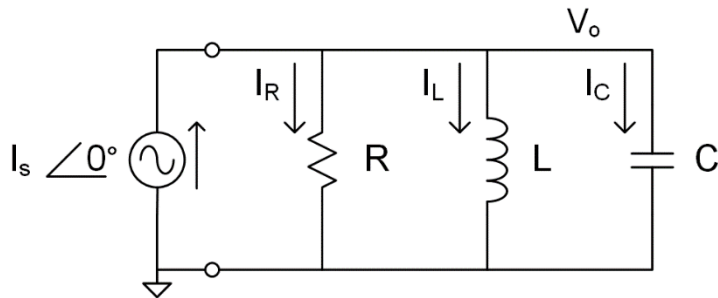

- The **inductor current** at resonance:

$$\mathbf{I}_L = \frac{\mathbf{V}_o}{j\omega_0 L} = \frac{I_s R}{\omega_0 L} \angle -90^\circ$$


- Again, substituting in the expression for quality factor gives

$$\mathbf{I}_L = Q_p \cdot I_s \angle -90^\circ$$

- The current through the inductor is the source current multiplied by the quality factor and phase shifted by  $-90^\circ$
- Capacitor and inductor current at resonance:
  - Equal magnitude
  - $180^\circ$  out of phase – opposite sign – they cancel

# Parallel RLC Circuit – Voltages and Currents

26

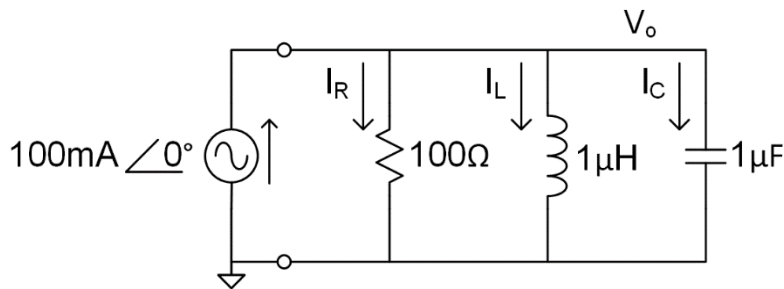

□ Now, assign component values

▣ The resonant frequency is

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1 \frac{\text{Mrad}}{\text{sec}}$$

▣ The quality factor is

$$Q_p = \frac{R}{\omega_0 L} = \frac{100 \Omega}{1 \frac{\text{Mrad}}{\text{sec}} \cdot 1 \mu\text{H}} = 100$$


□ The phasor for the voltage across the network at the resonant frequency is

$$\mathbf{V}_o = \mathbf{I}_s R = 100 \text{ mA} \angle 0^\circ \cdot 100 \Omega = 10 \angle 0^\circ \text{ V}$$
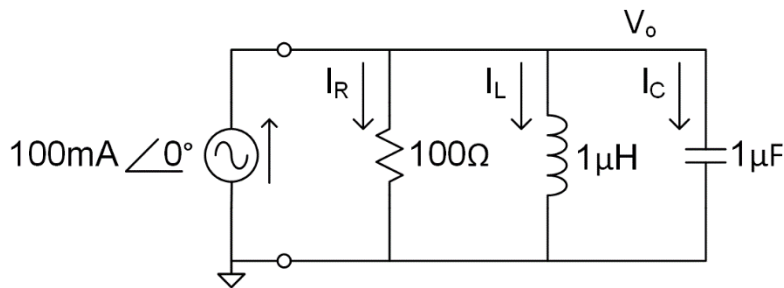
# Parallel RLC Circuit – Voltages and Currents

27

- The capacitor current at the resonant frequency is



$$\mathbf{I}_C = \mathbf{V}_o \cdot j\omega_0 C = I_s \cdot \omega_0 RC \angle 90^\circ$$

$$\mathbf{I}_C = Q_p \cdot I_s \angle 90^\circ = 100 \cdot 100 \text{ mA} \angle 90^\circ$$

$$\mathbf{I}_C = 10 \text{ A} \angle 90^\circ$$

- The inductor current at the resonant frequency:


$$\mathbf{I}_L = \frac{\mathbf{V}_o}{j\omega_0 L} = \frac{I_s R}{\omega_0 L} \angle -90^\circ = Q_p \cdot I_s \angle -90^\circ$$

$$\mathbf{I}_L = 100 \cdot 100 \text{ mA} \angle -90^\circ$$


$$\mathbf{I}_L = 10 \text{ A} \angle -90^\circ$$

# Parallel RLC Circuit – Voltages and Currents

28

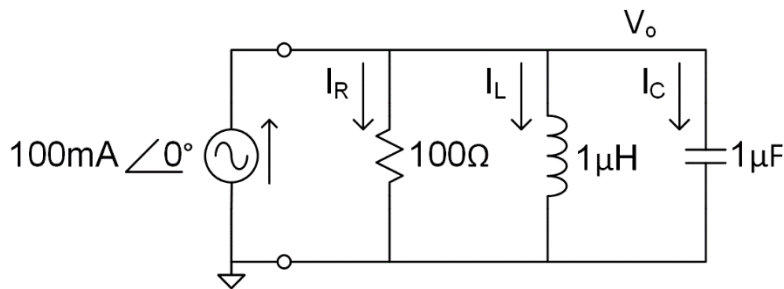


- $|\mathbf{I}_S| = 1\text{ V}$
- $\angle \mathbf{V}_o = 0^\circ$
- $|\mathbf{I}_C| = |\mathbf{I}_L| = Q_p |\mathbf{I}_S| = 10\text{ A}$
- $|\mathbf{I}_C|$  and  $|\mathbf{I}_L|$  are  $180^\circ$  out of phase
  - ▣ They cancel
  - ▣ KCL is satisfied

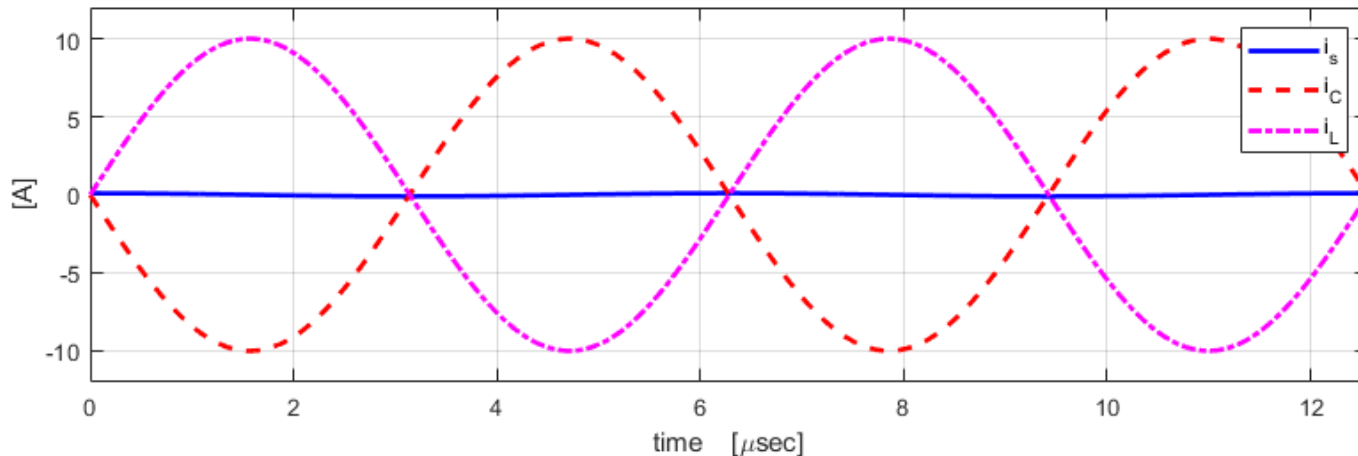

29

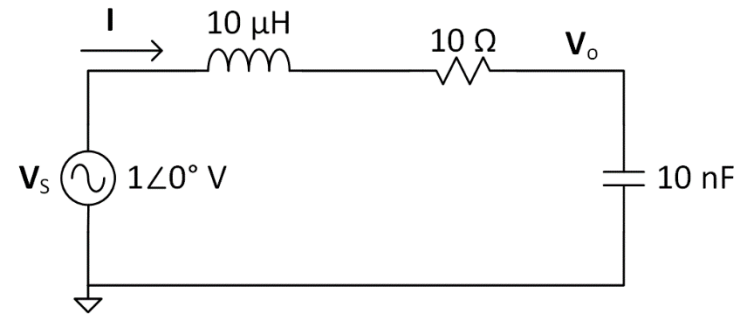
# Example Problems

Determine the voltage across the capacitor,  $V_o$ , at the resonant frequency.





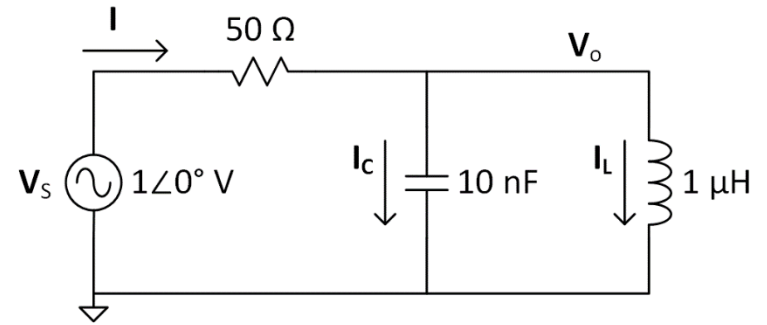
Determine  $V_o$ ,  $I$ ,  $I_C$ , and  $I_L$  at the resonant frequency.







Determine  $R$ , such that  $|V_o| = 100|V_s|$  at the resonant frequency.

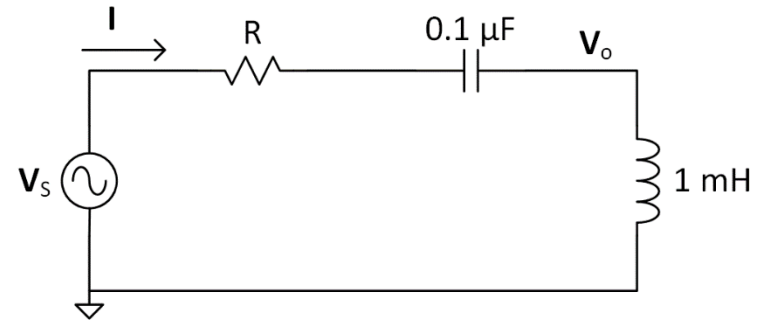


35

# Second-Order Filters
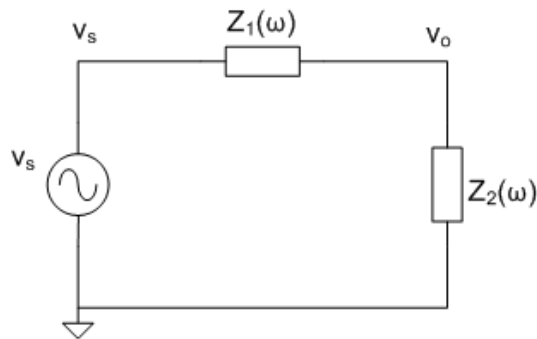
# Second-Order Filters as Voltage Dividers

36


- Derive the frequency response functions of second-order filters by treating the circuits as voltage dividers



$$H(\omega) = \frac{Z_2(\omega)}{Z_1(\omega) + Z_2(\omega)}$$

- Now,  $Z_1$  and  $Z_2$  can be either a single R, L, or C, or a series or parallel combination of any two

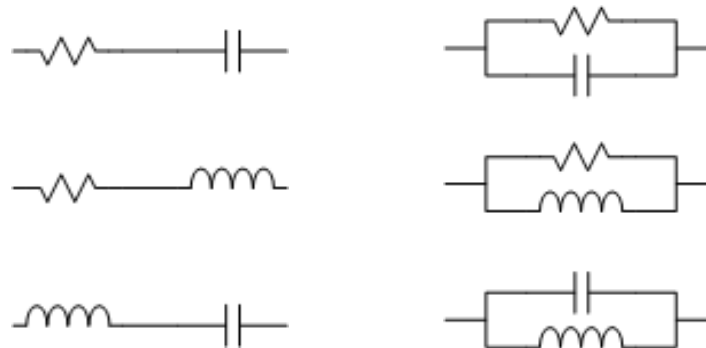Possible combinations of components for  $Z_1$  or  $Z_2$ :



37

# Second-Order Band Pass Filter

# Second-Order Band Pass Filter

38

- One option for a second-order band pass filter:
  - ▣ The frequency response function:

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$


where

$$Z_1 = R \quad \text{and} \quad Z_2 = \left[ j\omega C + \frac{1}{j\omega L} \right]^{-1} = \frac{j\omega L}{1 + (j\omega)^2 LC}$$

so

$$H(\omega) = \frac{\frac{j\omega L}{1 + (j\omega)^2 LC}}{R + \frac{j\omega L}{1 + (j\omega)^2 LC}} = \frac{j\omega L}{(j\omega)^2 RLC + j\omega L + R}$$


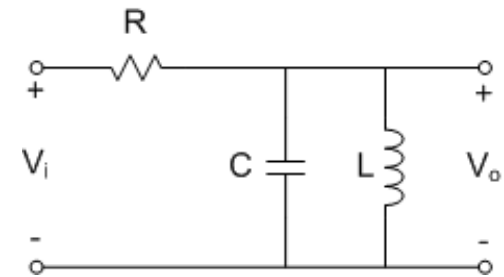
$$H(\omega) = \frac{j\omega/RC}{(j\omega)^2 + j\omega/RC + 1/LC}$$



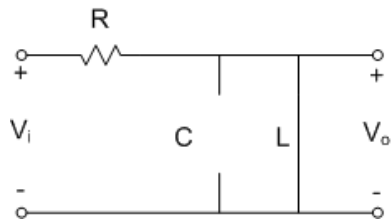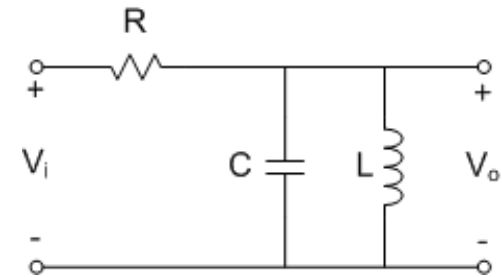
# Second-Order Band Pass Filter

39


- Consider the filter's behavior at three limiting cases for frequency



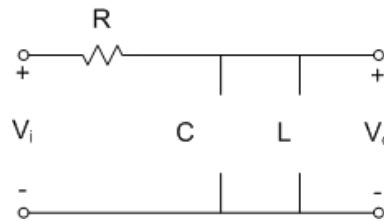- $f \rightarrow 0$ :
  - $C \rightarrow$  open
  - $L \rightarrow$  short
  - $v_o$  shorted to ground
  - Gain  $\rightarrow 0$



- $f = f_0$ :
  - $B_C, B_L$  cancel
  - $L||C \rightarrow$  open
  - $v_o = v_i$
  - Gain  $\rightarrow 1$

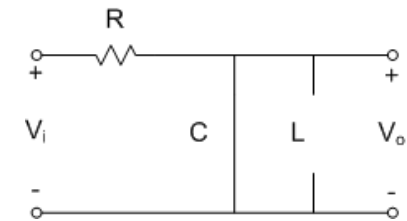

- $f \rightarrow \infty$ :
  - $C \rightarrow$  short
  - $L \rightarrow$  open
  - $v_o$  shorted to ground
  - Gain  $\rightarrow 0$


# Second-Order Band Pass Filter

40

- A second option for a second-order band pass filter:
  - ▣ Now, the impedances are:

$$Z_1 = j\omega L + \frac{1}{j\omega C} = \frac{(j\omega)^2 LC + 1}{j\omega C}$$

$$Z_2 = R$$

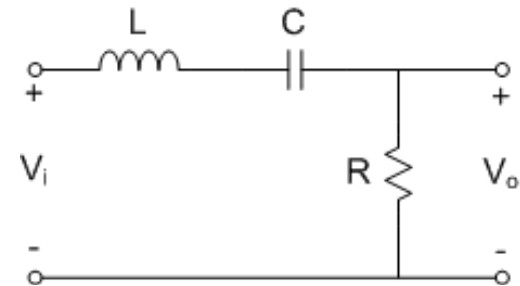

- ▣ The frequency response function:

$$H(\omega) = \frac{R}{R + \frac{(j\omega)^2 LC + 1}{j\omega C}} = \frac{j\omega RC}{(j\omega)^2 LC + j\omega RC + 1}$$



$$H(\omega) = \frac{j\omega R/L}{(j\omega)^2 + j\omega R/L + 1/LC}$$



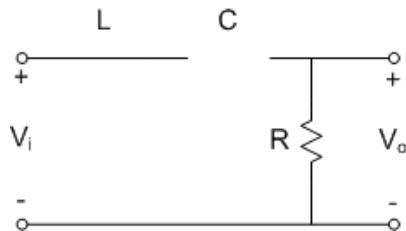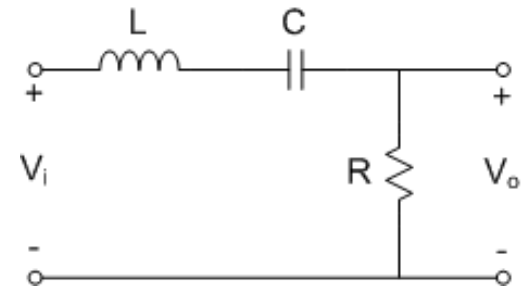
# Second-Order Band Pass Filter

41


- Consider the filter's behavior at three limiting cases for frequency



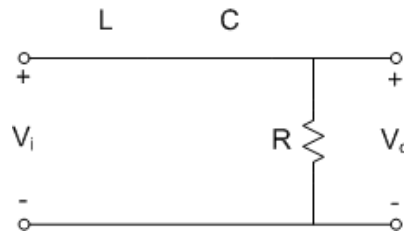- $f \rightarrow 0$ :
  - $C \rightarrow$  open
  - $L \rightarrow$  short
  - Current  $\rightarrow 0$
  - $v_o \rightarrow 0$
  - Gain  $\rightarrow 0$



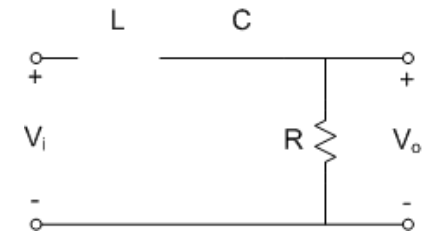- $f = f_0$ :
  - $X_C, X_L$  cancel
  - $L, C \rightarrow$  short
  - $v_o = v_i$
  - Gain  $\rightarrow 1$



- $f \rightarrow \infty$ :
  - $L \rightarrow$  open
  - $C \rightarrow$  short
  - Current  $\rightarrow 0$
  - $v_o \rightarrow 0$
  - Gain  $\rightarrow 0$


# 2<sup>nd</sup>-Order BPF – General-Form Frequency Response

42


- Each of the two BPF variations has the same resonant frequency:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

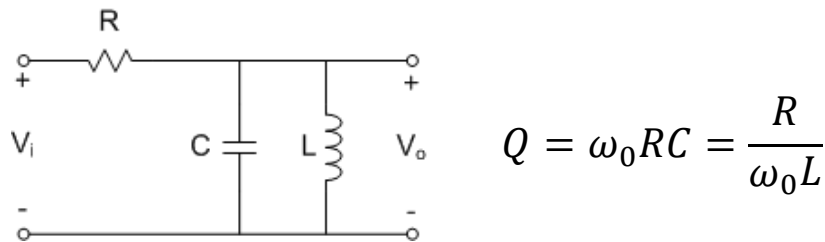- They have different frequency response functions and quality factors:


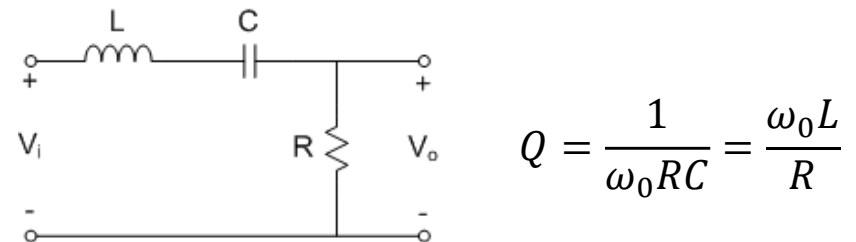
$$H(\omega) = \frac{j\omega/RC}{(j\omega)^2 + j\omega/RC + 1/LC}$$



$$H(\omega) = \frac{j\omega R/L}{(j\omega)^2 + j\omega R/L + 1/LC}$$


- Each frequency response function can be expressed in terms of  $\omega_0$  and  $Q$ :

$$H(\omega) = \frac{\frac{\omega_0}{Q} j\omega}{(j\omega)^2 + \frac{\omega_0}{Q} j\omega + \omega_0^2}$$
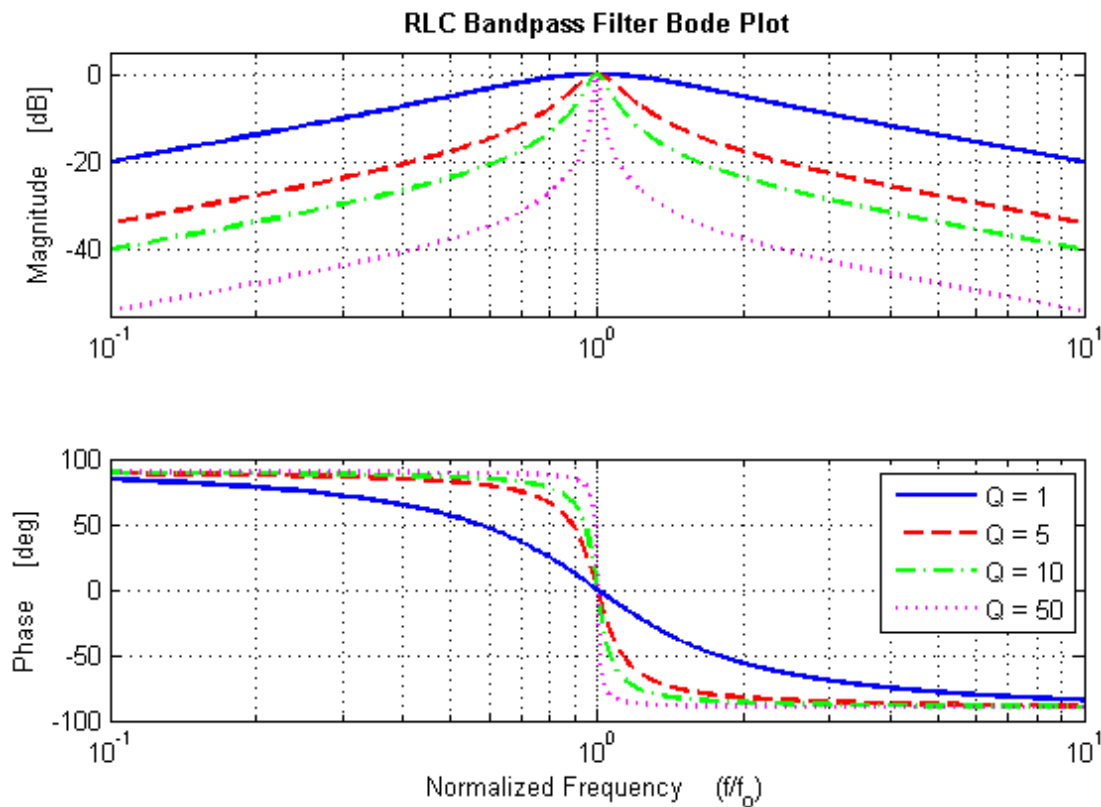
# Second-Order Band Pass Filter

43

- Same frequency response for each band pass filter



- $Q$  determines the sharpness of the resonance
- **Higher  $Q$**  provides **higher selectivity**
  - Narrower pass band
  - Steeper transition to the stop bands

# 2<sup>nd</sup>-Order BP Filter – Bandwidth


44

- Bandwidth of a low pass filter is the 3 dB frequency
- A **band pass filter** has two 3 dB frequencies
  - **Bandwidth** is the difference between the two 3 dB frequencies

$$BW = f_U - f_L$$

- Bandwidth is inversely proportional to Q

$$BW = \frac{f_0}{Q}$$

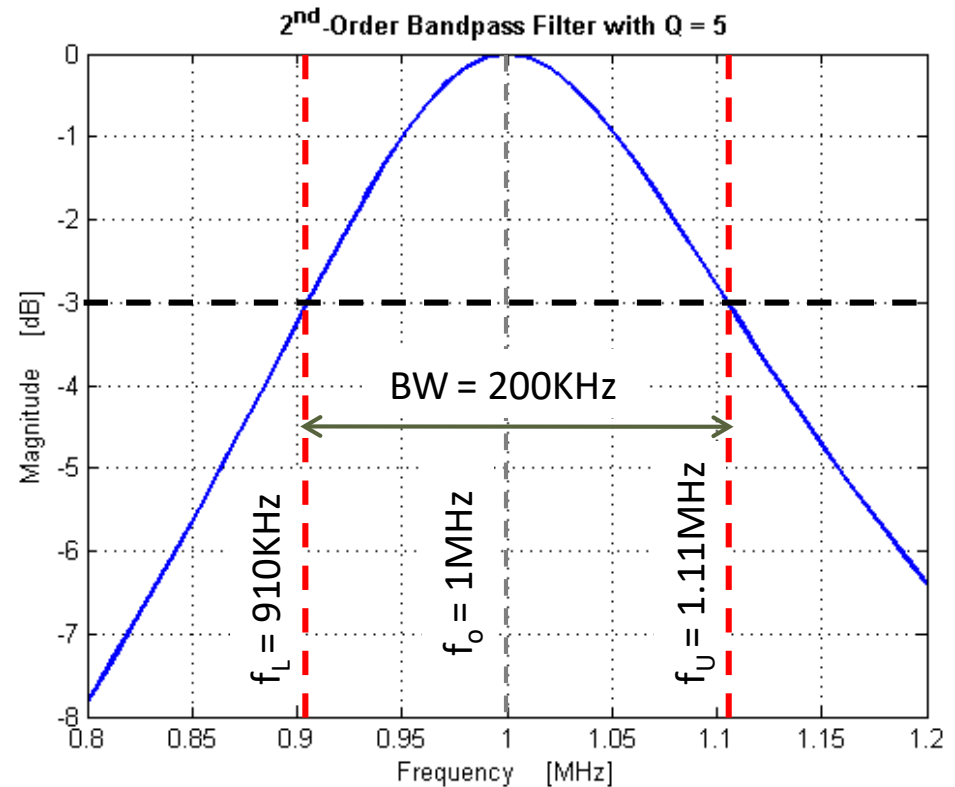

$$BW = f_U - f_L = \frac{f_0}{Q} = 200 \text{ kHz}$$


# 2<sup>nd</sup>-Order BP Filter – Example

45

- Need a band pass filter to isolate a broadcast TV channel
  - ▣ Carrier frequency: 180MHz
  - ▣ Bandwidth of the filter: 6MHz
  - ▣ Thévenin equivalent resistance of signal source:  $75\Omega$
- Use a parallel LC network
  - ▣ A ***tank circuit***

# 2<sup>nd</sup>-Order BP Filter – Example

46

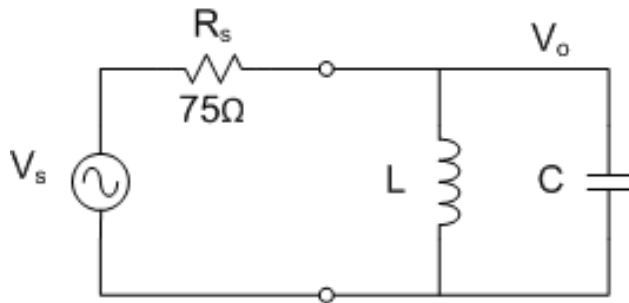

- Center frequency of the filter is:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 180\text{ MHz}$$

- Specified bandwidth dictates the required  $Q$  value

$$Q = \frac{f_0}{BW} = \frac{180\text{ MHz}}{6\text{ MHz}} = 30$$

- Calculate the required inductance (and/or capacitance) using the values of  $R_s$ ,  $Q$ , and  $f_0$ :

$$L = \frac{R_s}{\omega_0 Q} = \frac{75\ \Omega}{2\pi \cdot 180\text{ MHz} \cdot 30} = 2.2\text{ nH}$$




- Use the center frequency to determine the required capacitance

$$C = \frac{1}{L\omega_0^2} = \frac{1}{2.2\text{ nH}(2\pi \cdot 180\text{ MHz})^2} = 355\text{ pF}$$
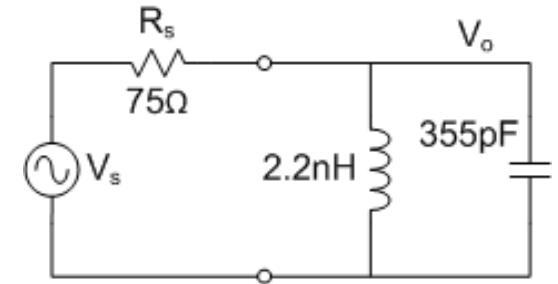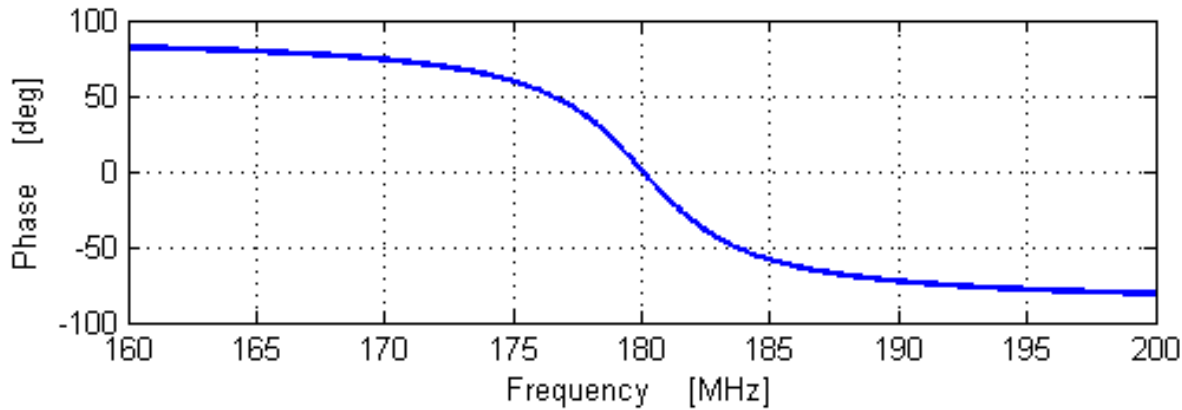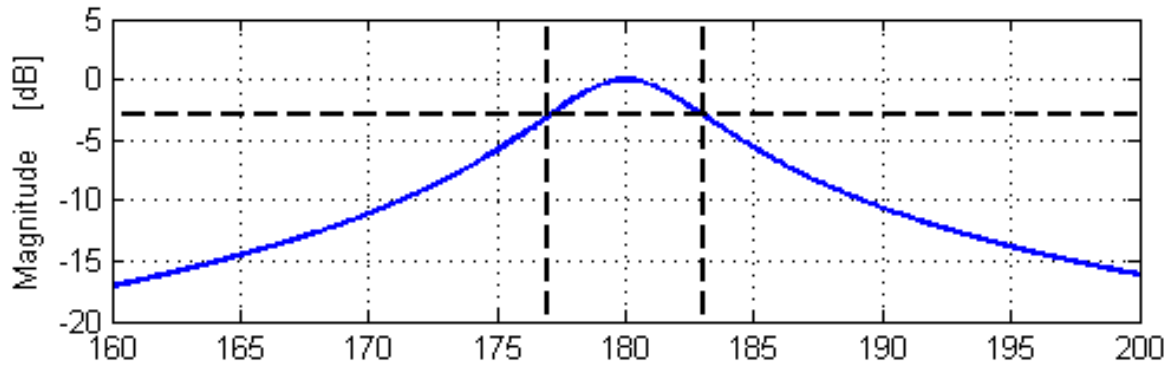
# 2<sup>nd</sup>-Order BP Filter – Example

47

2<sup>nd</sup>-Order Bandpass Filter with  $f_o = 180\text{MHz}$ ,  $Q = 30$



48

# Second-Order Band Stop Filter



# Second-Order Band Stop Filter

49

- One option for a second-order **band stop**, or **notch**, filter:
  - ▣ The frequency response function:

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$


where

$$Z_1 = R \quad \text{and} \quad Z_2 = j\omega L + \frac{1}{j\omega C} = \frac{(j\omega)^2 LC + 1}{j\omega C}$$

so

$$H(\omega) = \frac{\frac{(j\omega)^2 LC + 1}{j\omega C}}{R + \frac{(j\omega)^2 LC + 1}{j\omega C}} = \frac{(j\omega)^2 LC + 1}{(j\omega)^2 LC + j\omega RC + 1}$$


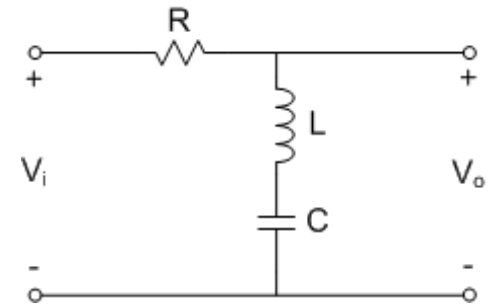
$$H(\omega) = \frac{(j\omega)^2 + 1/LC}{(j\omega)^2 + j\omega R/L + 1/LC}$$



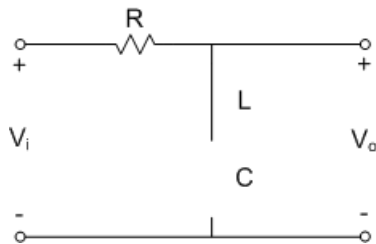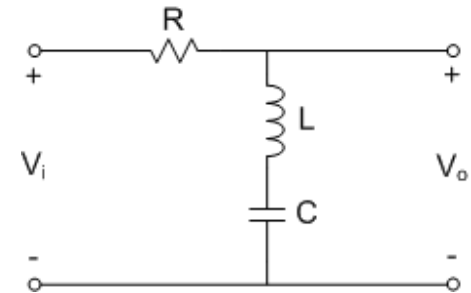
# Second-Order Band Stop Filter

50


- Consider the filter's behavior at three limiting cases for frequency



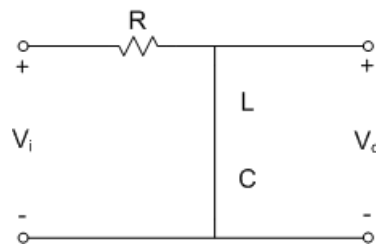- $f \rightarrow 0$ :
  - $C \rightarrow$  open
  - $L \rightarrow$  short
  - Current  $\rightarrow 0$
  - $v_o \rightarrow v_i$
  - Gain  $\rightarrow 1$



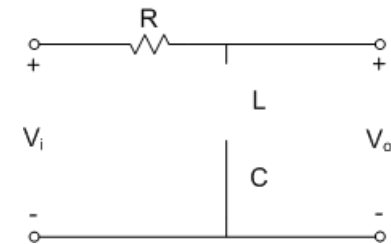- $f = f_0$ :
  - $X_C, X_L$  cancel
  - $L, C \rightarrow$  short
  - $v_o$  shorted to ground
  - Gain  $\rightarrow 0$



- $f \rightarrow \infty$ :
  - $C \rightarrow$  short
  - $L \rightarrow$  open
  - Current  $\rightarrow 0$
  - $v_o \rightarrow v_i$
  - Gain  $\rightarrow 1$

# 2<sup>nd</sup>-Order BSF – General-Form Frequency Response

51

## □ **Second-order band stop filter**

- Resonant (center) frequency:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

- Quality factor:


$$Q = \frac{1}{\omega_0 RC} = \frac{\omega_0 L}{R}$$

- Frequency response function:

$$H(\omega) = \frac{(j\omega)^2 + 1/LC}{(j\omega)^2 + j\omega R/L + 1/LC}$$


- General form, in terms of  $\omega_0$  and  $Q$ :
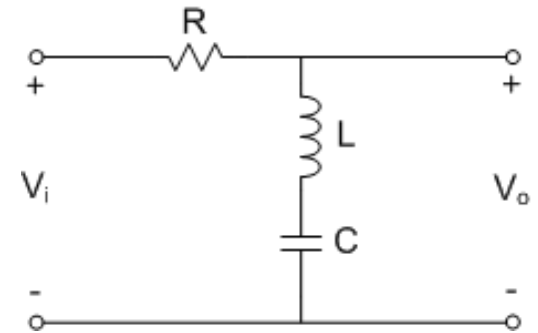
$$H(\omega) = \frac{(j\omega)^2 + \omega_0^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2}$$



# Second-Order Band Stop Filter

52

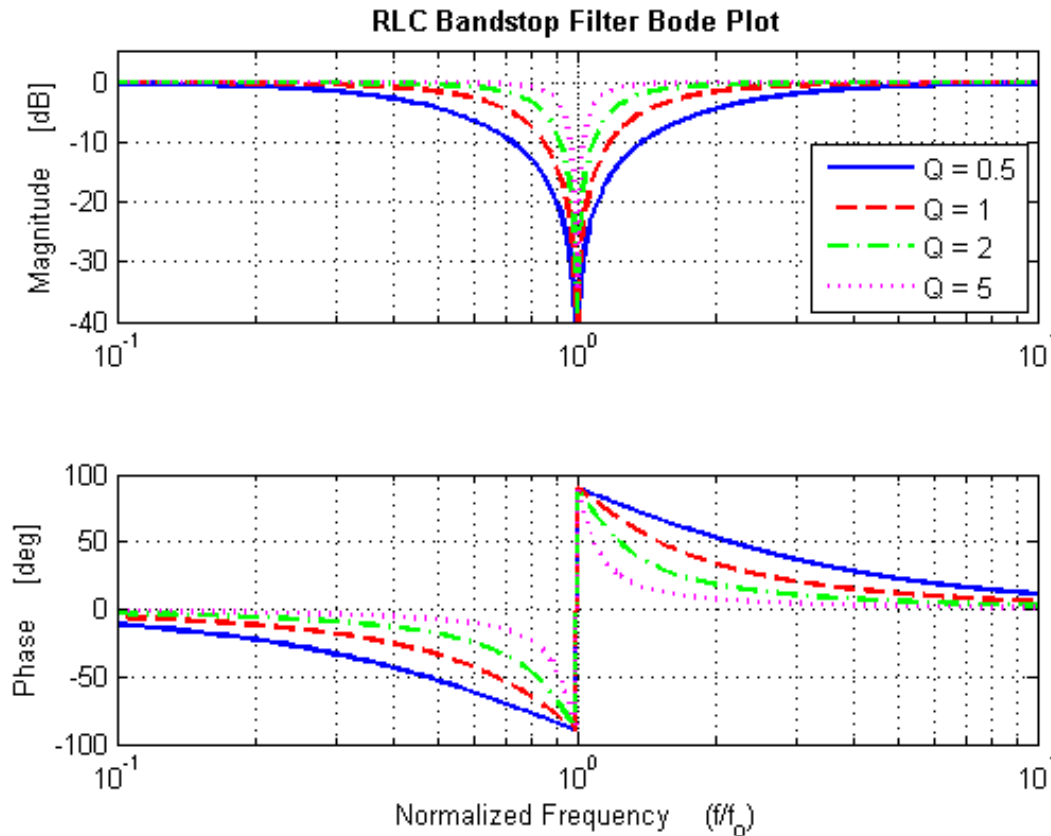

- All second-order notch filters provide same response as a function of  $Q$  and  $\omega_0$
- $Q$  determines the sharpness of the response
- **Higher  $Q$  provides higher selectivity**
  - ▣ Narrower stop band
  - ▣ Steeper transition to the pass bands

# 2<sup>nd</sup>-Order Notch Filter – Bandwidth

53


- Like the band pass filter, the **band stop filter** has two 3 dB frequencies

- **Bandwidth** is the difference between the two 3 dB frequencies

$$BW = f_U - f_L$$

- Bandwidth is inversely proportional to Q

$$BW = \frac{f_0}{Q}$$

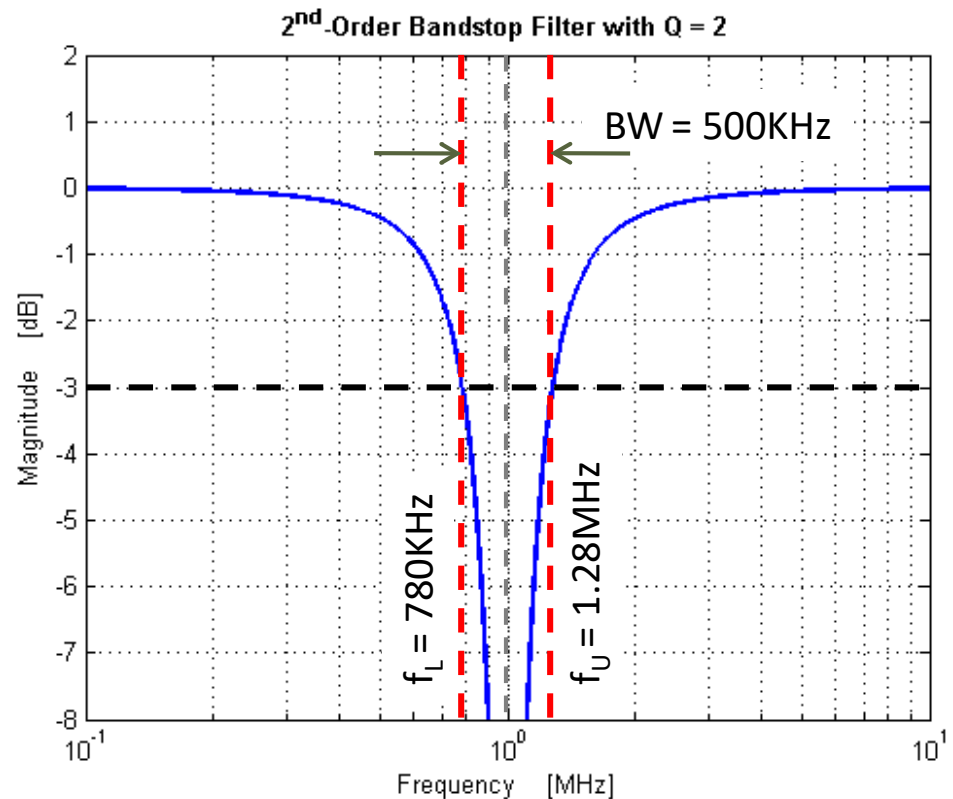

$$BW = f_U - f_L = \frac{f_0}{Q} = 500\text{ kHz}$$


# 2<sup>nd</sup>-Order Notch Filter – Example

54

- Consider the following scenario:
  - Measuring transient pressure fluctuations inside an enclosed chamber
  - Pressure transducer monitored by a data acquisition system
  - Measured signal is small – all frequency content lies in the 1KHz – 15KHz range
  - Also interested in the average (DC) pressure value
    - AC coupling (HP filter) is not an option
    - Need to keep DC as well as 1KHz – 15KHz
  - Measurements are extremely noisy
    - Signal is completely buried in 60Hz power line noise
  - Design a notch filter to reject any 60Hz power line noise

# 2<sup>nd</sup>-Order Notch Filter – Example

55

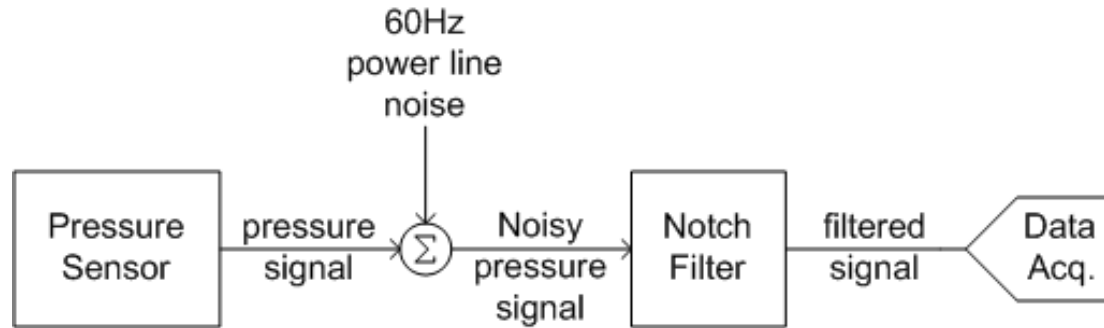

- Filter design considerations
  - Center frequency: 60 Hz
  - Attenuate signal of interest as little as possible
    - Set upper 3 dB frequency one decade below the lower end of the signal range (1 kHz)
  - Sensor output resistance: 100  $\Omega$
  - DAQ system input resistance: 1 M $\Omega$

# 2<sup>nd</sup>-Order Notch Filter – Example

56

- Upper 3 dB frequency is one decade below 1 kHz

$$f_U = 100 \text{ Hz}$$



- Simplify by assuming that the 3 dB frequencies are evenly spaced about  $f_0$

$$BW = 2(f_U - f_0) = 80 \text{ Hz}$$

- Required Q is then

$$Q = \frac{f_0}{BW} = \frac{60 \text{ Hz}}{80 \text{ Hz}} = 0.75$$

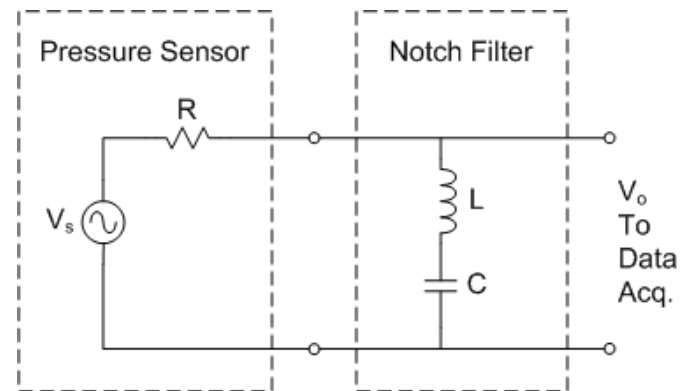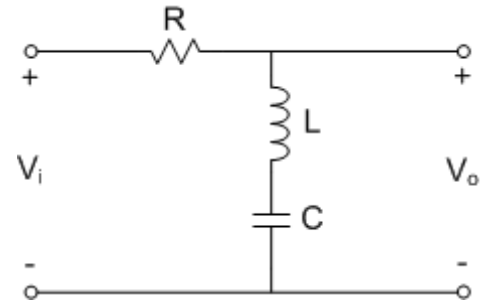- Sensor output resistance can serve as the filter resistor
- DAQ input resistance of 1 M $\Omega$  is large enough to be neglected





# 2<sup>nd</sup>-Order Notch Filter – Example

57

- Determine  $L$  and  $C$  values to satisfy  $f_0$  and  $Q$  requirements

- ▣ The required inductance:


$$L = \frac{Q \cdot R}{\omega_0} = \frac{0.75 \cdot 100 \Omega}{2\pi \cdot 60 \text{ Hz}} = 198 \text{ mH}$$

- ▣ Calculate  $C$  to place the center frequency at 60 Hz

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(2\pi \cdot 60 \text{ Hz})^2 \cdot 198 \text{ mH}} = 35.5 \mu\text{F}$$

- A couple things worth noting:


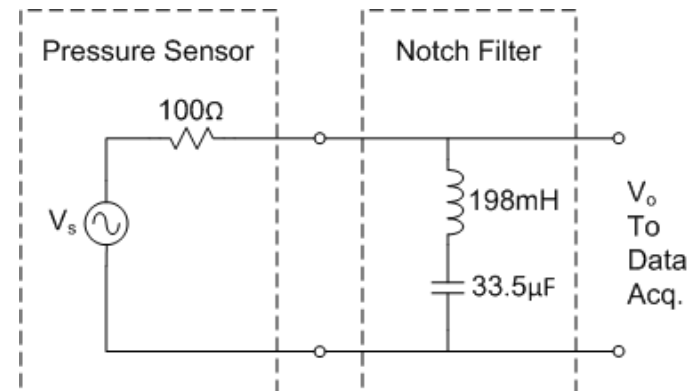
- ▣ Some iteration selecting standard-value components would be required
- ▣ Accuracy and stability of sensor output resistance would need to be verified


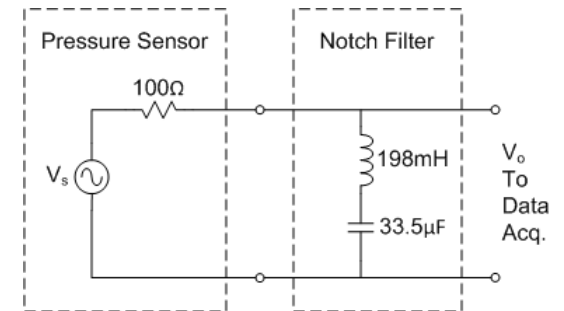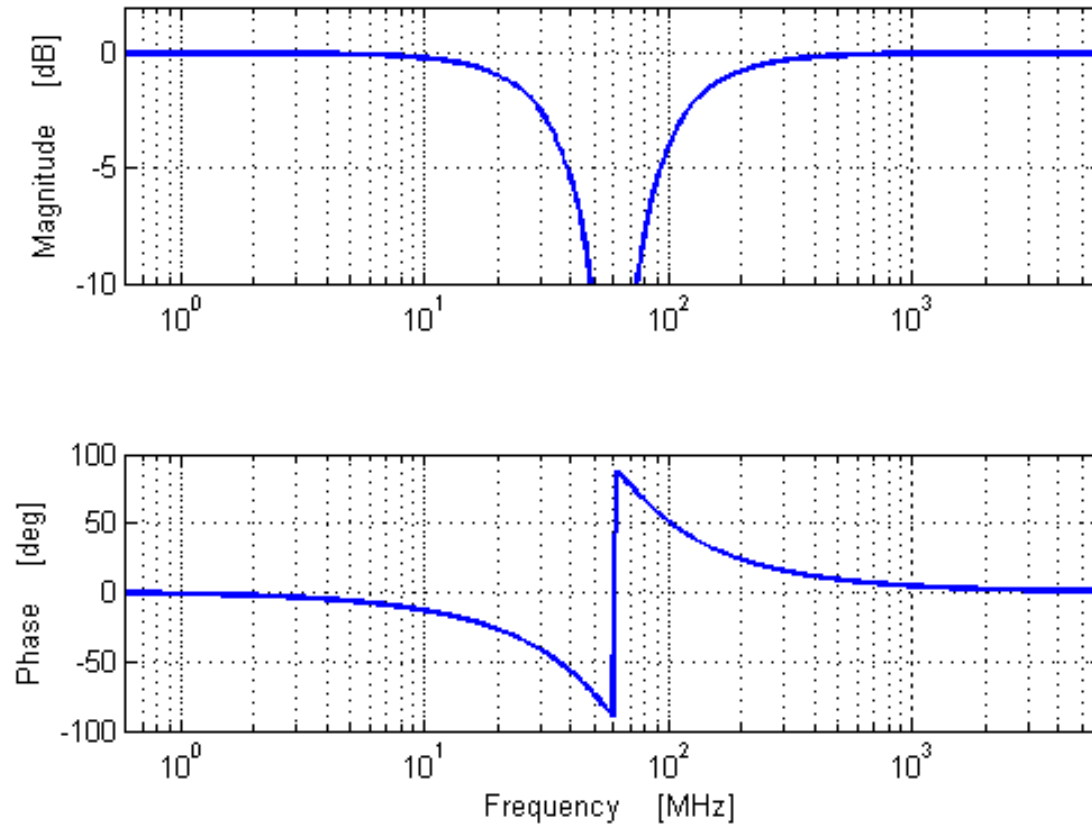
# 2<sup>nd</sup>-Order Notch Filter – Example

58

2<sup>nd</sup>-Order Bandstop Filter with  $f_0 = 60\text{Hz}$ ,  $Q = 0.75$



59

# Second-Order Low Pass Filter

# Second-Order Low Pass Filter

60

- Second-order low pass filter:
  - ▣ The frequency response function:

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$


where

$$Z_1 = R + j\omega L \quad \text{and} \quad Z_2 = \frac{1}{j\omega C}$$

so

$$H(\omega) = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{(j\omega)^2 LC + j\omega RC + 1}$$
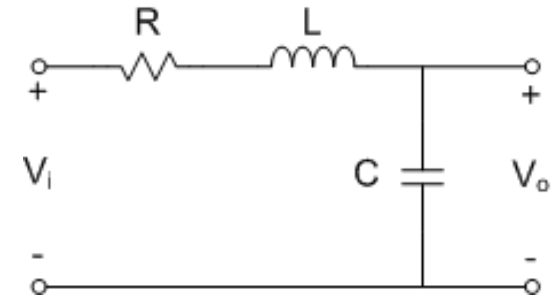
$$H(\omega) = \frac{1/LC}{(j\omega)^2 + j\omega R/L + 1/LC}$$



# 2<sup>nd</sup>-Order LPF – General-Form Frequency Response

61

## □ **Second-order low pass filter**

- Resonant frequency:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

- Quality factor:


$$Q = \frac{1}{\omega_0 RC} = \frac{\omega_0 L}{R}$$

- Frequency response function:

$$H(\omega) = \frac{1/LC}{(j\omega)^2 + j\omega R/L + 1/LC}$$

- General form, in terms of  $\omega_0$  and  $Q$ :


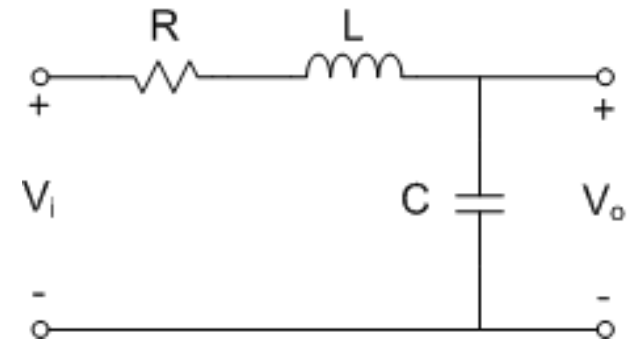
$$H(\omega) = \frac{\omega_0^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2}$$


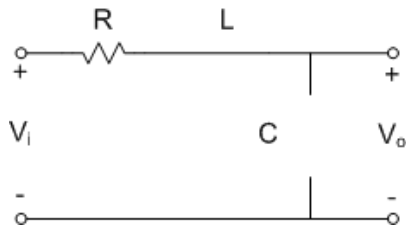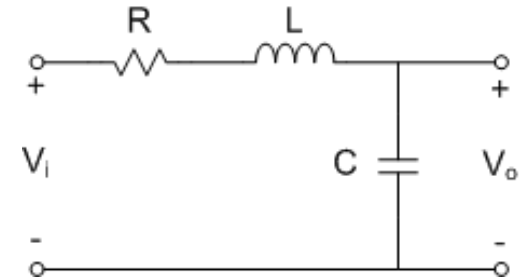
# Second-Order Low Pass Filter

62


- Consider the filter's behavior at three limiting cases for frequency



- $f \rightarrow 0$ :
  - $L \rightarrow$  short
  - $C \rightarrow$  open
  - Current  $\rightarrow 0$
  - $v_o \rightarrow v_i$
  - Gain  $\rightarrow 1$

?

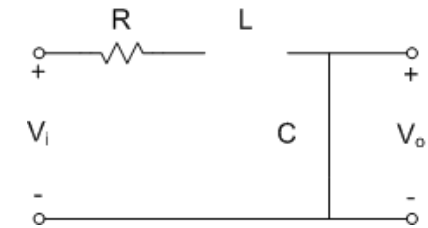- $f = f_0$ :
  - Behavior at resonance is a bit trickier here



- $f \rightarrow \infty$ :
  - $L \rightarrow$  open
  - $C \rightarrow$  short
  - $v_o$  shorted to ground
  - Gain  $\rightarrow 0$


# Second-Order LPF at Resonance

63

- Input impedance at resonance:  $Z_{in}(\omega_0) = R$
- The series LC section is essentially a short
  - But, neither the inductor nor the capacitor, individually, are shorts
  - And, output is taken across the capacitor
    - Recall that at resonance, capacitor and inductor voltages can exceed the input voltage

$Z_{in} = R$ , so

$$\mathbf{I} = \frac{\mathbf{V}_i}{R}$$

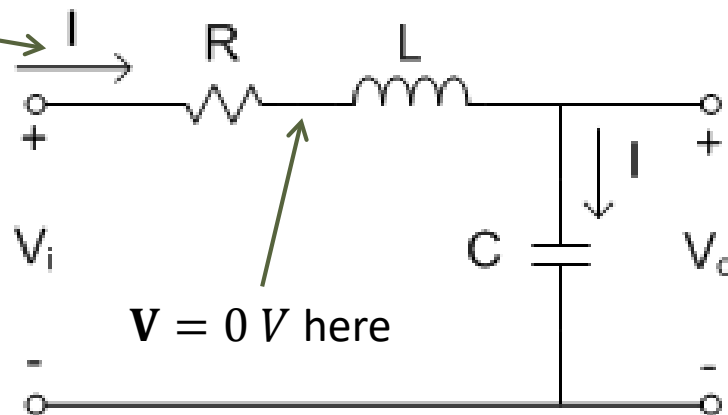

Output voltage phasor is:


$$\mathbf{V}_o = \frac{\mathbf{I}}{j\omega_0 C}$$

$$\mathbf{V}_o = \frac{\mathbf{V}_i}{\omega_0 RC} \angle -90^\circ$$

which may be larger than  $\mathbf{V}_i$

# Second-Order Low Pass Filter

64

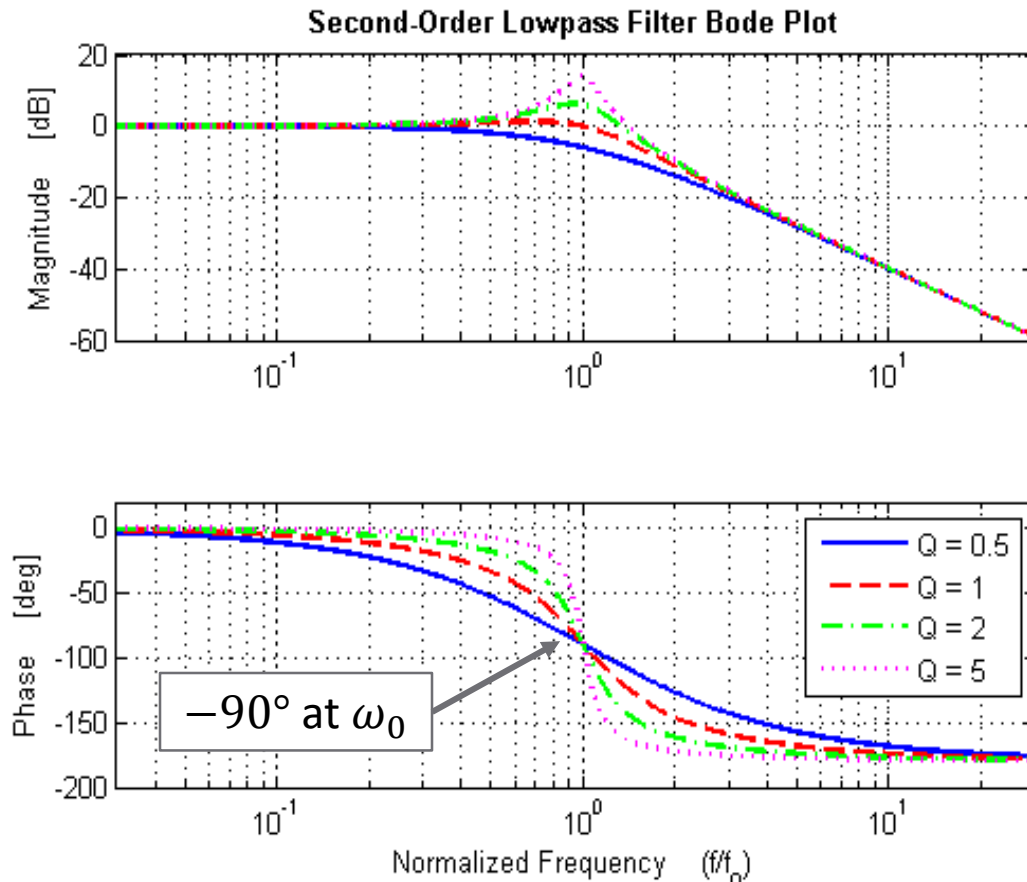

- Second-order roll-off rate:


$$40 \frac{dB}{dec}$$

- $Q$  determines:
  - ▣ Amount of peaking
  - ▣ Rate of phase transition
- No peaking at all for  $Q \leq \frac{1}{\sqrt{2}} = 0.707$
- Phase at  $\omega_0$ :  $-90^\circ$



# 2<sup>nd</sup>-Order Low Pass Filter – 3dB Bandwidth

65

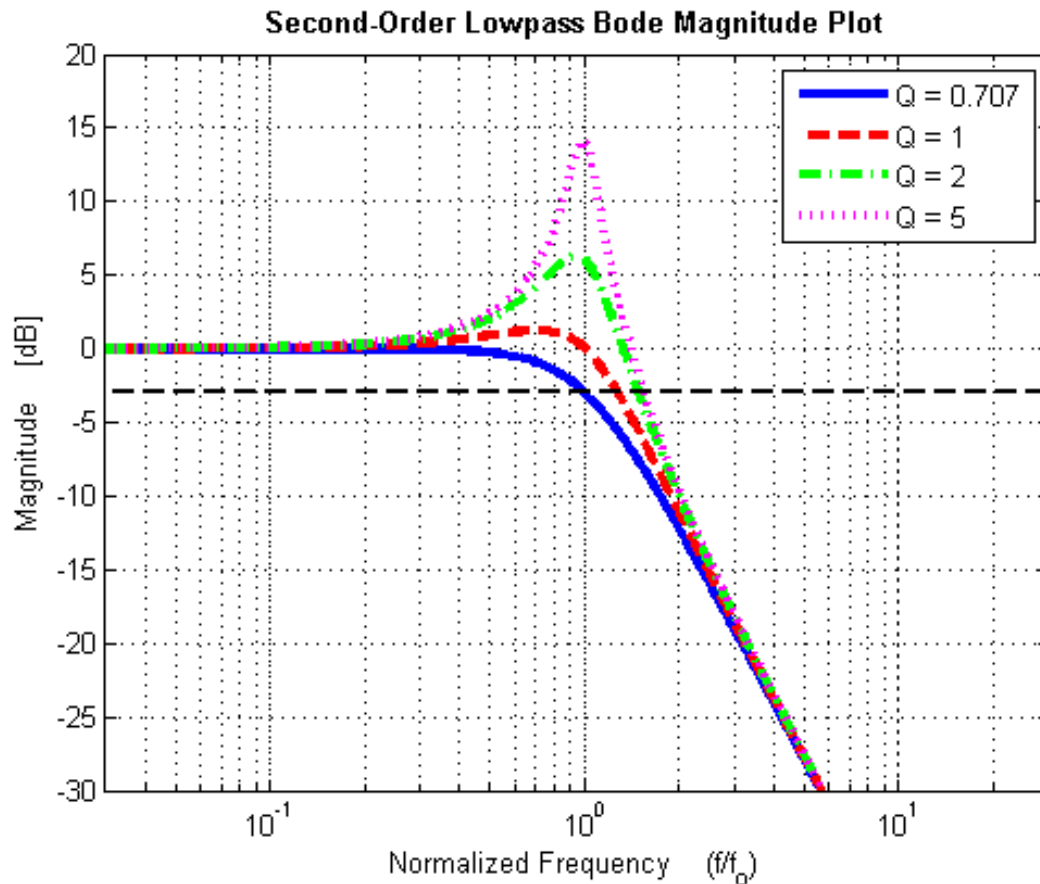

- 3 dB bandwidth is a function of  $Q$ 
  - ▣ Increases with  $Q$
- Peaking occurs for  $Q > 0.707$
- For  $Q = 0.707$ 
  - ▣ **Maximally-flat response**
  - ▣ **Butterworth response**
  - ▣ The 3 dB frequency is equal to the resonant frequency

$$f_c = f_0$$

66

# Second-Order High Pass Filter

# Second-Order High Pass Filter

67

- Second-order high pass filter:
  - ▣ The frequency response function:

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$


where

$$Z_1 = R + \frac{1}{j\omega C} \quad \text{and} \quad Z_2 = j\omega L$$

so

$$H(\omega) = \frac{j\omega L}{R + \frac{1}{j\omega C} + j\omega L} = \frac{(j\omega)^2 LC}{(j\omega)^2 LC + j\omega RC + 1}$$
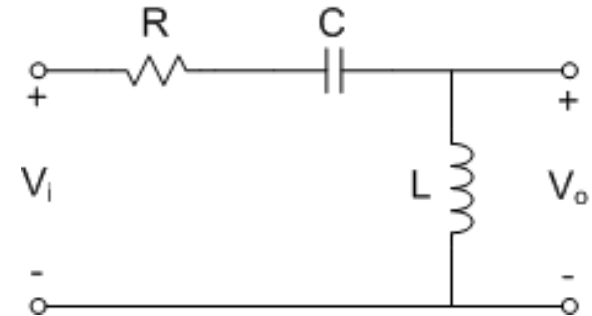
$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + j\omega R/L + 1/LC}$$



# 2<sup>nd</sup>-Order HPF – General-Form Frequency Response

68

## □ **Second-order high pass filter**

- Resonant frequency:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

- Quality factor:


$$Q = \frac{1}{\omega_0 RC} = \frac{\omega_0 L}{R}$$

- Frequency response function:

$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + j\omega R/L + 1/LC}$$

- General form, in terms of  $\omega_0$  and  $Q$ :


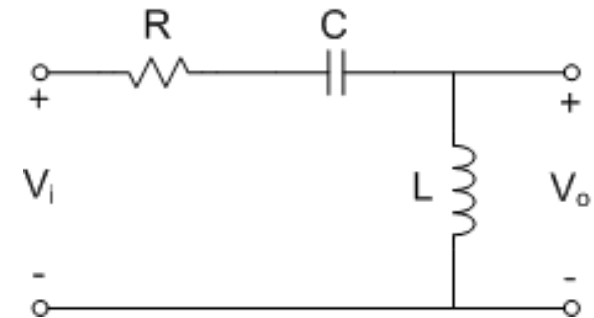
$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2}$$


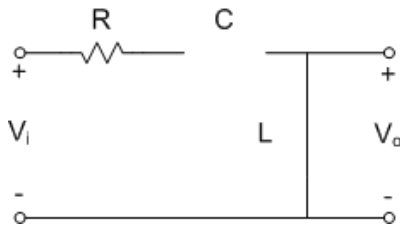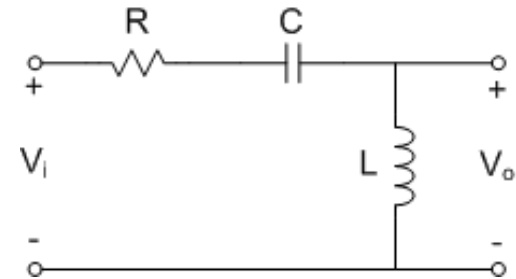
# Second-Order High Pass Filter

69


- Consider the filter's behavior at three limiting cases for frequency



- $f \rightarrow 0$ :
  - $L \rightarrow$  short
  - $C \rightarrow$  open
  - $v_o$  shorted to ground
  - Gain  $\rightarrow 0$

?

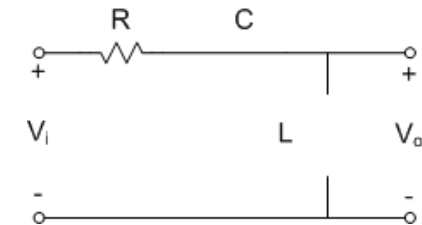- $f = f_0$ :
  - Behavior at resonance is, once again, a bit more complicated



- $f \rightarrow \infty$ :
  - $L \rightarrow$  open
  - $C \rightarrow$  short
  - Current  $\rightarrow 0$
  - $v_o \rightarrow v_i$
  - Gain  $\rightarrow 1$


# Second-Order HPF at Resonance

70

- Input impedance at resonance:  $Z_{in}(\omega_0) = R$
- The series LC section is essentially a short
  - But, neither the inductor nor the capacitor, individually, are shorts
  - And, output is taken across the inductor
    - Recall that at resonance, capacitor and inductor voltages can exceed the input voltage

$Z_{in} = R$ , so

$$\mathbf{I} = \frac{\mathbf{V}_i}{R}$$

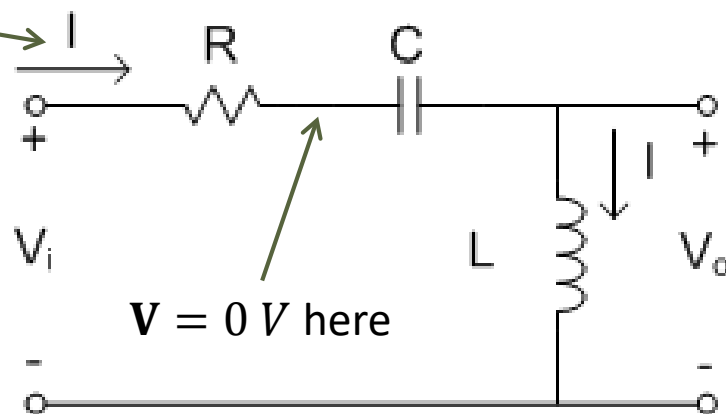

Output voltage phasor is:

$$\mathbf{V}_o = \mathbf{I} \cdot j\omega_0 L$$

$$\mathbf{V}_o = \frac{\mathbf{V}_i}{R} \omega_0 L \angle 90^\circ$$

which may be larger than  $\mathbf{V}_i$

# Second-Order High Pass Filter

71

- Second-order roll-off rate:


$$40 \frac{dB}{dec}$$

- $Q$  determines:
  - ▣ Amount of peaking
  - ▣ Rate of phase transition

- No peaking at all for

$$Q \leq \frac{1}{\sqrt{2}} = 0.707$$

- Phase at  $\omega_0$ :  $+90^\circ$

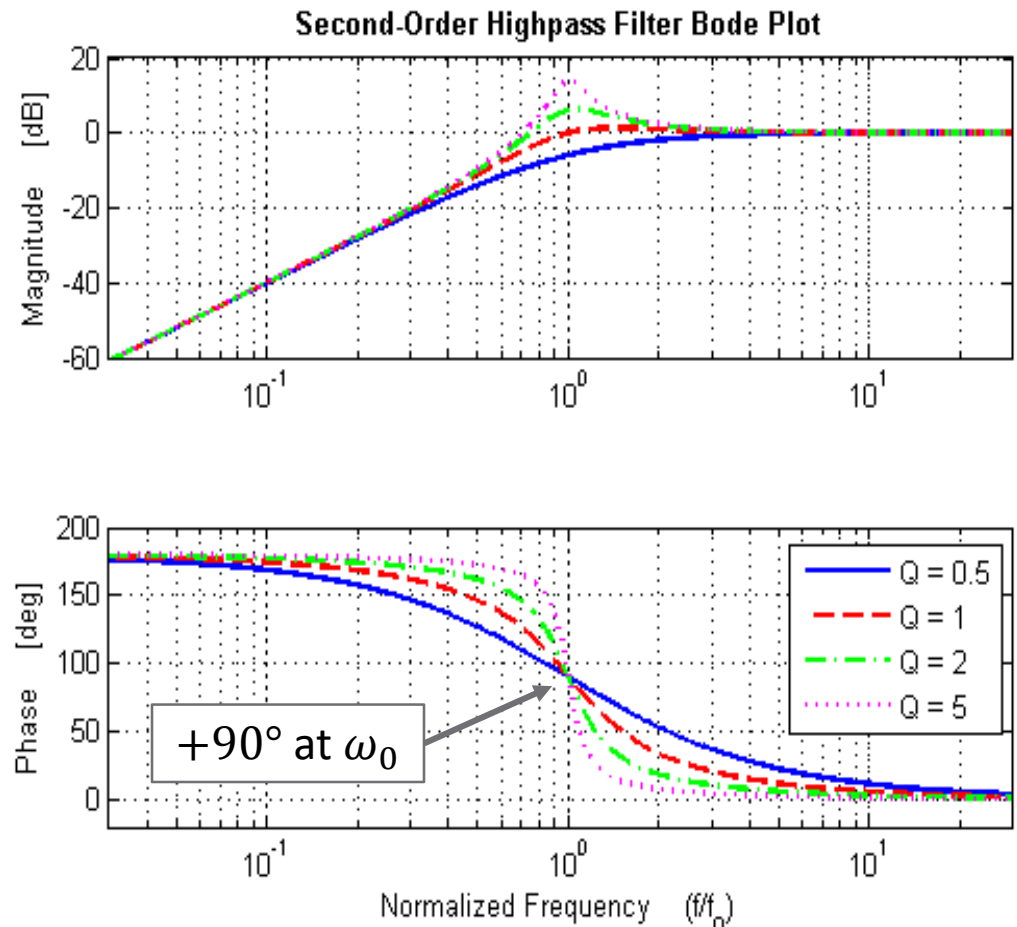


# 2<sup>nd</sup>-Order High Pass Filter – 3dB Bandwidth

72

- Corner frequency is a function of  $Q$ 
  - ▣ Decreases with increasing  $Q$
- Peaking occurs for  $Q > 0.707$
- For  $Q = 0.707$ 
  - ▣ **Maximally-flat response**
  - ▣ **Butterworth response**
  - ▣ The 3 dB frequency is equal to the resonant frequency

$$f_c = f_0$$

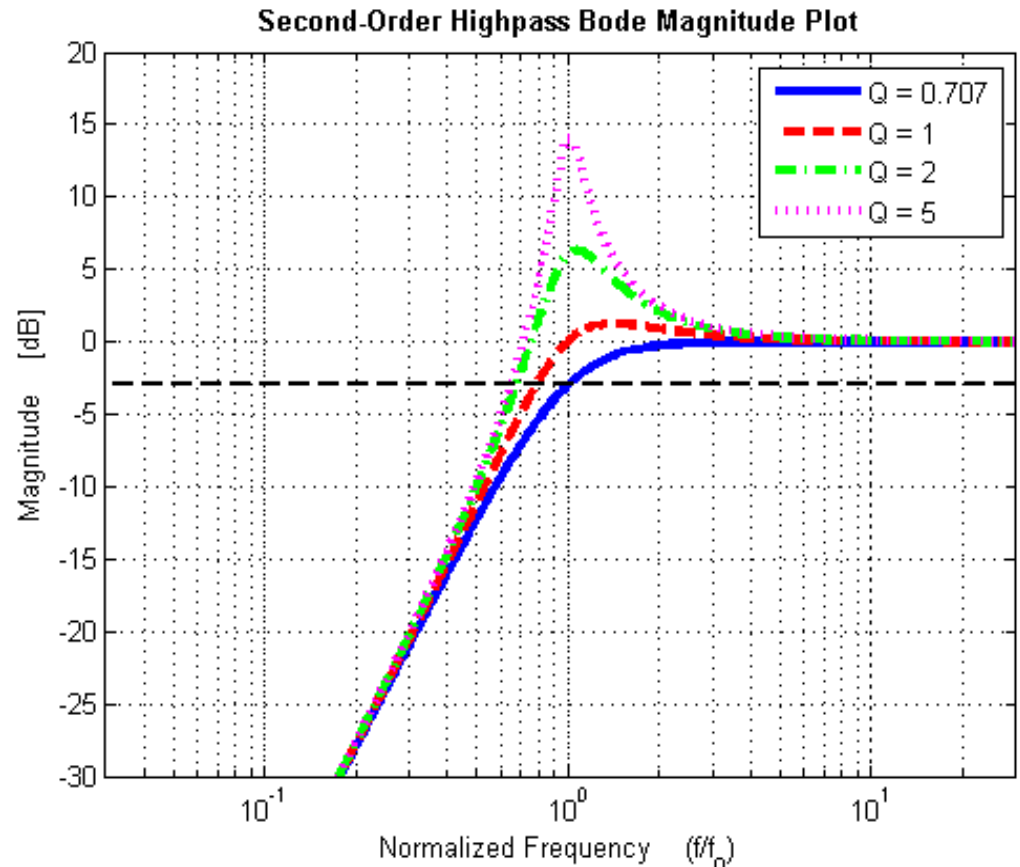



# Damping Ratio - $\zeta$

73

- We've been using **quality factor** to describe second-order filter response
  - A measure of the sharpness of the resonance
  - For band pass/stop filters, Q tells us about **bandwidth**
  - For low/high pass filters, Q tells us about **peaking**

---


- Another way to describe the same characteristic: **damping ratio**,  $\zeta$ 
  - Damping ratio is inversely proportional to Q:

$$\zeta = \frac{1}{2Q}$$

- A measure of the amount of **damping** in a circuit/system
- Higher  $\zeta$  implies a less resonant system
  - Less peaking
  - Wider bandwidth for band pass/stop filters

# 2<sup>nd</sup>-Order Low Pass Response vs. $\zeta$

74

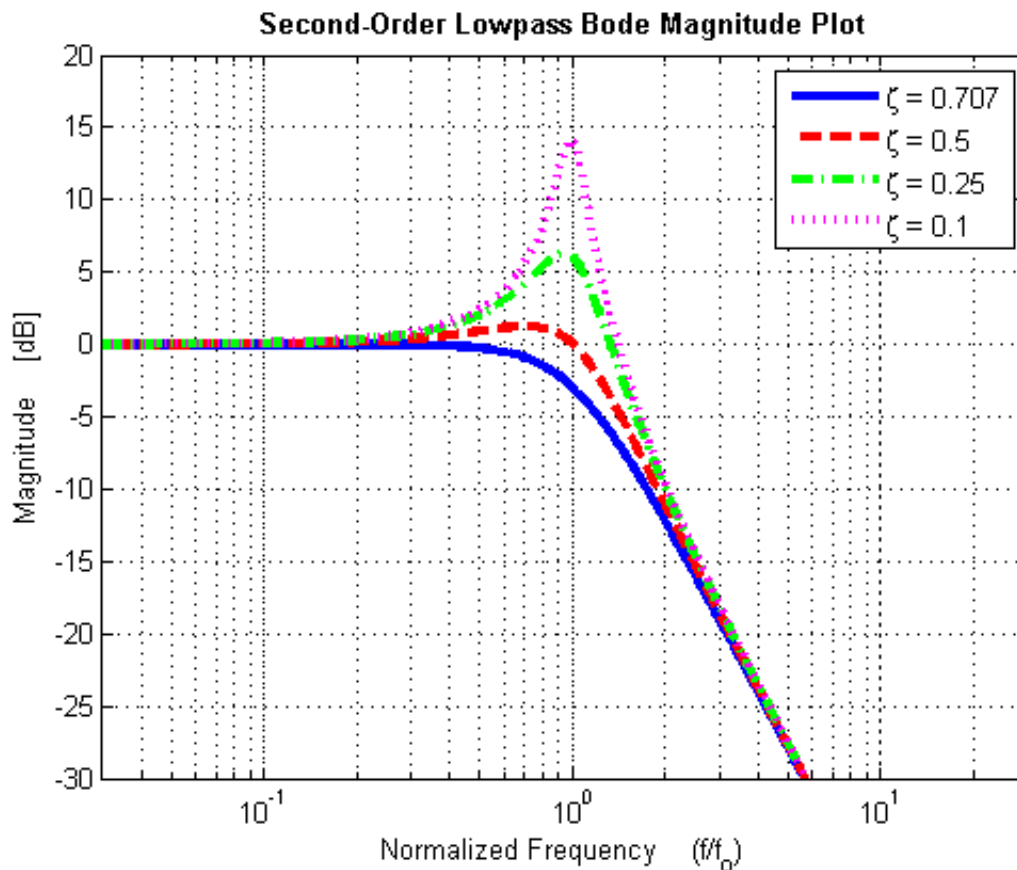

- As  $\zeta$  goes down,
  - ▣ Less damping
  - ▣ More peaking
- No peaking at all for  $\zeta \geq 0.707$
- For  $\zeta = 0.707$ 
  - ▣ **Maximally-flat response**
  - ▣ **Butterworth response**
  - ▣ The 3 dB frequency is equal to the resonant frequency

$$f_c = f_0$$

# General-Form Freq. Response Functions in Terms of $\zeta$

75

Low pass in terms of Q:

$$H(\omega) = \frac{\omega_0^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2}$$

Low pass in terms of  $\zeta$ :

$$H(\omega) = \frac{\omega_0^2}{(j\omega)^2 + 2\zeta\omega_0j\omega + \omega_0^2}$$

High pass in terms of Q:

$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2}$$

High pass in terms of  $\zeta$ :

$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + 2\zeta\omega_0j\omega + \omega_0^2}$$

76

# Audio Filter Demo

# Analog Discovery Instrument

77



- 2-chan. Scope
  - ▣ 14-bit, 100MSa/s
  - ▣ 5MHz bandwidth
- 2-chan. function generator
  - ▣ 14-bit, 100MSa/s
  - ▣ 5MHz bandwidth
- 2-chan. spectrum analyzer
- Network analyzer
- Voltmeter
- $\pm 5V$  power supplies
- 16-chan. logic analyzer
- 16-chan. digital pattern generator
- USB connectivity


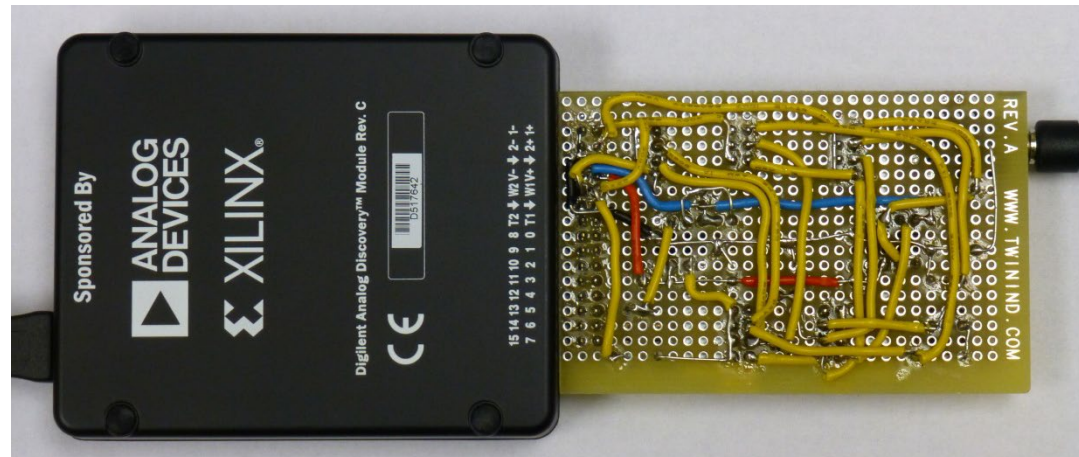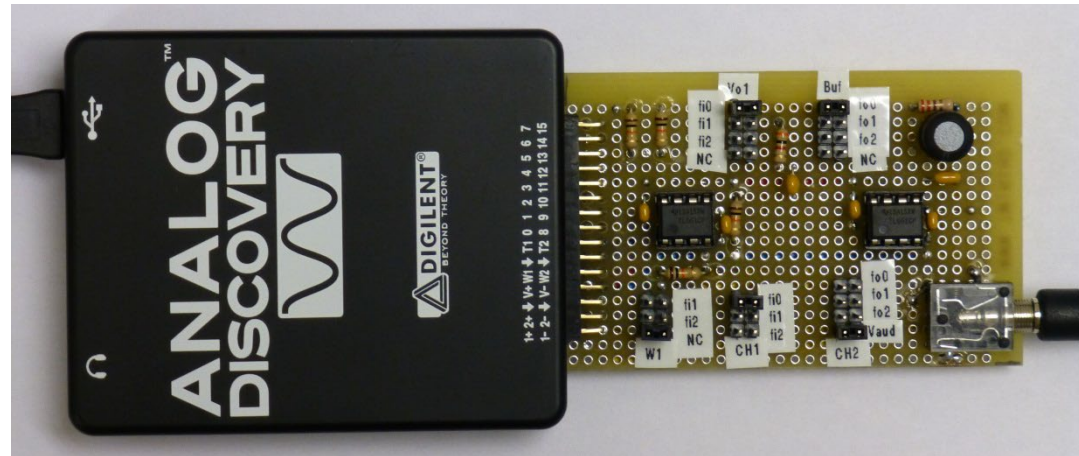
# Analog Discovery – Audio Demo


78

- Demo board plugs in to Analog Discovery module
- Summation of multiple tones
- Optional filtering of audio signal
- 3.5 mm audio output jack



# Analog Discovery – Audio Demo

79

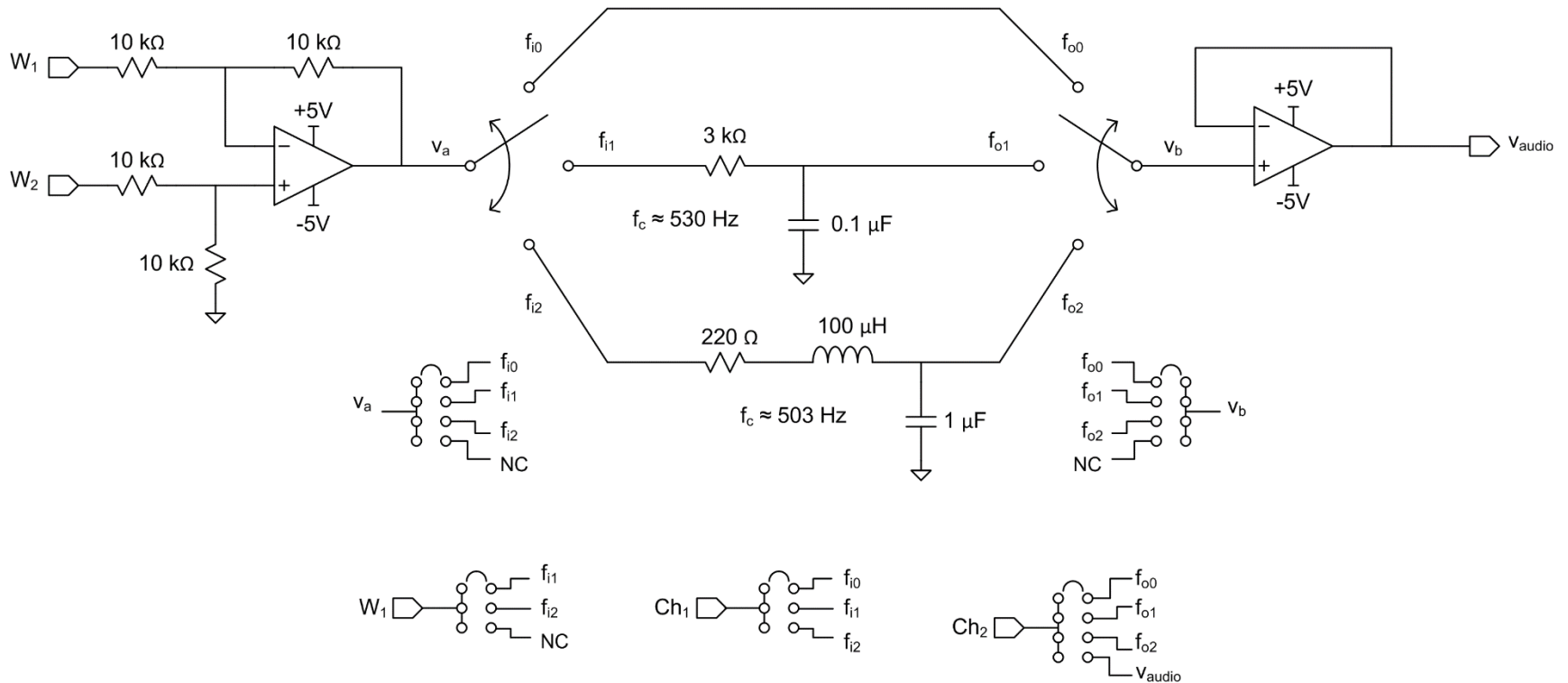

80

# Example Problems



The higher-frequency signal is unwanted noise. Design a second-order Butterworth LPF to attenuate the higher-frequency component by 40 dB.

What is the SNR at the output of the filter?

